



U.S.N 

--	--	--	--	--	--	--	--	--	--

**P.E.S. College of Engineering, Mandya - 571 401**  
 (An Autonomous Institution affiliated to VTU, Belgaum)  
**Fourth Semester, B.E. - Electrical and Electronics Engineering**  
**Semester End Examination; June/July - 2015**  
**Network Analysis - II**

Time: 3 hrs


Max. Marks: 100

Note: Answer **FIVE** full questions, selecting **ONE** full question from each Unit.

**UNIT - I**


1. a What are initial and final conditions in networks? Why is it necessary to study these conditions in networks? Explain with a practical example. 6

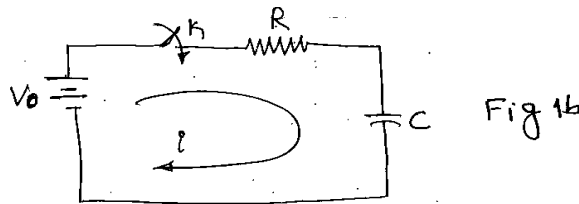b. In the circuit shown in Fig. 1b switch K is closed at  $t = 0$ . Find the expressions for  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  all at  $t = 0+$




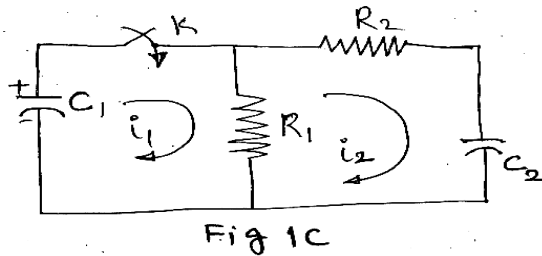c. In the circuit shown in Fig. 1c, capacitor C is charged to 100 V in the polarity shown. Switch K is closed at  $t = 0$ . Find the values of  $i_1$ ,  $i_2$ ,  $\frac{di_1}{dt}$ ,  $\frac{di_2}{dt}$ ,  $\frac{d^2i_1}{dt^2}$ ,  $\frac{d^2i_2}{dt^2}$  all at  $t = 0+$ .


Given;  $C_1 = C_2 = 1\mu\text{F}$ .  $R_1 = R_2 = 10\text{ k}\Omega$ .



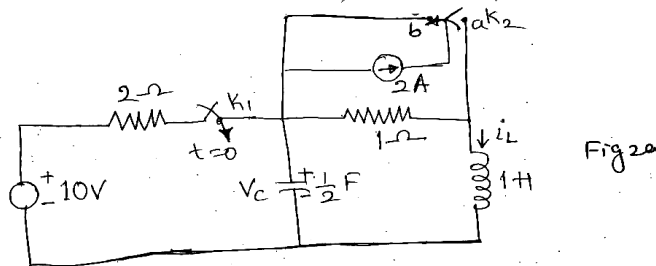2 a. Find  $i_L(0+)$ ;  $v_c(0+)$ ;  $\frac{dv_c(0+)}{dt}$  &  $\frac{di_L(0+)}{dt}$  for the circuit shown in Fig. 2a.



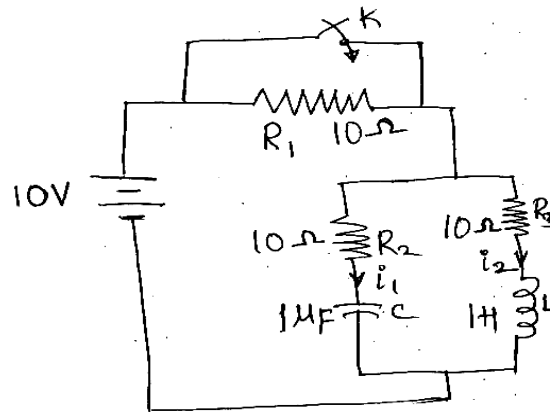b. In the given ckt shown in Fig. 2b steady state is reached with switch K open. Switch K is closed at  $t = 0$ . Find the voltage  $V_c$  across the capacitor and current  $i_2$  through inductor at  $t = 0-$ . Also find the values of  $i_1$ ,  $i_2$ ,  $\frac{di_1}{dt}$  and  $\frac{di_2}{dt}$  at  $t = 0+$ . 10




**UNIT-II**

3 a. Find the inverse Laplace transform of the following functions;

i)  $F(s) = \frac{1}{s(s^2 - \theta^2)}$     ii)  $F(s) = \frac{250}{(s+2)(s^2 + 625)}$

10

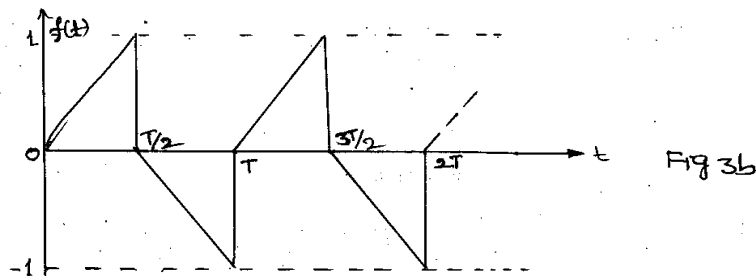b. Find the Laplace transform of the periodic waveform shown in Fig. 3b.




10

4 a. In a series RLC circuit the following equation for the current is obtained. Use Laplace transform to solve the equation and find an expression for current  $i(t)$ .

$\frac{di(t)}{dt} + 3i(t) + 2\int_0^t i(t)dt + 8\delta(t) = 2e^{-3t}$  with  $i(0^-) = 4$  and  $2q(0^-) = 8$ .

10

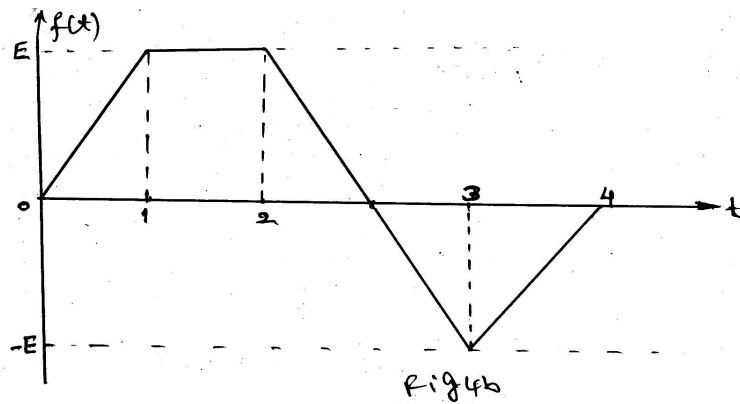
b. Find the Laplace transform of the periodic waveform shown in Fig. 4b using waveform synthesis.



10


UNIT- III

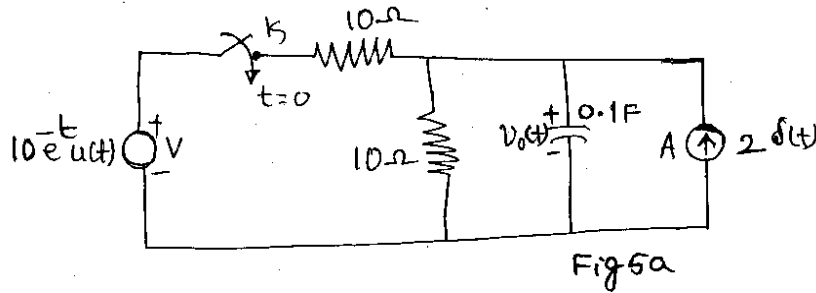- 5 a. For the circuit shown in Fig. 5a, switch K is closed at  $t = 0$ . Find  $V_o(t)$  using Laplace transform. Assume  $V_o(0^-) = 5$  volts.



10

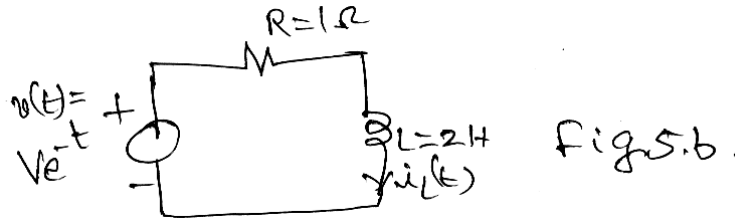
- b. Determine the current in the inductive branch, shown in Fig. 5b, using impulse response.



10

6. a In a series RC circuit with  $R = 10 \Omega$  and  $C = 50 \mu\text{F}$ , switch K is closed at  $t = 0$  connecting a DC voltage source of 100 V to the circuit. The capacitor has an initial charge of 2 nC. Use Laplace transform to find current  $i(t)$  through the circuit at  $t = 0^+$ .
- b. For the circuit shown in Fig. 6b determine an expression for current  $i(t)$  by Laplace transform considering initial conditions given, by writing equations in time domain.

5

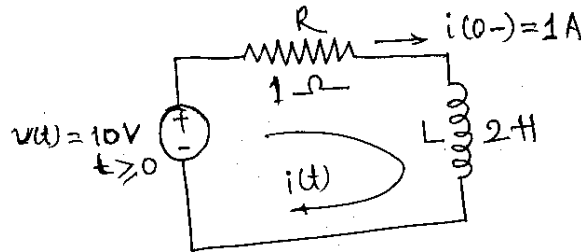

5


- c. If impulse response  $h(t) = 2e^{-3t}u(t)$  and input  $x(t) = u(t) - \delta(t)$  determine output  $r(t)$  using convolution theorem and verify the same by finding inverse Laplace transform.

10

UNIT - IV


- 7 a. List the restrictions on locations of poles and zeros in driving point functions.
- b. For the circuit shown in Fig. 7b find  $Z_{in}$  and voltage ratio transfer function.

4

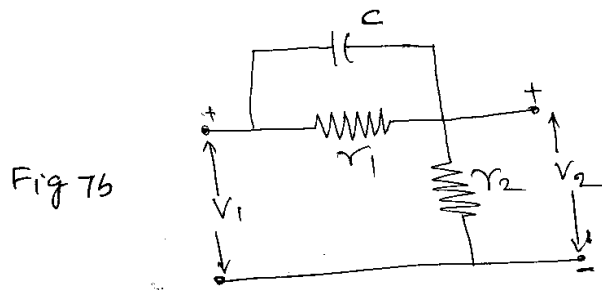

6

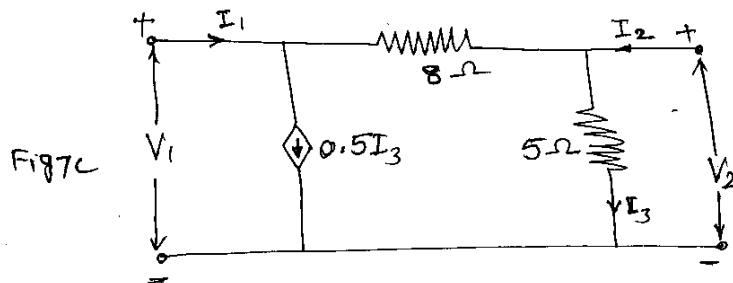c. Obtain the z parameters for the  $\pi$  network shown in Fig. 7C.




10

8 a. Obtain the pole – zero diagram of the given function and obtain the time domain response.

$$I(s) = \frac{2s}{(s+1)(s^2+2s+4)}$$

10

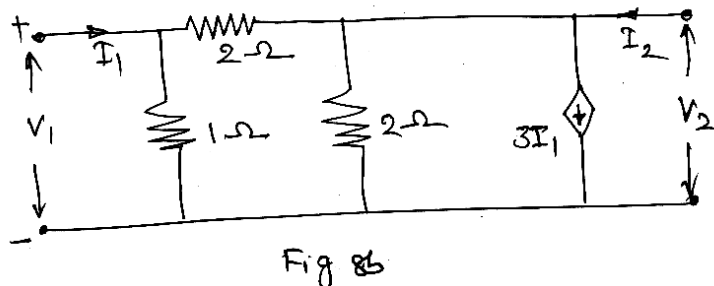b. Determine Y parameter and hence Z parameters of the circuit shown in Fig. 8b.



10

UNIT - V

9 a. Explain the properties of Hurwitz polynomial.

8

b. Check whether the following functions are Hurwitz polynomial.

i)  $F(s) = s^7 + 3s^5 + s^3 + 2s$       ii)  $F(s) = s^4 + s^3 + 3s^2 + 2s + 2$

12

10 a. The driving point impedance of a one port LC network is given by

$$Z(s) = \frac{(s^2+1)(s^2+3)}{s(s^2+2)(s^2+4)}$$

obtain the first and second form of Foster network.

10

b. A driving point function is give by  $F(s) = \frac{s^2+6s+8}{s^2+4s+3}$ . Show that the function can be realized in both cauer RC and RL forms.

10

\* \* \* \* \*