



--	--	--	--	--	--	--	--	--	--

P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belgaum)
Fifth Semester, B.E. - Electrical and Electronics Engineering
Semester End Examination; Dec. - 2014
Operational Amplifiers and Linear Integrated Circuits

Time: 3 hrs

Max. Marks: 100

Note: i) Answer any **FIVE** full questions, selecting at least **TWO** full questions from each part
 ii) Op-amp data sheet and resistor, capacitor standard value list are permitted.

PART - A

1. a. Sketch the circuit of a high Z_{in} capacitor-coupled voltage follower. Briefly explain the design operation. 8
- b. A capacitor coupled non-inverting amplifier is to be designed to have $A_v = 90$ and $V_o = 3$ V. The load resistance is 10 k Ω and the lower cut off frequency is to be 70 Hz. Design the circuit using a 741 Op-amp. Assume; $R_2 = 56$ k Ω 8
- c. Sketch the circuits for:
 - i) Capacitor coupled voltage follower using a single polarity supply. 4
 - ii) Capacitor coupled non inverting amplifier using a single polarity supply.
- 2 a. What is Barkhausen Criteria? Explain phase margin and also sketch typical gain/frequency response, and phase/frequency response graphs. 8
- b. With a neat circuit show that compensating for stray capacitance can be achieved by making time constant $C_2R_2 = C_5R_1$ 6
- c. List out any six precautions that should be met for OP-amp circuit stability. 6
- 3 a. With a neat circuit diagram, explain precision full-wave rectifier with a combination of Half wave rectifier and summing circuit. 8
- b. With a neat circuit explain symmetrical precision clipper with the necessary waveforms. 10
- c. List the advantages of precision rectifier over an ordinary diode circuit. 2
- 4 a. Discuss the circuit operation of an inverting op-amp Schmitt trigger circuit with relevant Diagrams. 6
- b. Draw the circuit of an op-amp Monostable multi vibrator. Show the relevant voltage waveforms and explain its operation. 8
- c. A capacitor coupled zero-crossing detector is to handle a 1khz square wave input with a peak-to-peak amplitude of 6 V. Design a suitable circuit using a 741 op-amp with a ± 12 V supply. Assume $V_{BE} = 0.1V$ and $\Delta V = 1V$. 6

Contd.....2

PART - B

- 5 a. Draw the circuit of a RC phase shift oscillator with amplitude stabilization. Discuss the role of adjustable resistor included in such a circuit and explain the design issues concerned. 10
- b. Sketch a Wein Bridge Oscillator and explain circuit operation. Also design Wein Bridge Oscillator using a BIFET op-amp with a supply a ± 12 V, to have an output frequency of 15 kHz. 10
- 6 a. Show how a band stop filter can be constructed using a low pass filter and a high –pass filter. Draw the expected frequency response and explain the band-stop filter operation. 10
- b. Design:
- i) First-order active low-pass filter circuit with a cut-off frequency of 1 kHz 10
- ii) Second order active low-pass filter circuit with a cut off frequency of 1 kHz. Both using 741 Op-amp.
- 7 a. What is PLL? Mention its application and explain its principle of operation using relevant diagrams. 6
- b. Draw the circuit of a universal active filter and explain its operations. 6
- c. Explain integrated circuit-voltage regulator with relevant circuit diagram. 8
8. Write explanatory notes on the following with relevant diagram and waveforms: 6
- i) Small signal and power amplifiers. 8
- ii) Triangular/Rectangular wave generator 6
- iii) Adjustable output regulator.

* * * * *