



--	--	--	--	--	--	--	--	--	--

## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Fifth Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec. - 2015

Power Electronics

Time: 3 hrs

Max. Marks: 100

**Note:** Answer **FIVE** full questions, selecting **ONE** full question from each **unit**.

### UNIT - I

- 1 a. Define Power electronics. Explain the Power Electronic converter system with the help of block diagram. Explain the peripheral effects and their remedies. 10
- b. Describe the construction and switching characteristics of a MOSFET. 10
- 2 a. Draw the circuit symbol, VI characteristics and one application of various types of semiconductor devices. 10
- b. Explain the switching characteristics of a transistor. 6
- c. Give the comparison between MOSFET and BTJ. 4

### UNIT - II

- 3 a. Explain any two methods of base drive control with relevant circuit and expressions. 8
- b. Discuss the methods of providing Isolation of drive circuits from power circuits. 4
- c. Explain the two transistor model of a thyristor and comment on their switching characteristics. 8
- 4 a. Explain  $\frac{di}{dt}$  and  $\frac{dv}{dt}$  effects and their protection. Explain the operation of Snubber circuit. 10
- b. What is the need of series and parallel operation of thyristors? With relevant circuit and VI characteristics explain series and parallel operation. 10

### UNIT - III

- 5 a. Mention and explain the various types of communication circuits in brief. 10
- b. What do you mean by AC voltage controller? Explain the principle of ON/OFF Control ACVC. Derive an expression for its rms O/P voltage. 10
- 6 a. Explain the working of a resonant pulse SCR communication circuit with necessary diagram and waveforms. 8
- b. An impulse commutated thyristor circuit has  $V_s = 200$  V,  $R = 10 \Omega$ ,  $C = 5 \mu\text{F}$ . Determine the available turn OFF time of the circuit if capacitor is initially charged to  $-V_0 = -V_s$ . 4
- c. Explain why short duration pulses are not suitable for ACVC with inductive loads. 4

- d. A full wave ACVC controller supplies to a resistive load of  $R = 10 \Omega$  from an input voltage  $V_s = 200 \text{ V}$ , 60 Hz. The delay angles of the thyristors are equal  $\alpha_1 = \alpha_2 = \pi/2$ . Determine ; 4
- i) RMS output voltage and      ii) Input power factor.

#### UNIT - IV

- 7 a. Explain the principle of operation of step up chopper with the circuit and waveforms. 6
- b. A step up chopper has an input voltage of 220 V and output voltage of 660 V. If the conducting time of the thyristor chopper is 100  $\mu\text{s}$ , compute the pulse width of output voltage. 4
- c. Give the comparison between half bridge and full bridge inverters. 6
- d. A single phase full bridge inverter has  $R = 10 \Omega$  and the DC input voltage is  $V_s = 220 \text{ V}$ . Calculate; 4
- i) RMS output voltage
- ii) Average and peak current of thyristor
- iii) Output power.
- 8 a. Explain one, two and four quadrant choppers with relevant circuit and operating characteristics. 10
- b. With necessary circuit and waveforms, explain 3 phase bridge inverter in  $120^\circ$  mode. 10

#### UNIT - V

- 9 a. Mention the applications of Converters? Explain the principle of operation of  $1\phi$  half wave converter with RL load. Derive an expression for its output voltage. 10
- b. The  $1\phi$  full converter is operating from a 120 V, 50 Hz supply and provides an average load current of 5 A at a delay angle of  $\alpha = 30^\circ$ , if the ripple content of the load current is negligible. Calculate; 10
- (i) DC load voltage
- (ii) DC output power
- (iii) The quantities mentioned above when freewheeling diode is connected to the same circuit.
- 10 a. With necessary circuit and waveforms, explain the operation of  $1\phi$  full bridge converter. 10
- b. With necessary circuit and waveforms, explain the operation of  $3\phi$  half controlled converter. 10

\* \* \* \*