



--	--	--	--	--	--	--	--	--	--

P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Fifth Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec. - 2015

Operational Amplifier and Linear Linear Integrated Circuits

Time: 3 hrs

Max. Marks: 100

- Note:** i) Answer **FIVE** full questions, selecting **ONE** full question from each **unit**.
 ii) Assume missing data suitably if any.
 iii) Use of resistor and capacitor standard values list and op-amp data sheets are permitted.

UNIT - I

- 1 a. Sketch and design a capacitor coupled voltage follower and briefly explain the operation of the name. 6
- b. Design a high input impedance capacitor coupled voltage follower with a cut off frequency of 50 Hz and load resistance of 3.9 k Ω . Also determine the minimum theoretical input impedance of the circuit. 8
- c. Sketch the circuit of an inverting amplifier and show how the upper cut off frequency can be set for the same. 6
- 2 a. Sketch and design a high Z_{in} capacitor coupled non investing amplifier and briefly explain the operation of the same. 6
- b. Using a 741 op-amp, design a capacitor coupled non investing amplifier to have a voltage gain of 66 with load resistor of 2.2 k Ω and LCF of 120 Hz. Assume $V_i = 15$ mV. 8
- c. Sketch and design a capacitor coupled inverting amplifier using single polarity supply. 6

UNIT - II

- 3 a. Sketch typical gain / frequency and phase / frequency response, and discuss the stability of high gain and low gain amplifiers. 8
- b. Sketch the circuit for phase lag and phase lead compensation and briefly explain the circuit operation. 6
- c. Using a 709 op-amp, design an inverting amplifier to have $A_u = 100$ and $V_s = 50$ mV. Select suitable compensating components. 6
- 4 a. Discuss the effect of stray capacitance on op-amp circuit stability. Write the equations to determine the value of input stray capacitance that might produce instability. 8
- b. Explain miller effect. Derive an equation relating the input capacitance of an inverting amplifier to the capacitance connected between input and output terminals. 6
- c. Using LM 108 op-amp, design an inverting amplifier to amplify a 100 mV signal by a factor 3. Select suitable frequency compensation. 6

UNIT - III

- 5 a. With neat circuit diagram and relevant waveforms, explain precision full wave rectifier. 8
- b. Design an adjustable peak clipping circuit to clip at approximately $\pm (3 \text{ V to } 5 \text{ V})$. The circuit is to have unity voltage gain before clipping. 6
- c. With neat circuit diagram and relevant waveforms explain plan shift oscillator. 6
- 6 a. Draw the circuit of a triangular / rectangular waveform generator which has frequency and duty cycle controls. Show all waveforms and explain the circuit operation. 8
- b. Using a BIFET op-amp with a supply of $\pm 12 \text{ V}$, design a Wein bridge oscillator to have an output frequency of 15 kHz. 6
- c. With a neat circuit diagram and relevant waveforms, explain sample - and - hold circuit. 6

UNIT - IV

- 7 a. Draw an op-amp Non – Inverting Schmitt trigger circuit and explain its operation. 6
- b. Using 741 op-amp with a supply of $\pm 12 \text{ V}$, design an Inverting Schmitt trigger circuit to have trigger points of $\pm 2 \text{ V}$. 8
- c. Sketch the circuit of second order active high pass filter. Briefly explain its operation. 6
- 8 a. Draw an Astable multivibrator. Explain the circuit operation with relevant waveforms. 8
- b. Discuss the differences between wide band and narrow band pass filters. Sketch typical frequency responses and write the related equation. 6
- c. Using 741 op-amp, design a first order active low pass filter to have cut off frequency of 1 kHz. 6

UNIT - V

- 9 a. Briefly explain the action of a dc voltage regulator. Write the equations for line regulation, load regulation and ripple rejection. 8
- b. Briefly explain the circuit operation of adjustable output regulator. 6
- c. Draw the relevant sketch and explain the operation of a universal Active filter. 6
- 10 a. What is PLL? Mention its application and explain its principle of operation using relevant diagrams. 8
- b. Explain the basic circuits 723 Integrated circuit voltage regulation. 6
- c. What is a power booster? With example explain the need of it. 6

* * * *