

--	--	--	--	--	--	--	--	--	--



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Fifth Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec - 2016/Jan - 2017

Power Electronics

Time: 3 hrs

Max. Marks: 100

Note: i) Answer **FIVE** full questions, selecting **ONE** full question from each unit.
ii) Assume missing data if any.

UNIT - I

- 1 a. List the major types of power electronic circuits and mention in each case, the type of input supply given and the output we get. 8
- b. Mention two applications of each power electronic converter. 6
- c. What are the peripheral effects of power electronic equipment? 6
- 2 a. With neat wave forms, explain the switching characteristics of Power B.J.T. 8
- b. List the merits, demerits and applications of MOSFETs. 9
- c. Compare BJT and IGBT. 3

UNIT - II

- 3 a. What is $\frac{di}{dt}$ and $\frac{dv}{dt}$? How power electronic devices are protected against $\frac{di}{dt}$ and $\frac{dv}{dt}$? 8
- b. What is isolation? Why isolation is necessary in power electronic circuits? Explain in brief. 5
- c. Explain the typical gate drive circuit for MOSFET. 7
- 4 a. Using two transistor analogy explain the principle of switching on of an SCR. 8
- b. A SCR is connected in series with a 0.5 H inductor and 20 Ω resistance. A 100 V DC voltage is applied to this circuit. If the latching current of the SCR is 4 mA, find the maximum width of the gate triggering pulse required to properly turn - ON the SCR. 5
- c. Briefly explain the necessity of series and parallel connection of thyristors. 7

UNIT - III

- 5 a. Distinguish between natural commutation and forced commutation for SCR with illustrative examples. 10
- b. Explain with the help of a circuit and relevant wave forms, the commutation of SCR using an LC circuit. 10
- 6 a. What is AC voltage controller? Explain two types of AC voltage control. 5
- b. Derive an expression for R.M.S. and average value of output voltage for 1- ϕ half wave controller. 10
- c. What are the advantages and disadvantages of ON-OFF control used in AC voltage controllers? 5

UNIT - IV

- 7 a. Derive an expression for average and r.m.s. value of the load voltage for the step down chopper having inductive load. 10
- b. A chopper circuit drives an inductive load from 200 V DC supply. Given the load resistance as 4Ω , the average load current as 30 A and operating frequency is 400 Hz. Compute the ON period and OFF period of the chopper. Also determine the duty cycle of the chopper. 10
- 8 a. Explain the operation of a 1- ϕ full wave bridge inverter. 10
- b. Explain 120° mode of 3- ϕ inverters with the help of wave forms. 10

UNIT - V

- 9 a. Derive an expression for average value of o/p voltage for 1- ϕ half wave controlled rectifier for RL load and freewheeling diode. 10
- b. A 1- ϕ half wave converter is operated from a 120 V, 50 Hz supply and the load resistance $R = 10 \Omega$. If the average output voltage is 25% of the maximum possible average o/p voltage, calculate: 10
- i) Delay angle α
- ii) Average of r.m.s. output currents
- iii) Average and r.m.s. thyristor currents.
- 10 a. What is a dual converter? Draw the power circuit arrangement of a 1 ϕ dual converter. What are the applications of dual converters? 10
- b. Derive the expression for average o/p voltage of 3 ϕ half wave converter for highly inductive load. 6
- c. What are the advantages of 3- ϕ rectifiers over single phase rectifier circuits? 4

* * *