



**P.E.S. College of Engineering, Mandya - 571 401**

*(An Autonomous Institution affiliated to VTU, Belgaum)*

**Sixth Semester, B.E. – Electrical and Electronics Engineering**

**Semester End Examination; June/July - 2015**

**Advanced Power Electronics**

*Time: 3 hrs*

*Max. Marks: 100*

**Note:** Answer any **FIVE** full questions, selecting atleast **TWO** full questions from **each part**.

**PART – A**

1. a. What are the different topologies of dc-dc converter systems? Draw the equivalent circuits in each case. 6
- b. Explain the operation of a buck-boost converter with relevant equivalent circuits for the switch states and wave diagrams. 6
- c. The inductance in a buck-boost converter operating at 20 kHz is 0.05 mH. The input voltage is 15 V and the capacitor is sufficiently large. Calculate the duty ratio if the output voltage is to be regulated at 10 V when supplying a load of 10 W. 8
2. a. Explain the operation of full bridge dc – dc converter with bipolar voltage switching. 8
- b. Explain the operation of Cuk converter. 6
- c. In a Cuk converter operating at 50 kHz,  $L_1 = L_2 = 1$  mH and  $C_1 = 5\mu\text{F}$ . The output capacitor is sufficiently large to keep output voltage constant. The converter is fed at 10 V and the output voltage is regulated to be constant at 5 V when supplying a load of 5 W. Assuming continuous current conduction mode, calculate the percentage errors in assuming constant voltage across  $C_1$  or in assuming constant inductor currents. 6
3. a. What are voltage source inverters? Explain the basic concepts used in the three VSI categories. 6
- b. Explain the operation of a single – phase full – bridge inverter with the help of necessary circuit diagram and waveforms. 6
- c. A single-phase full-bridge inverter operating at 400 Hz with an input dc voltage of 220 V supplies an RLC load with  $R = 5 \Omega$ ,  $L = 10$  mH, and  $C = 26 \mu\text{F}$ . Determine the rms load current and the TDH of the load current considering only up to 5<sup>th</sup> harmonic. 8
4. a. Explain the operation square wave inverter. 6
- b. Discuss the effect of blanking time on the output voltage of a single-phase full-bridge inverter. 6
- c. Explain the operation of a full bridge inverter using PWM with unipolar voltage switching with relevant diagrams. 8

**PART - B**

5. a. What are the limitations of switch-mode converters? How are these limitations minimized in resonant converters? Give the classification of resonant converters. 6
- b. Explain the operation of any one ZCS resonant-switch converter configurations with the necessary diagrams. 8
- c. A thyristor based resonant RLC inverter has  $R = 1 \Omega$ ,  $L = 0.1 \text{ mH}$ , and  $C = 10 \mu\text{F}$ . Find the maximum switching frequency for non-overlap operation if the turn-off time of the thyristor is  $12 \mu\text{s}$ . 6
6. a. Explain the operation of a fly back converter with the help of circuit diagram and waveforms. 6
- b. Explain the operation of an actively clamped resonant inverter. 6
- c. Explain the basic operation of a resonant-dc-link inverter with zero-voltage switching. 8
7. a. Explain the two basic configurations of an UPS system. 6
- b. Give the basic configurations of switched-mode dc power supplies. 6
- c. The dc output voltage of a dc push-pull converter is 24 V at a resistive load of  $0.4 \Omega$ . The on-state voltages of transistor and diodes are 1.2 V and 0.7 V respectively. The primary to secondary turn's ratio of the transformer is 2. Determine the average input current, and the efficiency. Assume ideal transformer and neglect input and output ripple currents. 8
8. a. What are the problems of the transformer core? How can these be minimized? 4
- b. Explain the procedure the single-pass method of designing a transformer, with flow chart. 8
- c. Describe the algorithmic steps involved in the single-pass algorithm for the design of inductors. 8

\* \* \* \* \*