



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Sixth Semester, B.E. – Electrical and Electronics Engineering

Semester End Examination; June/July - 2015

Programmable Logic Controller

Time: 3 hrs

Max. Marks: 100

Note: i) Answer any **FIVE** full questions, selecting atleast **TWO** full questions from each part.

ii) Missing data may suitably assumed

PART-A

- 1 a. What is PLC? Briefly explain the basic functional components of a PLC system with figure. 10
- b. Explain the following PLC I/O devices. i) Reed switch ii) Photoelectric sensors iii) Relay 10
- 2 a. With diagrams explain the terms sourcing and sinking in a PLC system. 8
- b. Briefly explain the advantages and disadvantages of PLC. 6
- c. Explain the location of stop and emergency switches for safe operation of motors with necessary diagrams. 6
- 3 a. What is ladder diagram? Explain the conventions adopted in drawing ladder diagram with an example. 10
- b. Write ladder diagram, functional block diagram and I/O timing diagram for OR and NOR logic. 6
- c. Draw the ladder diagram and functional block diagram for the given Boolean equation. 4
- $$Y = A\bar{B} + \bar{A}B$$
- 4 a. Define sequential function charts (SFC) and structured text (ST). Part of the washing cycle of a domestic washing machine where the drum is to be filled with water and then when full, a heater has to be switched ON and remain ON until the temperature reaches the required level. Then the drum is to be rotated for a specific time. Draw the sequential function chart and ladder diagram for the above washing machine problem. 10
- b. Explain conditional statements and iteration statements used in structured text program with an example. 10

PART - B

- 5 a. What are internal Relays? Illustrate the function of one-shot operation with an example. 10
- b. Write the importance of Master Control Relay (MCR) and explain with ladder diagram the master control relay. 10
- 6 a. Devise a ladder diagram which can be used to maintain an o/p ON, even when the input ceases and when there is power failure. Explain the type of relay used. 10
- b. Name 3 different forms of timers. With timing diagram example ON-delay and pulse timers. 10

- 7 a. Show how a ON-delay timer can be used to produce on OFF – delay timer. With ladder diagram and timing diagram explain OFF – delay timer. 8
- b. Explain basic counter program with the help of ladder diagram and program instructions. 6
- c. Devise a ladder program for system that shows a red light when the count is less than 5 and a green light when it is equal to or greater than 5. 6
- 8 a. With ladder diagram explain 4-bit shift register. 8
- b. What is drum sequencer? With timing diagram explain drum sequencer. 6
- c. Program the PLC to perform basic arithmetic operations. 6

* * * * *