



--	--	--	--	--	--	--	--	--	--

## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution under VTU, Belgaum)

**Eighth Semester, B.E. – Electrical and Electronics Engineering**

**Semester End Examination; June/July - 2015**

**HVDC Power Transmission**

*Time: 3 hrs*

*Max. Marks: 100*

*Note: i) Answer any FIVE full questions, selecting at least TWO full questions from each part  
ii) Smith chart will be provided.*

### PART – A

1. a. Compare AC and DC transmission based on their relative, technical performance and reliability. 10
- b. Mention the principle applications and limitations of DC transmission. 6
- c. Explain the various types of DC links along with their schematic connections diagrams. 4
2. a. Discuss the turn- on and turn – off switching characteristics of thyristor. 10
- b. Discuss the properties of converter circuits. 5
- c. Define pulse number and comment on choice of best converter configuration. 5
- 3.a. State any three HVDC projects in India and mention their technical specifications. 6
- b. Bring out the comparison between AC and DC transmission systems on the economics of power transmission front. Explain the significance of ‘Breakeven distance’ in this context. 6
- c. Discuss the choice of optimum system voltage for a fixed power transfer over long distance transmission lines. 8
- 4.a. Perform the analysis of Gratez circuit (i) with no overlap, and (ii) with overlap less than 60 degrees. Obtain the expression for average direct voltage in each case. 12
- b. A bridge connected rectifier is fed from 220 kV / 110 kV transformer with primary connected to 220 kV. Determine the DC output voltage when the commutation angle is 15° and delay angle is 30°. 8

### PART – B

- 5.a. Explain the basic principles of controlling the voltage at any point on the DC line and the current. Mention the considerations influencing the selection of control characteristics. 10
- b. Discuss the actual characteristics of converter control. In this context, explain the significance of current margin and its range. 6
- c. Explain the general forms of equations for average DC current and average DC voltage in terms of ignition advance angle  $\beta$  and extinction advance angle  $\gamma$  leading to equivalent circuit representation for the inverter. 4

- 6. a. Mention the limitations of manual control. 5
- b. What are MTDC system? Explain the two configurations of MTDC systems. 5
- c. What is mode ambiguity and in this context explain the modification of V-I characteristic for mode stabilization. 10
- 7. a. With suitable assumptions, analyze and workout the expression for optimal value of resistance for damping the oscillations in the DC line. 10
- b. Discuss the procedure for clearing the line faults and re-energizing the line. 10
- 8. a. Define Characteristic and Non-characteristic harmonics. Explain the troubles caused by harmonics and functioning of harmonics filters. 10
- b. Explain the phenomenon of 'Telephone interference' and the factors affecting it in detail. 10

\* \* \* \* \*