



U.S.N

--	--	--	--	--	--	--	--	--	--

P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Third Semester, B.E. – Electronics and Communications Engineering

Semester End Examination; Dec. - 2014

Transistor Circuits


Time: 3 hrs

Max. Marks: 100


Note :i) Answer **FIVE** full questions, selecting **ONE** full question from each Unit.
 ii) Assume suitable missing data if any.

Unit - I

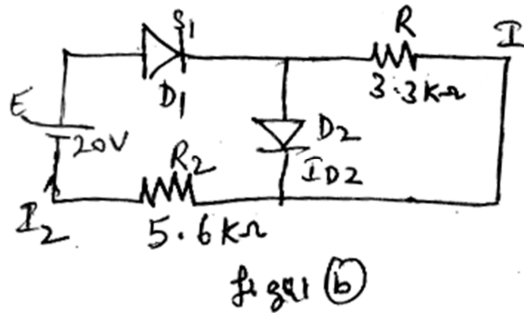- 1 a. Discuss the approximate and piecewise linear model of a diode. 6
- b. Determine the current I_1 , I_2 and I_{D2} for the network shown below in Fig. (b)



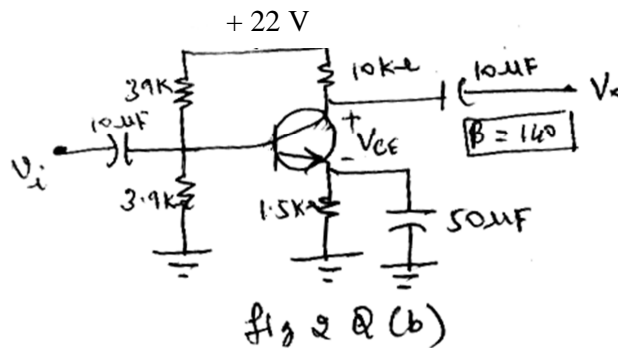- c. What is a clamper? With a neat circuit and waveform explain positive clamper. 6
- 2 a. What is biasing of a transistor? Explain the factors that affect selection of Q point anywhere in active region for the transistor to operate as an amplifier. 6
- b. Determine the dc bias voltage V_{CE} and the current I_C for the voltage divider configuration of Fig. 2 (b) shown below.




- c. With the help of a neat diagram explain the use of transistor as an inverter. 6

Unit - II

- 3a. What are the advantages of using hybrid model to represent the transistor? Explain how h – parameter can be obtained from the transistor. 6
- b. For the CE amplifier circuit derive the expression for A_i , Z_i , A_v and V_o in term of transistor h – parameter. 8

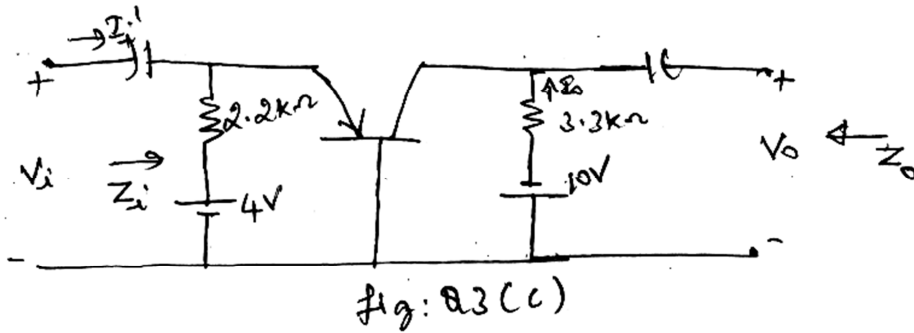- c. For CB configuration shown below in Fig.3 (c), determine Z_i , Z_o , A_v and V_i



6

- 4 a. Briefly explain the miller effect capacitance. 10
 b. Discuss the factors that affect the low frequency response of a BJT – CE amplifier. 10

Unit - III

- 5 a. With a neat diagram, determine the expression for Z_{in} , A_v , Z_o for a Darlington emitter follower. 10
 b. Compare the cascade and cascode connection. List the advantages and disadvantages. 10
 6 a. Explain the feedback connection types with a neat diagram and tabulate the summary of gain without feedback and gain with feedback. 10
 b. What are the effects of negative feedback? 4
 c. Determine the voltage gain, input and output impedance with feedback for voltage series feedback having $A = -100$, $R_i = 10\text{ k}\Omega$, $R_o = 20\text{ k}\Omega$ for feedback of
 (i) $\beta = -0.1$ (ii) $\beta = -0.5$ 6

Unit - IV

- 7 a. With a neat sketch explain the classification of power amplifier based on the location of Q – point? 10
 b. Derive an equation for second harmonic distortion in terms of current. 10
 8 a. Explain the working of a transformer coupled class A amplifier and prove that the maximum efficiency for the same is 50%. 10
 b. Calculate the efficiency of a transformer coupled class A amplifier for a supply of 12 V and output of 12 V. 4
 c. For a class B amplifier providing a 20V peak signal to a 16Ω loud speaker and a power supply of $V_{CC} = 30V$, determine the input power, output power and – circuit efficiency. 6

Unit - V

- 9 a. Explain how a feedback circuit can be used as an oscillator. 6
 b. Calculate operating frequency of a BJT phase – shift oscillator for $R = 6\text{ k}\Omega$, $C = 1500\text{ pF}$, $R_c = 18\text{ k}\Omega$. 4

- c. Explain the characteristics of a quartz crystal with a neat diagram explain the crystal oscillator in parallel – resonant circuits. 10
- 10 a. With the help of transfer characteristics explain how trans conductance of a FET can be obtained using graphical method. 6
- b. Design the FET fixed bias circuit for the following specification given $A_v = 10$, $I_{DSS} = 10 \text{ mA}$, $V_P = -4\text{V}$, $y_{OS} = 20 \mu\text{s}$, $V_{DD} = 30 \text{ V}$, $C_1 = 0.1 \mu\text{F}$, $R_G = 10 \text{ M}\Omega$. 8
- c. Write the circuit symbol and small signal ac model of n – channel D – MOSFET and explain. 6

* * * * *