



U.S.N

--	--	--	--	--	--	--	--	--	--

**P.E.S. College of Engineering, Mandya - 571 401**

*(An Autonomous Institution affiliated to VTU, Belgaum)*

**Third Semester, B.E. – Electronics and Communications Engineering**

**Semester End Examination, Dec-2014**

**FET and Op – Amp Circuits**

Time: 3 hrs

Max. Marks: 100

**Note :** i) Answer **FIVE** full questions, selecting **ONE** full question from each Unit.  
 ii) Assume suitably missing data if any.

**Unit - I**

- 1 a. With a neat sketch explain current – voltage characteristics of an n – channel enhancement type MOSFET. Also write the large signal equivalent circuit model of an n – channel enhancement MOSFET operating in the saturation region. 9
- b. Explain how MOSFET is used as a switch. 5
- c. Design a circuit of Fig. 1(c) so that the transistor operates at  $I_D = 0.4 \text{ mA}$  and  $V_D = 0.5 \text{ V}$ . The NMOS transistor has  $V_t = 0.7$ ,  $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $L = 1 \mu\text{m}$  and  $\omega = 32 \mu\text{m}$ ,  $V_{DD} = 2.5 \text{ V}$  and  $V_{SS} = -2.5 \text{ V}$ . Neglect the channel length modulation effect.

 


Fig 1(c)

- 2 a. Explain the purpose of biasing. Discuss biasing using constant current source. 10
- b. Discuss high frequency response of the common source amplifier. 10

**Unit - II**

- 3a. Define the following terms with respect to Op-Amp. 8
  - (i) CMRR      (ii) PSRR      (iii) Input offset voltage      (iv) Output impedance.
- b. Sketch an illustration to show the effect of op-amp slow rate and explain. State a typical op – amp slow rate. 6

- c. Design a non – inverting amplifier of voltage gain  $A_V = 66$  and  $V_{in} = 15$  mV using 741 op – amp. 6
- 4 a. Draw a circuit for a differential input / output amplifier. Explain the circuit operator and derive an equation for voltage gain. 10
- b. Briefly explain a high input impedance capacitor coupled voltage follower. 10

### Unit - III

- 5 a. Explain the capacitor – coupled difference amplifier with relevant circuit diagram. 6
- b. With a neat circuit diagram explain phase – lag compensation technique of frequency compensation. 8
- c. What are the effects of slew rate on  
(i) Bandwidth (ii) Output amplitude (iii) Output pulse rise time. 6
- 6 a. What precautions should be observed for Op – amp circuit stability? Draw the necessary diagram. 8
- b. Design a voltage source with Zener diode as a reference voltage to provide an output of 9 V to a  $500 \Omega$  load. The available supply is  $\pm 12V$ . Take  $V_z = 4.5$  V and  $I_z = 20$  mA 7
- c. With circuit diagram explain the working of current amplifier. 5

### Unit - IV

- 7 a. Design an inverting Schmitt trigger circuit for the following specification  $V_{cc} = \pm 12$  V trigger point =  $\pm 2$  V. 8
- b. With a neat circuit diagram explain the circuit operation of Integrating circuit. 6
- c. What is limiting circuits? Explain. 6
- 8 a. Design a precision full – wave – rectifier to provide 2 V peak output from a sine – wave input with a peak value of 0.5 V and frequency of 1 MHz. 10
- b. With a neat sketch explain the working operation of sample and hold circuits. 10

### Unit - V

- 9 a. With a net circuit diagram and waveform explain operation of triangular / rectangular waveform generator with frequency and duty cycle. 10
- b. Design a second – order high – pass filter to have a cut–off frequency of 12 kHz. 10
- 10 a. Define and explain the following terms as applied to voltage regulator. 6
- i) Line regulation ii) Load regulation iii) Ripple rejection.
- b. Explain voltage follower regulator with relevant circuit diagram. 8
- c. List and briefly explain the characteristics of three terminal IC regulators with standard representation of the same. 6