



U.S.N

--	--	--	--	--	--	--	--	--	--

## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

**Third Semester, B.E. – Electronics and Communications Engineering**

**Semester End Examination; Dec. – 2014**

### Digital Circuit Design

Time: 3 hrs

Max. Marks: 100

**Note :** i) Answer **FIVE** full questions, selecting **ONE** full question from each Unit.

ii) Assume suitable missing data if any..

#### Unit - I

- 1 a. With the help of circuit diagram explain the operation of 8
- i) 2 input CMOS NAND gate                      ii) 2 input CMOS NOR gate.
- b. Explain with diagram the operation of 2 input TTL NAND gate. 7
- c. Explain the following terms with respect to gates. 5
- i) Output switching time    ii) Fan-out and Fan-in.
- 2 a. Explain with the help of circuit diagram the operation of 8
- (i) 2 input NMOS NAND gate                      ii) 2 input PMOS NOR gate.
- b. Explain the construction and operation of; 12
- i) NMOS enhancement – mode FET    ii) PMOS enhancement mode FET

#### Unit – II

- 3a. Design a combinational logic circuit with 4 inputs a, b, c, d and one output f, which goes high whenever LSB of input or MSB of input is high. Implement using two level basic gates structure. 7
- b. Write the Boolean expression for the schematic shown in fig. 1. 5
- c. Obtain minimal SOP and minimal POS expression for the function 8
- $$f(a, b, c, d) = \overline{a}b\overline{d} + bcd + a\overline{b}d + \overline{b}c\overline{d} \text{ using K-map.}$$
- 4 a. Find all the prime implicants for the following function using Quine – Mccluskey method. 12
- $$f(a, b, c, d) = \pi M(0, 2, 3, 4, 5, 12, 13) + \pi d(8, 10)$$
- b. For the function  $f(a, b, c, d) = \sum m(3, 4, 5, 7, 8, 11, 12, 13, 15)$  obtain minimal product and minimal sum using MEV method. 8

#### Unit - III

- 5 a. Explain the working of look ahead carry adder derive the equation for sum and carry. 10
- b. Design and implement using basic gates 2 bit magnitude comparator. 10

Contd...2

- 6 a. Implement full adder and full subtractor using multiplexer. 10
- b. Implement the following functions using a single 3 to 8 line decodes and external gates.

$$f_1(a,b,c) = \pi M(2,3,4,5,7)$$

10

$$f_2(a,b,c) = \pi M(0,2,4,6,7)$$

**Unit - IV**

- 7 a. Explain how S-R latch can be used as key denouncer. 6
- b. Obtain the characteristics equation for SR, JK, D and T flip flop using K – map. 8
- c. Draw the circuit of basic bistable element and explain its operation. 6
- 8 a. With the help of neat diagram explain the working of master slave SR FF. 8
- b. What is edge triggering? Explain the working of +ve edge triggered D – FF 6
- c. Draw the output waveform for a gated SR Latch, if S, R and clock inputs are as shown in Fig. 2. 6


**Unit - V**

- 9 a. Design a 4 – bit register using +ve edge triggered D – FF to operate as per the following table.

Mode select		Register operation
S <sub>1</sub>	S <sub>0</sub>	
0	0	Hold
0	1	Clear
1	0	Complement the content
1	1	Circular shift register

8

- b. Design a mod – 77 synchronous counter by cascading two 4 bit binary counter. 8
- c. Construct a 4 bit ring counter using a universal shift register. 4
- 10 a. Design a synchronous mod – 6 counter using clocked JK – FF. 10
- b. Construct the excitation table, Transition table, State table and State diagram for the Moore sequential circuit shown in Fig. 3. 10

 

 


fig 2

 


fig 3

\*\*\*\*\*