



U.S.N 

--	--	--	--	--	--	--	--	--	--

**P.E.S. College of Engineering, Mandya - 571 401**

(An Autonomous Institution affiliated to VTU, Belgaum)

**Third Semester, B.E. - Electronics and Communication Engineering**

**Semester End Examination; Dec. - 2015**

**Electric Circuit Theory**

Time: 3 hrs

Max. Marks: 100

Note: i) Answer **FIVE** full questions, selecting **ONE** full question from each unit.  
ii) Justify any Assumptions made.

**UNIT - I**

1 a. Define the following :


- i) Branch of a network
- ii) Potential Source
- iii) Current Source
- iv) Network and circuit.

5

b. Explain with figures the four types of dependent sources.

8

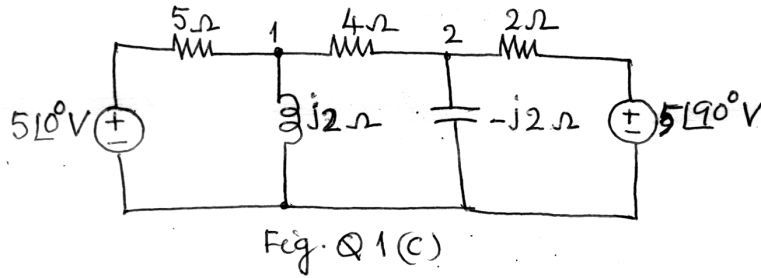c. For the network shown in Fig .Q1(c), use nodal analysis to determine the node voltages.




7

2 a. For a network, develop the generalized mesh equation in the matrix form  $[Z][I]=[V]$  where  $[Z]$  = impedance matrix,  $[I]$  = mesh current matrix and  $[V]$  = source voltage matrix.


7

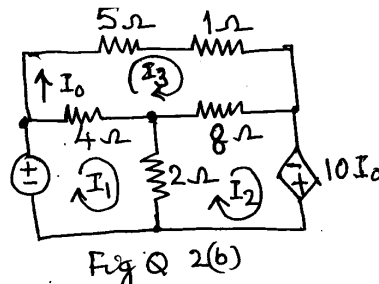b. Using mesh analysis, find the current  $I_0$  and the power dissipated in the  $5 \Omega$  resistor in the current of Fig. Q 2(b).



7

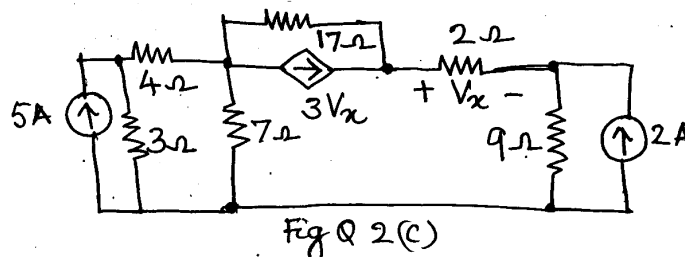c. Calculate the current through  $2 \Omega$  resistor in the circuit of Fig. Q2(c) using source information.



6


**UNIT - II**

3 a. Define the following with an example each :

- (i) Oriented graph
- (ii) Tree
- (iii) Incidence matrix
- (iv) Fundamental cut-set
- (v) fundamental tie-set

b. For the network shown in Fig. Q 3(b) draw its dual. Write in the integrodifferential form,

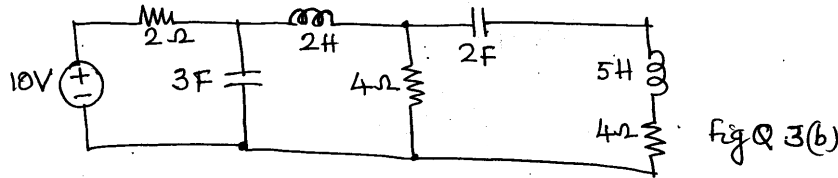
- (i) Mesh equations for the given network
- ii) Node equations for the dual.



4 a. Distinguish between the following terms as applied to network topology. Give suitable examples: (i) Planar graph and non-planar graph (ii) Links and twigs.

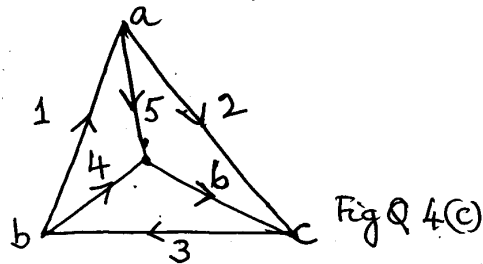b. The reduced incidence matrix of a network is given below. Draw the oriented graph corresponding to it.

$$\begin{bmatrix} -1 & +1 & 0 & 0 & 0 & -1 \\ 0 & -1 & -1 & +1 & 0 & 0 \\ 0 & 0 & +1 & 0 & -1 & +1 \end{bmatrix}$$




c. For the oriented graph shown in Fig. Q4 (c) write the complete incidence matrix. Also write the cut-set and tieset matrices considering branches 4, 5 and 6 as twigs.


**UNIT - III**

5 a. State and explain Reciprocity theorem.

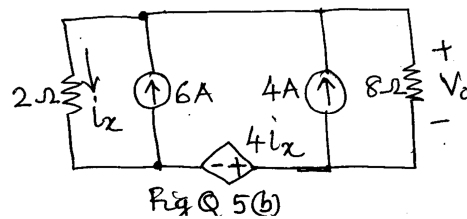
b. Use superposition theorem to find  $V_o$  in the circuit of Fig. Q 5(b).



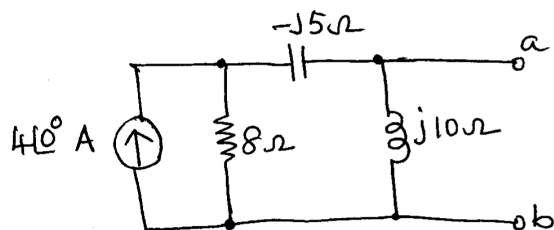c. Find the Thevenin equivalent circuit at terminals a-b in the circuit shown in Fig. Q5(c). What is the impedance  $Z_L$  to be connected across a-b so that maximum power is delivered to  $Z_L$ ? What is that maximum power?




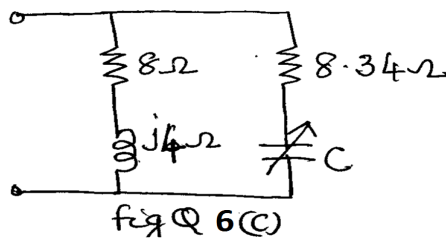6. a. For a series resonant circuit show that  $\omega_0 = \sqrt{\omega_1\omega_2}$  where  $\omega_0$  = resonant frequency and  $\omega_1, \omega_2$  = half power frequencies. 6
- b. A coil under test is connected in series with a variable capacitor C and a sine wave generator giving a 10 V rms output at a frequency of 1k rad/s. By adjusting C, the current is found to be maximum when  $C = 10 \mu\text{F}$ . Further the current falls down to 0.707 times the maximum value when  $C = 12.5 \mu\text{F}$ ; 7
- i) Find the inductance and resistance of the coil      ii) Find the Q of the coil at resonance
- iii) What is the maximum current in the circuit?
- c. In the network shown in Fig. Q6(c), find the values of C for which the circuit resonates at  $\omega = 5000 \text{ rads/s}$ .



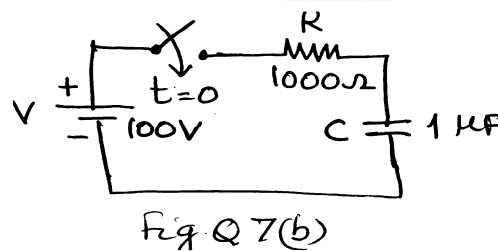**UNIT - IV**


- 7 a. Write the equivalent form of the elements in terms of, 8
- (i) The initial conditions of the elements      (ii) the final conditions of the elements.
- b. In the network shown in Fig. 7(b) the switch is closed at  $t = 0$  with the capacitor uncharged find the values of  $i$  and  $\frac{di}{dt}$  at  $t = 0+$ .



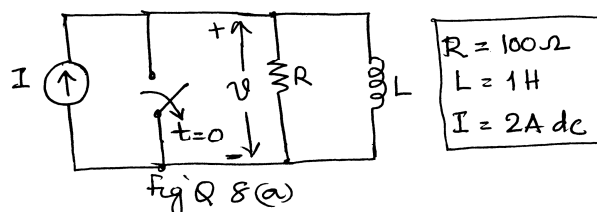- c. State convolution theorem as applied to Laplace transforms. Use convolution theorem to find the Laplace inverse of the function, 8

$$F(s) = \frac{s}{(s+1)(s+2)}$$


- 8 a. Determine  $v, \frac{dv}{dt}$  and  $\frac{d^2v}{dt^2}$  at  $t = 0+$  when the switch k is opened at  $t = 0$  in the circuit of Fig. Q 8(a).



b. What are the advantages of Laplace transform method over classical method for solving differential equation. 3

c. Show that  $L\left\{\frac{df(t)}{dt}\right\} = sf(s) - f(0^-)$  where  $F(s) = L\{f(t)\}$  and  $f(0^-) = \lim_{t \rightarrow 0} f(t)$ . 3

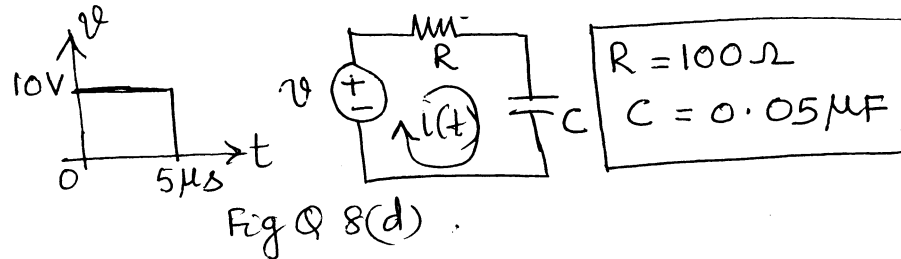
d. A pulse of 10 V magnitude and 5 μs duration is applied to the RC circuit as shown in Fig. Q 8(d). Find the current  $i(t)$  using Laplace transform method. Fig.




**UNIT - V**

9 a. What are poles and zeros of a network functions? List the restrictions on pole and zero locations for transfer functions. 10

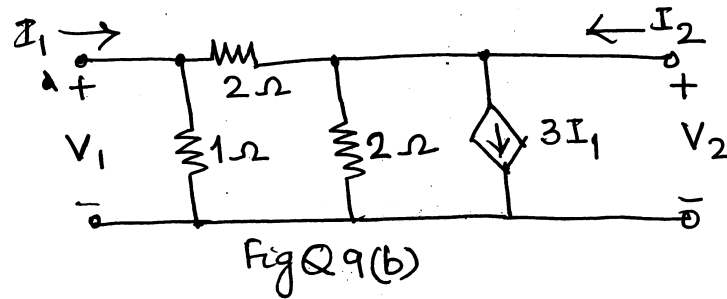b. Determine the y-parameters for the two-port network shown in Fig. Q 9(b) and draw the y-parameter equivalent circuit.



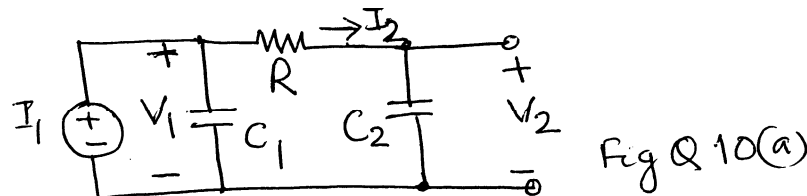10a. For the network shown in Fig. 10(a) compute  $\alpha_{12}(s) = \frac{I_2(s)}{I_1(s)}$  and  $Z_{12}(s) = \frac{V_2(s)}{I_1(s)}$ . Also locate the poles and zeroes of  $\alpha_{12}(s)$  and  $Z_{12}(s)$  on the s-plane. Assume  $R = 1 \Omega$ ,  $C_1 = 1 \text{ F}$  and  $C_2 = 2 \text{ F}$ . 10



b. Explain the symmetry and reciprocity properties of two port networks. 4

c. Show that the overall transmission parameter matrix for the cascaded connection of two two-port networks is the matrix product of the transmission parameter matrices of the individual two-port networks in the cascade. 6