



--	--	--	--	--	--	--	--	--	--

## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Third Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; Dec. - 2015

FET and Op-Amp Circuits

Time: 3 hrs

Max. Marks: 100

**Note:** Answer any FIVE full questions, selecting ONE full question from each unit.

### UNIT - I

- 1 a. Derive  $i_D$ - $V_{DS}$  relationship of the NMOS transistor with suitable figure. 10
- b. For a 0.8  $\mu\text{m}$  process technology for which  $t_{ox} = 15$  nm and  $\mu_n = 550$   $\text{cm}^2/\text{V-s}$ , find  $C_{OX}$   $K'_n$  and the overdrive voltage required to operate a transistor having  $W/L = 20$  in saturation with  $I_D = 0.2$  mA. 6
- c. Explain the operation of MOSFET as a switch. 4
- 2 a. Explain the operation of MOSFET common source amplifier circuit and derive expressions for its input resistance, voltage gain and output resistance. 10
- b. Find the mid band gain and upper 3-dB frequency of a MOSFET common source amplifier fed with a signal source having an internal resistance  $R_{sig} = 100$   $\Omega$ . The amplifier has  $R_G = 4.7$   $\text{M}\Omega$ ,  $R_D = R_L = 15$   $\text{k}\Omega$ ,  $g_m = 1$   $\text{mA/V}$ ,  $r_0 = 150$   $\text{k}\Omega$ ,  $C_{gs} = 1$   $\text{pF}$  and  $C_{gd} = 0.4$   $\text{pF}$ . 6
- c. Briefly discuss depletion type MOSFET. 4

### UNIT - II

- 3 a. Explain the following : 12
  - i) Input Offset voltage      ii) Input offset current
  - iii) Offset Nulling      iv) Slew rate and frequency limitation.
- b. Design an inverting amplifier using 741 Op-Amp to obtain a voltage gain of 50 and the output voltage amplitude of 2.5 V. 8
- 4 a. Illustrate how the input impedance of a high  $Z_{in}$  capacitor coupled voltage follower can be increased? 6
- b. Sketch and explain the circuit of a capacitor coupled non inverting amplifier. 6
- c. Using a 741 Op-Amp, design a high input impedance non-inverting amplifier to operate with a single polarity power supply of + 36 V and a load resistance 12  $\text{k}\Omega$ , to achieve a voltage gain of 7 at lower cutoff frequency of 150 Hz. 8

### UNIT - III

- 5 a. Explain the operation of capacitor coupled inverting amplifier and also the procedure to set the upper cutoff frequency in such circuit. 8

- b. In a capacitor-coupled inverting amplifier having a signal frequency range of 10 Hz to 1 kHz, if the values of  $R_1$ ,  $R_2$  and  $R_L$  are 1 k $\Omega$ , 47 k $\Omega$  and 250  $\Omega$  respectively, calculate the required capacitor values. 6
- c. Explain the capacitor-coupled voltage follower using a single-polarity supply. 6
6. a. With suitable diagrams, explain various frequency compensating methods. 12
- b. Explain the current amplifier. 5
- c. Calculate the slew rate limited cutoff frequency for a voltage follower circuit using a 741 Op-Amp if the peak of Sine wave output is to be 5 V. 3

#### UNIT - IV

- 7 a. Sketch the output waveforms produced by an Op-Amp differentiating circuit with triangular and rectangular inputs. Explain each output wave shape. Discuss the distortion that occurs and how it can be minimized. 10
- b. Explain the precision full-wave rectifier. 10
- 8 a. Explain the operation of inverting Schmitt trigger circuit and its input/output characteristics. 10
- b. Explain the operation of Op-amp monostable multivibrator and discuss its design procedure. 10

#### UNIT - V

- 9 a. Draw the II order high pass filter circuit and its input and output waveforms. Explain its operation. 10
- b. What is Barkhausen Criteria? Explain Wein bridge oscillator. 10
- 10 a. Discuss the operation and performance of Adjustable output regulator. 10
- b. Explain the operation, the design procedure and performance of voltage follower regulator circuit. 10

\* \* \* \*