



U.S.N

--	--	--	--	--	--	--	--	--	--

P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Third Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; Dec. - 2015

Electrical Network Analysis

Time: 3 hrs

Max. Marks: 100

Note: i) Answer **FIVE** full questions, selecting **ONE** full question from each unit.
ii) Justify any Assumptions made.

UNIT - I

1 a. Define the following :


- i) Branch of a network
- ii) Potential Source
- iii) Current Source
- iv) Network and circuit.

5

b. Explain with figures the four types of dependent sources.

8

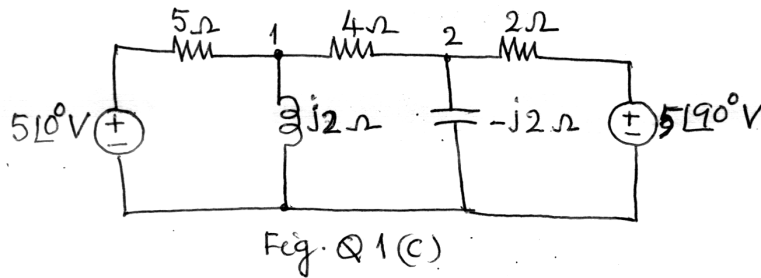c. For the network shown in Fig .Q1(c), use nodal analysis to determine the node voltages.




7

2 a. For a network, develop the generalized mesh equation in the matrix form $[Z][I]=[V]$ where $[Z]$ = impedance matrix, $[I]$ = mesh current matrix and $[V]$ = source voltage matrix.


7

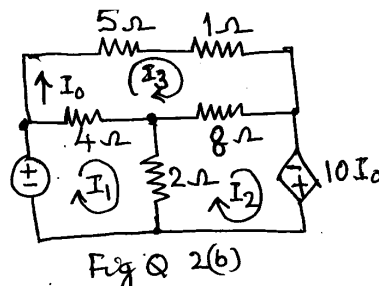b. Using mesh analysis, find the current I_0 and the power dissipated in the 5Ω resistor in the current of Fig. Q 2(b).



7

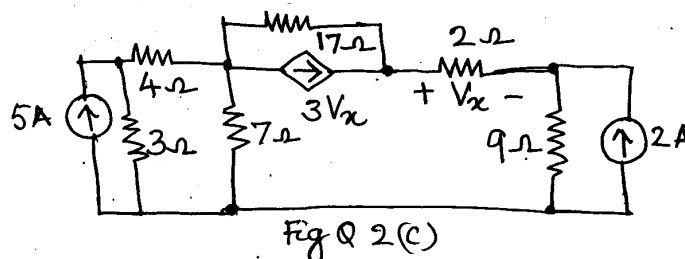c. Calculate the current through 2Ω resistor in the circuit of Fig. Q2(c) using source information.



6


UNIT - II

3 a. Define the following with an example each :

- (i) Oriented graph
- (ii) Tree
- (iii) Incidence matrix
- (iv) Fundamental cut-set
- (v) fundamental tie-set

b. For the network shown in Fig. Q 3(b) draw its dual. Write in the integrodifferential form,

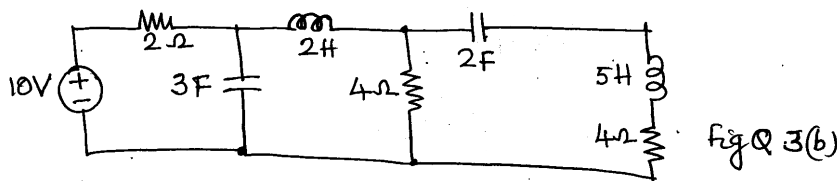
- (i) Mesh equations for the given network
- ii) Node equations for the dual.



4 a. Distinguish between the following terms as applied to network topology. Give suitable examples: (i) Planar graph and non-planar graph (ii) Links and twigs.

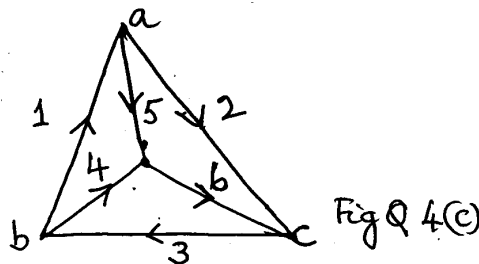b. The reduced incidence matrix of a network is given below. Draw the oriented graph corresponding to it.

$$\begin{bmatrix} -1 & +1 & 0 & 0 & 0 & -1 \\ 0 & -1 & -1 & +1 & 0 & 0 \\ 0 & 0 & +1 & 0 & -1 & +1 \end{bmatrix}$$




c. For the oriented graph shown in Fig. Q4 (c) write the complete incidence matrix. Also write the cut-set and tieset matrices considering branches 4, 5 and 6 as twigs.

UNIT - III

5 a. State and explain Reciprocity theorem.

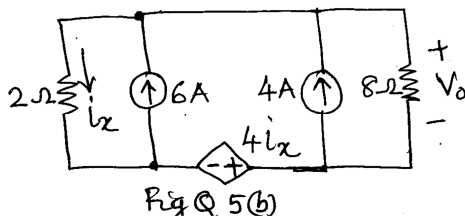b. Use superposition theorem to find V_o in the circuit of Fig. Q 5(b).



c. Find the Thevenin equivalent circuit at terminals a-b in the circuit shown in Fig. Q5(c). What is the impedance Z_L to be connected across a-b so that maximum power is delivered to Z_L ? What is that maximum power?


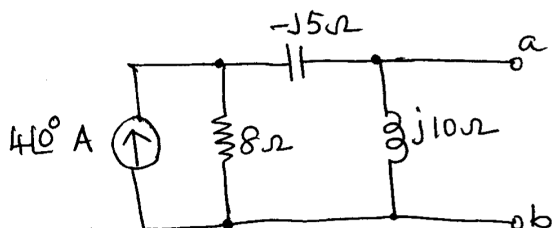



Fig. Q 5(C)

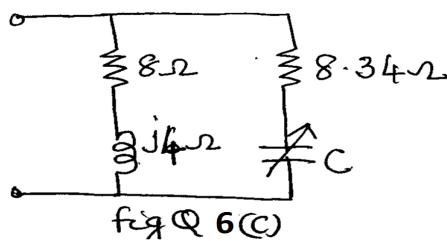6. a. For a series resonant circuit show that $\omega_0 = \sqrt{\omega_1\omega_2}$ where ω_0 = resonant frequency and ω_1, ω_2 = half power frequencies.
- b. A coil under test is connected in series with a variable capacitor C and a sine wave generator giving a 10 V rms output at a frequency of 1k rad/s. By adjusting C, the current is found to be maximum when $C = 10 \mu\text{F}$. Further the current falls down to 0.707 times the maximum value when $C = 12.5 \mu\text{F}$;
- i) Find the inductance and resistance of the coil ii) Find the Q of the coil at resonance
- iii) What is the maximum current in the circuit?
- c. In the network shown in Fig. Q6(c), find the values of C for which the circuit resonates at $\omega = 5000 \text{ rads/s}$.



UNIT - IV

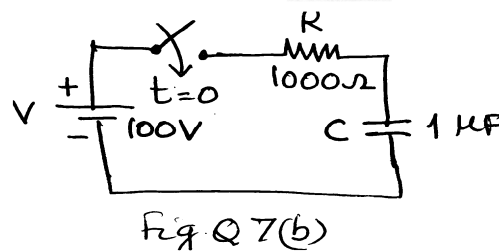
- 7 a. Write the equivalent form of the elements in terms of,
- (i) The initial conditions of the elements (ii) the final conditions of the elements.
- b. In the network shown in Fig. 7(b) the switch is closed at $t = 0$ with the capacitor uncharged find the values of i and $\frac{di}{dt}$ at $t = 0+$.



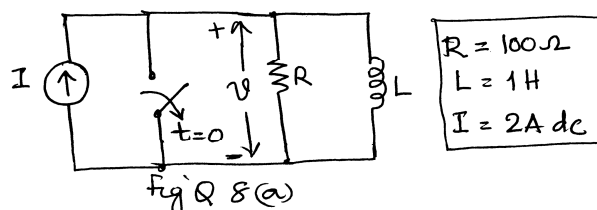- c. State convolution theorem as applied to Laplace transforms. Use convolution theorem to find the Laplace inverse of the function,

$$F(s) = \frac{s}{(s+1)(s+2)}$$


- 8 a. Determine $v, \frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t = 0+$ when the switch k is opened at $t = 0$ in the circuit of Fig. Q 8(a).



b. What are the advantages of Laplace transform method over classical method for solving differential equation. 3

c. Show that $L\left\{\frac{df(t)}{dt}\right\} = sf(s) - f(0^-)$ where $F(s) = L\{f(t)\}$ and $f(0^-) = \lim_{t \rightarrow 0^-} f(t)$. 3

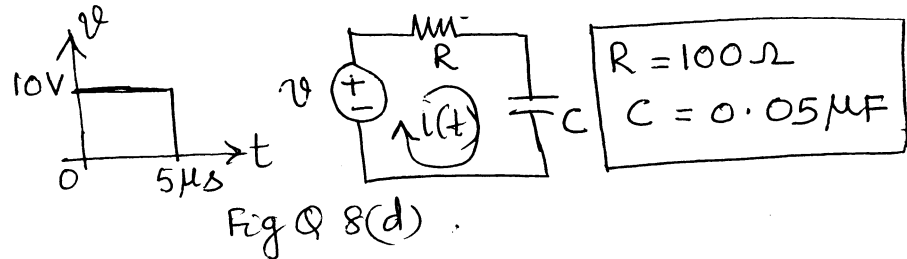
d. A pulse of 10 V magnitude and 5 μs duration is applied to the RC circuit as shown in Fig. Q 8(d). Find the current $i(t)$ using Laplace transform method. Fig.




UNIT - V

9 a. What are poles and zeros of a network functions? List the restrictions on pole and zero locations for transfer functions. 10

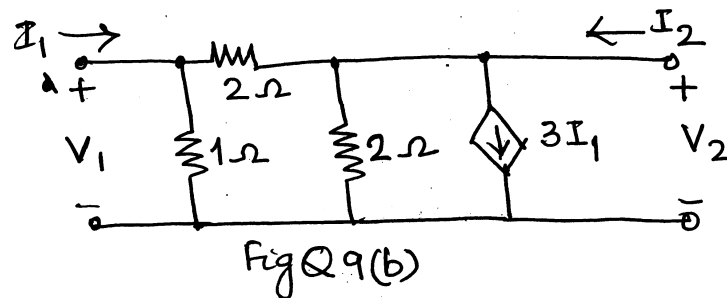b. Determine the y-parameters for the two-port network shown in Fig. Q 9(b) and draw the y-parameter equivalent circuit.



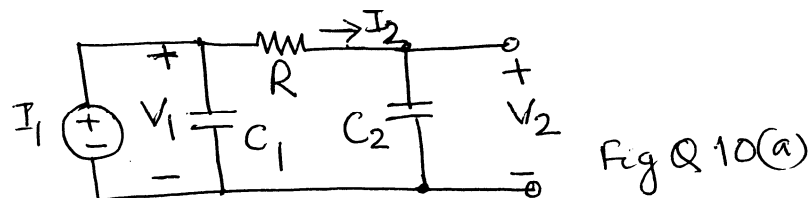10a. For the network shown in Fig. 10(a) compute $\alpha_{12}(s) = \frac{I_2(s)}{I_1(s)}$ and $Z_{12}(s) = \frac{V_2(s)}{I_1(s)}$. Also locate the poles and zeroes of $\alpha_{12}(s)$ and $Z_{12}(s)$ on the s-plane Assume $R = 1 \Omega$, $C_1 = 1 \text{ F}$ and $C_2 = 2 \text{ F}$. 10



b. Explain the symmetry and reciprocity properties of two port networks. 4

c. Show that the overall transmission parameter matrix for the cascaded connection of two two-port networks is the matrix product of the transmission parameter matrices of the individual two-port networks in the cascade. 6