



P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belgaum)
Third Semester, B.E. – Electronics and Communication Engineering
Make-up Examination; Jan / Feb - 2017
Network Analysis and Synthesis


Time: 3 hrs

Max. Marks: 100


Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

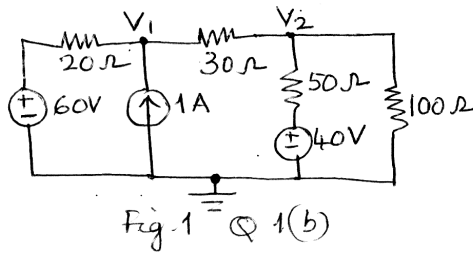
- 1 a. State and prove maximum power transfer theorem as applied to DC circuits. 7
- b. Use nodal analysis in the circuit of Fig.1 to found the current through 30 Ω resistor. 7



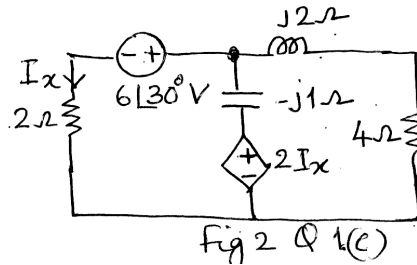
- c. Find the voltage across the 4 Ω resistor using mesh analysis in the network of Fig. 2. 6



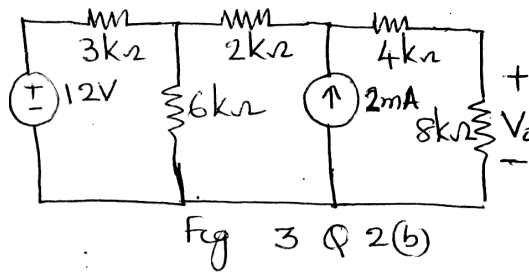- 2 a. State and explain Norton's theorem as applied to AC circuits. 7
- b. Use repeated application of source transformation to find V₀ in the circuit of Fig. 3. 6




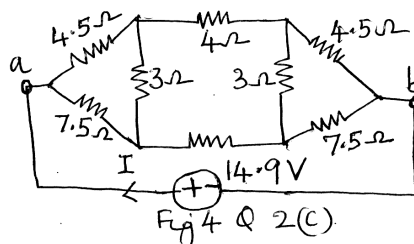- c. By using star-delta transformation technique, find the equivalent resistance R_{ab} and current I in the circuit shown in Fig. 4. 7



UNIT - II


- 3 a. For a series resonant circuit, obtain the expressions for ω_1 and ω_2 in terms of components values R, L and C also show that $\omega_0 = \sqrt{\omega_1 \omega_2}$. 7
- b. A series RLC circuit has $R = 10 \Omega$, $L = 0.01 \text{ H}$ and $C = 100 \mu\text{F}$, compute the resonant frequency, bandwidth, quality factor and half-power frequencies. 6
- c. Define resonance in electric circuits. Compute the numerical values of ω_0 , α , ω_d and R for a parallel resonant circuit having $L = 2.5 \text{ mH}$, $Q_0 = 5$ and $C = 0.01 \mu\text{F}$. 7
- 4 a. What do you mean by initial conditions in electric networks? Show mathematically that the voltage across a capacitor cannot change instantaneously. 7
- b. Determine the transient response of a series RL circuit under DC excitation. 7
- c. In the network shown in Fig. 5 the switch is changed from position 1 to position 2 at $t = 0$, steady state having reached before switching. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t = 0^+$. 7

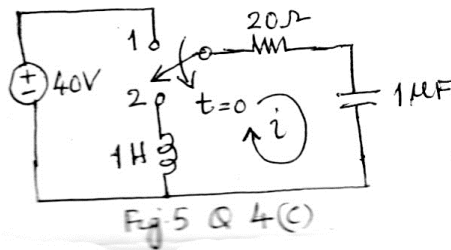

6


UNIT - III

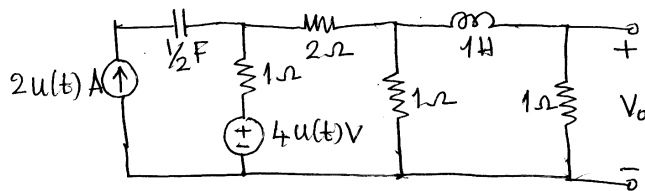- 5 a. Find the inverse Laplace transform of $V_s = \frac{2}{s^3 + 12s^2 + 36s}$. 6
- b. State and prove convolution theorem as applied to Laplace transform. 7
- c. For the network shown in Fig. 7 find $V_o(t)$ for $t > 0$ using mesh analysis in the s -domain circuit. 7




7

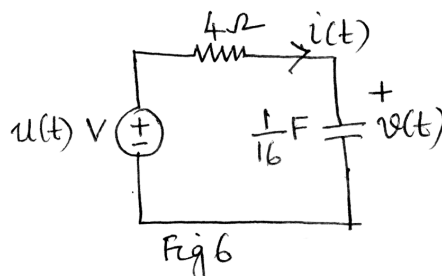- 6 a. Determine $V(t)$ for $t > 0$ in the series RC circuit shown in Fig. 6. 7



7

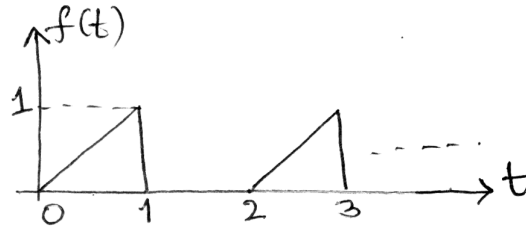b. Find the Laplace transform of the waveform shown below.



7

c. Develop the models for an inductor and a capacitor in the s -domain.

6

UNIT - IV

7 a. Find the input impedance of the network shown in Fig. 8

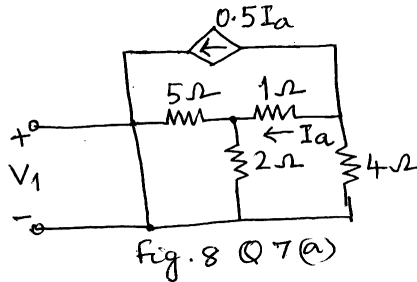


Fig. 8 Q 7(a)

7

b. Find the y -parameters for the network shown in Fig. 9.

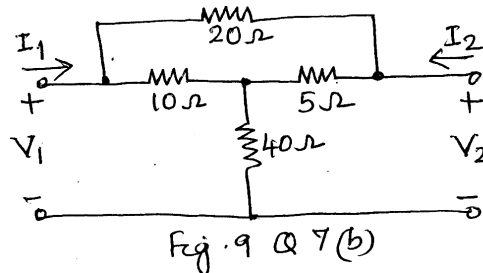


Fig. 9 Q 7(b)

7

c. Define h -parameters for a two-port network. Explain them in terms of Z -parameters.

6

8 a. Define the following with examples :

6

- i) Planar graph
- ii) Sub-graph
- iii) Tree.

b. For the circuit shown in Fig. 10, draw the oriented graph and write,

- i) The incidence matrix
- ii) Tie set matrix
- iii) f -cutset matrix.

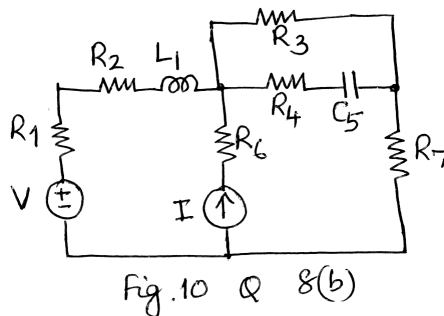


Fig.10 Q 8(b)

8

c. Draw the dual of the network shown in Fig. 11.

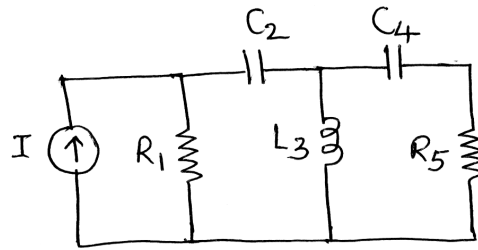


Fig. 11 Q 8 (C)

6

UNIT - V

9 a. List the properties of Hurwitz polynomials.

6

b. Test whether $f(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$ is a positive real function.

6

c. Test whether the polynomial, $P(s) = s^4 + s^3 + 3s^2 + 2s + 12$ is Hurwitz.

8

10 a. Realize the Cauer forms of the LC-impedance function, $Z(s) = \frac{10s^4 + 12s^2 + 1}{2s^2 + 2s}$.

6

b. List the properties of positive real functions.

7

c. Realize Foster I form realization of the RC-impedance function :

$$Z(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$$

7

* * *