



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Third Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; Dec - 2016/Jan - 2017

Network Analysis and Synthesis

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

1 a. Determine the value of the voltage labeled V_1 shown in Figure-1a.

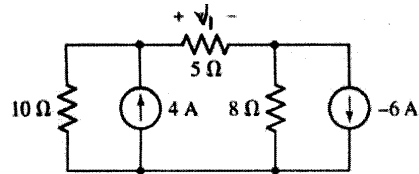


Figure-1a

6

b. For the circuit of Figure-1b, use nodal analysis to determine V_1 and V_2 .

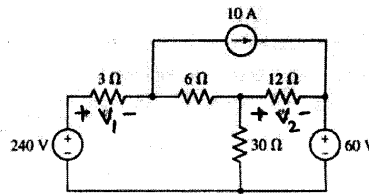


Figure-1b

7

c. Employ mesh analysis to determine the current flowing in the circuit of Figure-1c through the 2 ohm resistor.

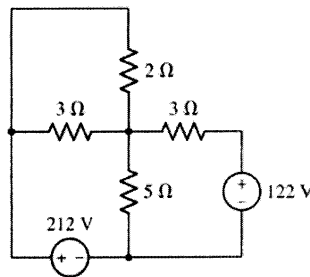


Figure-1c

7

2 a. Using source transformation, determine the power dissipated by the 5.8 k ohm resistor in Figure-2a.

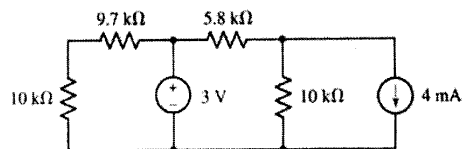


Figure-2a

6

- b. Find the frequency domain Thevenin equivalent of the network shown in Figure-2b. Show the result as V_{th} in series with Z_{th} .

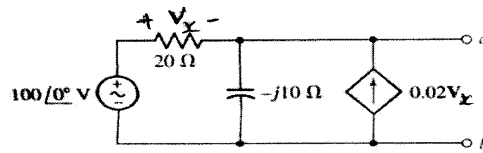


Figure-2b

7

- c. Find the average power absorbed by the 10 Ω resistor shown in Figure-2c.

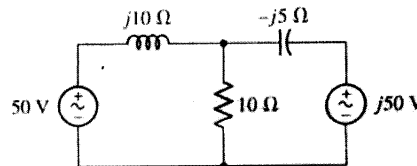


Figure-2c

7

UNIT - II

- 3 a. Define quality factor and prove that for a parallel RLC circuit quality factor $Q_0 = \omega_0 RC$. 6
 b. A parallel resonant circuit has $\omega_0 = 1000 \text{ rad/s}$, $Q_0 = 80$, and $C = 0.2 \mu\text{F}$. Find R and L . 7
 c. A series resonant network consists of a 50 Ω resistor, a 4 mH inductor, and a 0.1 μF capacitor. Calculate values for, (i) ω_0 (ii) f_0 (iii) Q_0 and (iv) Bandwidth B. 7
- 4 a. In the network shown in Figure-4a, the switch is changed from the position 1 to the position 2 at $t = 0$. Steady state condition having reached before switching. Find the values of i , di/dt and d^2i/dt^2 at $t = 0^+$.

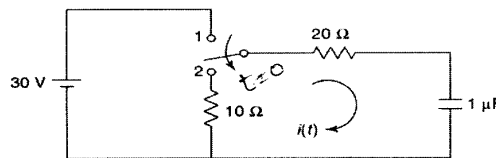


Figure-4a

10

- b. For the network shown in Figure-4b, the switch is open for a long time and closes at $t = 0$. Determine $V_C(t)$.

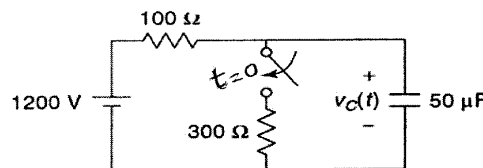


Figure-4b

10

UNIT - III

- 5 a. State and prove : 6
 (i) Initial value theorem (ii) Final value theorem as applied to Laplace transform.
 b. Find the Laplace transform of the following : 6
 i) $3u(t - 3) - 3$ (ii) $3u(3 - t)$.

- c. Referring to the RL circuit of Figure-5c, (i) Write a differential equation for the inductor current $i_L(t)$, (ii) Find $I_L(s)$ the Laplace transform $i_L(t)$, (iii) Solve for $i_L(t)$ by taking the inverse Laplace transform of $I_L(s)$.

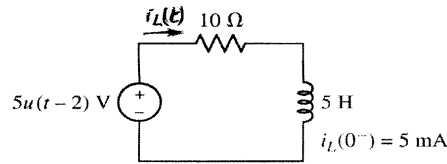


Figure-5c

8

- 6 a. Find the Thevenin equivalent impedance seen looking into the terminals of the circuit depicted in Figure-6a. Do the analysis in S-domain only.

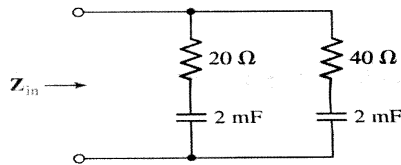


Figure-6a

7

- b. Prove that the inverse Laplace transform of the product of two Laplace transforms is the convolution of the individual Laplace transforms.
 c. State all poles and zeros of each of the following s-domain functions :

i) $\frac{3s^2}{s(s^2 + 4)(s-1)}$

ii) $\frac{s^2 + 2s - 1}{s^2(4s^2 + 2s + 1)(s^2 - 1)}$

7

6

UNIT - IV

- 7 a. Find y_{11} and y_{12} for the two-port shown in Figure-7a.

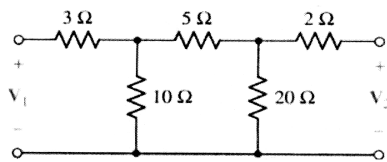


Figure-7a

6

- b. Convert the Δ network of Figure-7b to a Y connected network.

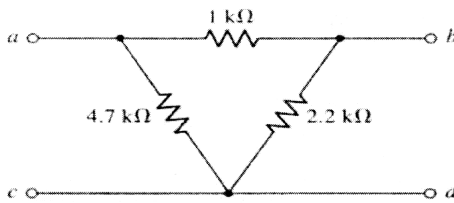


Figure-7b

7

- c. Find t_A for the single 2Ω resistor of Figure-7c. Show that t for a single 10Ω resistor can be obtained by $(t_A)^5$.

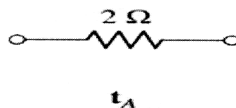


Figure-7c

7

- 8 a. Compare the following terms as applied to network topology with suitable examples : 6
 (i) Planar graph and non planar graph (ii) Links and twigs.
 b. For the circuit shown in Figure-8b,
 (i) Draw its graph (ii) Draw its tree (iii) Write the fundamental cutset matrix.

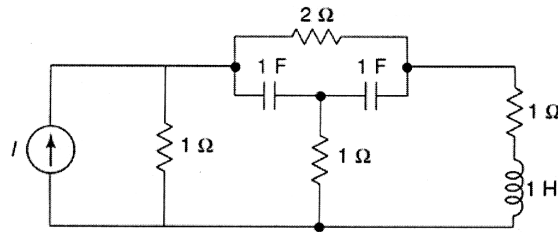


Figure-8b

- c. The reduced incidence matrix of a graph is given in Figure-8C. Express branch voltages in terms of node voltages. 7

$$Q = \begin{bmatrix} -1 & 1 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 & -1 \\ 1 & 0 & 0 & 1 & 0 \end{bmatrix}$$

Figure-8c

UNIT - V

- 9 a. Test whether the following polynomial is Hurwitz, 7
 $P(s) = s^4 + s^3 + 5s^2 + 3s + 4.$
 b. Test whether the function given is a positive real function $f(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}.$ 7
 c. Justify which of the function is RL or RC impedance functions : 6
 i) $z(s) = \frac{4(s+1)(s+3)}{s(s+2)}$ ii) $z(s) = \frac{s(s+4)(s+8)}{(s+1)(s+6)}$.

- 10 a. Realize Cauer-II form of the function : 7

$$z_{LC}(s) = \frac{s(s^4 + 3s^2 + 1)}{3s^4 + 4s^2 + 1}.$$

- b. Realize Foster-I form of the function : 7

$$z(s) = \frac{(s+1)(s+3)}{s(s+2)}.$$

- c. List any five properties of LC driving point immittance function. 6

* * *