



--	--	--	--	--	--	--	--	--	--

## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Fifth Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; Dec - 2016/ Jan - 2017

Digital CMOS VLSI Design

Time: 3 hrs

Max. Marks: 100

Note: i) Answer **FIVE** full questions, selecting **ONE** full question from each unit.

ii) Missing data, if any, may be suitably assumed.

### UNIT - I

- 1 a. Calculate the threshold voltage  $V_{TO}$  for  $V_{SB} = 0$ , given substrate doping  $10^{15} / cc$ , poly silicon gate doping density  $10^{20} / cc$ , gate oxide thickness  $650 \text{ \AA}$ ,  $N_{ox} = 2 \times 10^{10} / cm^2$ ,  $\epsilon_{Si} = 11.7\epsilon_0$ ,  $\epsilon_{ox} = 3.97\epsilon_0$ . 12
- b. Analyze the input of second order effects with respect to; 8
  - (i) Substrate bias effect
  - (ii) Channel length modulator.
- 2 a. Draw the layout of resistive load inverter with diffused resistor and undoped poly silicon resistor. 4
- b. Analyze the VTC of 3 CMOS invertors with different  $\frac{\beta_n}{\beta_p}$ . 4
- c. Calculate the noise margins of CMOS inverter. Given  $V_{DD} = 3.3V$ ,  $V_{TO,n} = 0.6$ ,  $V_{TP} = -0.7V$ ,  $K_n = 200 \mu A / V^2$ ,  $K_p = 80 \mu A / V^2$ . 12

### UNIT - II

- 3 a. Derive an expression for  $\tau_{PLH}$  and  $\tau_{PHL}$  of CMOS inverter considering; 10
  - (i)  $V_{50\%}$
  - (ii)  $V_{10\%}$
  - (iii)  $V_{90\%}$  along with I/O w/f.
- b. Briefly analyze the influence of fringing electric fields upon the parasitic wire capacitance. 4
- c. Along with voltage and current waveform, obtain an expression for average power in CMOS inverter. 6
- 4 a. Analyse the impact of interconnect delay over gate delay in sub-micron CMOS technology. 6
- b. Obtain an expression for delay by considering Elmore delay concept in a general RC tree network. 8
- c. With a typical voltages waveform, obtain an expression for oscillation frequency in a 3-stage ring oscillator. 6

**UNIT - III**

- 5 a. Obtain an expression for switching threshold voltage of CMOS NOR<sub>2</sub> Gate. 6
- b. Realize the function  $F = ABC\bar{C} + \bar{A}B + A\bar{C}$  using CMOS TG (transmission gates). 4
- c. Obtain the Euler path and draw the optimized stick diagram for the function,  

$$F = \overline{A(D+E)+BC}.$$
 10
- 6 a. Along with CMOS schematic and waveform, explain the working of NOR based clocked SR latch. 8
- b. Along with gate level schematic, nMOS schematic and waveform explain the working of NAND based SR latch. 8
- c. Realize the schematic of CMOS D latch version 1. 4

**UNIT - IV**

- 7 a. Discuss the charge storage and charge leakage phenomenon at a soft node in a CMOS n/w. 8
- b. Analyze the working of high performance of DOMINO CMOS logic. In what way it is better than Dynamic CMOS logic? Explain. 12
- 8 a. Explain the voltage boot strapping principle. Hence derive an expression for  $C_{boot}/C_S$ . 8
- b. Analyze the performance of NORA CMOS logic and obtain pipelined architecture using NORA CMOS logic. 12

**UNIT - V**

- 9 a. Derive an expression for  $I_C$  in forward Active mode, using Ebers-moll equivalent circuit. 10
- b. Realize the schematic of BiCMOS, NAND3 gate. 4
- c. Discuss the H-tree and Buffered clock distribution n/w. 6
- 10 a. Analyze the response of delay V/s  $C_L$  for CMOS and BiCMOS technology. 5
- b. Discuss briefly  $L\left(\frac{di}{dt}\right)$  noise effect in output circuits. 6
- c. Analyze the performance of 3 clock generation n/ws. 9

\* \* \*