



U.S.N

--	--	--	--	--	--	--	--	--	--

P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Sixth Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; June/July - 2015

Operational Amplifier and Application

Time: 3 hrs

Max. Marks: 100

Note: Answer any FIVE full questions, selecting at least TWO full questions from each part.

UNIT - I

1. a. Explain the following: i) CMRR ii) input offset voltage (iii) Slew rate 9
- b. Using a 741 op-amp, design a non inverting amplifier to have a voltage gain of 66. The signal amplitude is 15 mV. 5
- c. Show that non-inverting amplifier can be employed as a summing circuit. 6
2. a. Explain difference amplifier. 7
- b. Design a capacitor-coupled voltage follower using 741 op-amp. The lower cut-off frequency for the circuit is to be 50 Hz and the load resistance is $R_L = 3.9 \text{ k}\Omega$. 7
- c. Sketch the circuit of a capacitor-coupled non-inverting amplifier. Briefly explain the circuit operation. 6

UNIT - II

3. a. Explain how the upper cutoff frequency can be set for inverting amplifier. 7
- b. Describe capacitor- coupled difference amplifier. 6
- c. Explain capacitor coupled inverting amplifier using a single polarity supply. 7
4. a. Explain different frequency compensation methods. 10
- b. Describe the precautions that should be observed for op-amp circuit stability. Draw the necessary diagram. 10

UNIT - III

5. a. Draw the circuit of a precision voltage source using an op-amp and a Zener diode. Explain the circuit operation and derive the equation relating V_0 and V_2 10
- b. Design a precision full-wave rectifier to provide 2 V peak output from a sine-wave input with a peak value of 0.5 V and frequency of 1 MHz. 10
6. a. Draw an op-amp sample and hold circuit. Sketch the signal, control and output voltage wave forms. Explain the circuit operations 10
- b. A $\pm 5 \text{ V}$, 10 kHz square wave from a signal source with a resistance of 100Ω is to have its positive peak clamped precisely at ground level. Tilt on the output is not to exceed 1% of the peak amplitude of the wave. Design a suitable op-amp circuit. 10

Contd...2

UNIT - IV

- 7. a. Sketch the circuit of a triangular /rectangular waveform generator. Draw the output waveform from the circuit showing their phase relationship. Explain the circuit operation. 10
- b. State the Barkhausen Critetria for sine wave oscillator. Explain the operation of op-amp phase shift oscillator. 10
- 8. a. Using a 741 op-amp with a supply of ± 12 V, design an inverting Schmitt trigger circuit to have trigger points of ± 2 V. 10
- b. Sketch the circuit of a second-order low-pass active filter. Explain its operation. 10

UNIT - V

- 9. a. Write a circuit diagram of a op-amp series voltage regulator. Explain its operation. 10
- b. Sketch the basic circuit of a 723 IC Voltage regulator. Explain. 10
- 10 a. What is a PLL? Explain its operating principles. 10
- b. Describe the working of digital of analog converter. 10

* * * * *