



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Seventh Semester, B.E. – Electronics and Communication Engineering

Semester End Examination; Dec. - 2015

Analog CMOS VLSI Design

Time: 3 hrs

Max. Marks: 100

Note: i) Answer any **FIVE** full questions, selecting atleast **TWO** full questions from each **part**.
 ii) Assume missing data if any appropriately.

PART - A

- 1 a. Derive and explain I/V characteristics of MOSFET from fundamental concepts. 12
- b. Explain the working of source follower with its I/O characteristic and small signal equivalent circuit obtain expression for g_m and A_v . 8
- 2 a. Explain the operation of basic differential pair with a relevant diagram and I/O characteristics. 8
- b. In the circuit shown in Fig. 2(b) M_2 is twice as wide as M_1 . Calculate the small signal gain, if the bias voltage of V_{in1} and V_{in2} are equal.

 


Fig. 2(b)

- c. The circuit of Fig. 2.C uses a resistor rather than a current source to define a tail current of 1 mA.

 


Fig 2.c


Assume $(W/L)_{1,2} = 2.5/0.5$, $\mu_n C_{Ox} = 50 \mu A/V^2$, $V_{TH} = 0.6 V$, $\lambda = \gamma = 0$ and $V_{DD} = 3 V$.

- i) What is the required input CM for which R_{SS} sustains 0.5 V?
- ii) Calculate R_D for a differential gain of 5.

- 3 a. Discuss the working of cascode current mirror with cascode current source and bias voltage generator. 10
- b. Draw the circuit for calculation of G_m and calculation of R_{out} with respect to Active current mirror and derive the respective expressions. 10
- 4 a. Explain the conceptual generation of temperature independent voltage in the band gap reference and draw the actual implementation circuit of the concept. 12
- b. Explain the effect of op - amp offset voltage on the output voltage of band gap reference and means to overcome the same. 8

PART - B

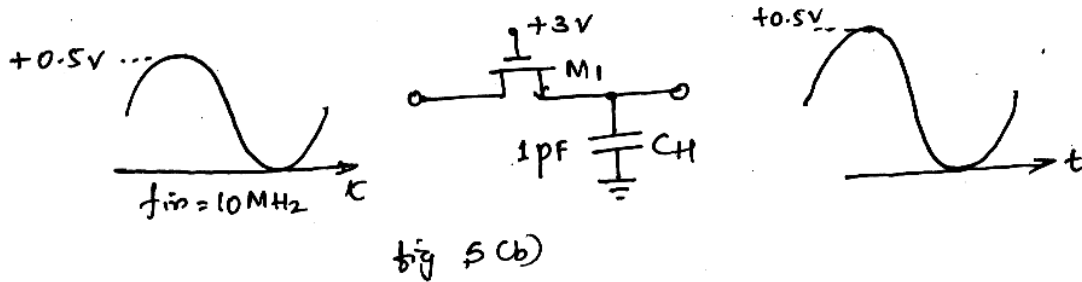- 5 a. Explain the track and hold capabilities of a sampling circuit using MOSFET switch. 6
- b. In the circuit shown in Fig. 5 (b), calculate minimum and maximum on – resistance of M_1 . Assume; $\mu_n C_{Ox} = 50 \mu A/V^2$. $W/L = 10/1$, $V_{TH} = 0.7 V$, $V_{DD} = 3 V$ and $\gamma = 0$



- c. Explain the unity gain sampler in sampling mode and in amplification mode with relevant diagrams. 8
- 6 a. Explain the working of crossed coupled oscillator with the help of loop gain characteristics. 10
- b. Explain the significance of any five parameters of VCO. 10
- 7a. Explain the working of a charge pump PLL with relevant circuit diagram and waveforms. 10
- b. Explain the process of frequency multiplication and frequency synthesis. 10
- 8 a. Discuss the short channel effects with respect to,
 - i) Threshold voltage variation 10
 - ii) Velocity saturation.
- b. Explain level 3 MOS device model along with fabrication structure and respective expressions. 10

* * * *