



**P.E.S. College of Engineering, Mandya - 571 401**  
 (An Autonomous Institution affiliated to VTU, Belgaum)  
**Second Semester, B.E. - Semester End Examination; June – 2016**  
**Electronic Devices and Communication**  
 (Common to All Branches)

Time: 3 hrs

Max. Marks: 100

Note: i) Answer **FIVE** full questions, selecting **ONE** full question from each unit.  
 ii) Assume missing data suitably.

**UNIT - I**

- 1 a. Explain full wave rectification and write the value of  $V_{dc}$ . 7  
 b. Determine  $I_D$ ,  $V_D$  and  $V_O$  for the circuit shown in Fig.1;

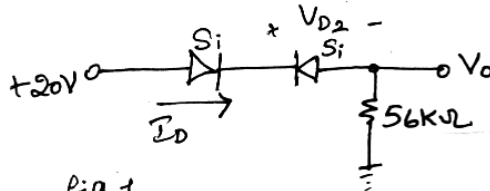


fig 1.

- c. For the network shown in Fig.2, determine the range of  $R_L$  and  $I_L$  that will result in  $V_{RL}$  being maintained at 10 V and also determine the maximum wattage rating of the diode. 6

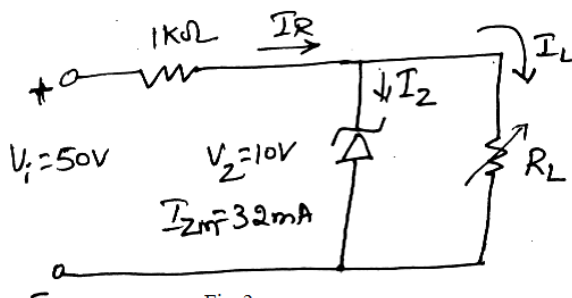


Fig. 2

- 2 a. Explain working principle of photo conductive cells. 7  
 b. Determine  $V_0$ ,  $I_1$ ,  $I_{D1}$  and  $I_{D2}$  for the parallel diode configuration shown in Fig.3,  $E = 10\text{ V}$


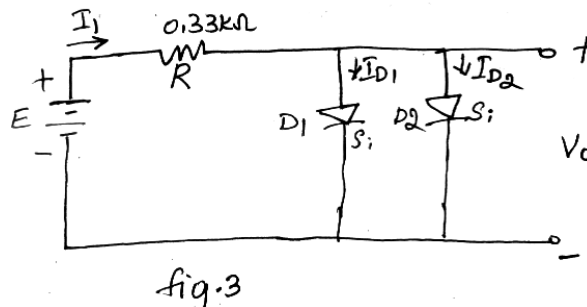


fig.3

- c. What are photo diodes? Explain the V-I characteristics of Photodiodes. 6

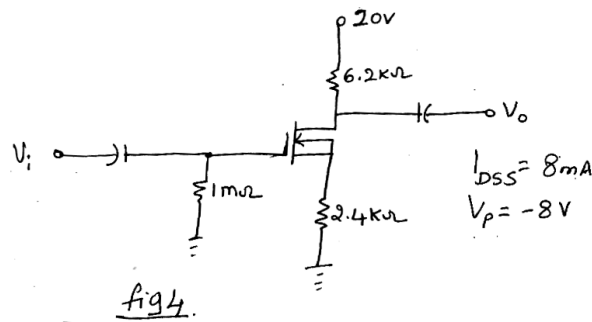**UNIT - II**

- 3 a. With neat diagram, explain the operation of an N-channel Depletion type MOSFET and write its transfer characteristics. 8  
 b. Explain the construction and characteristics of an N-channel MESFET. 7  
 c. Explain the  $I_{DQ}$ ,  $V_{GSQ}$  and  $V_D$  for the network shown in Fig.4. 6



- 4 a. Explain E-MOSFET ac small-signal model and give the equation for  $g_m$ . 7
- b. Write the block diagram of feedback circuit used as an oscillator and explain Barkhausen criterion for oscillation. 6
- c. Describe the ideal phase-shift oscillator and write the practical circuits for FET Version and explain. 7

**UNIT - III**

- 5 a. Explain the concept of virtual ground. Sketch the following circuits and explain their operation: 8
  - (i) Non-Inverting amplifier
  - (ii) Integrator.
- b. Explain the following Op-amp specification frequency parameters : 7
  - (i) Gain Band width
  - (ii) Slew Rate (SR)
  - (iii) Maximum signal frequency
  - (iv) Output offset frequency
- c. Determine the output voltage of an Op-amp for input voltages of  $V_{i1} = 150 \mu V$  and  $V_{i2} = 140 \mu V$ . The amplifier has a differential gain of  $A_d = 4000$  and the value of CMRR is: 5
  - (i) 100
  - (ii)  $10^5$
- 6 a. Show the connection of an LM124 quad Op-amp as a three-stage amplifier with gain of +10, -18 and -27. Use a 270 kΩ feedback resistor for all three circuits. What output voltage will result for an input of 150 μV? 8
- b. Draw the circuit diagram of voltage controlled voltage source and voltage controlled current source. Derive an expression for output current  $I_o$ . 6
- c. Draw the circuit and frequency response of a first order High pass filter and explain its operation. 6

**UNIT - IV**

- 7 a. Explain the working of microprocessor with neat block diagram. 6
- b. Write in brief about 8-bit, 16-bit and 32-bit micro controllers. 8
- c. Calculate the equivalent values : 6
  - (i)  $(101010111100)_2 = (?)_8 = (?)_{16}$
  - (ii)  $(240)_{10} = (?)_2 = (?)_{BCD}$
- 8 a. Explain the Internal RAM of 8051. 6
- b. Explain the following : (i) PSW 8 (ii) Special function Register (SFR).
- c. Explain in detail stack and stack pointer. 6

**UNIT - V**

- 9 a. Define the following terms : 6
  - (i) Mobile station
  - (ii) SIM
  - (iii) MSC
  - (iv) Hand-off
  - (v) FDD
  - (vi) full duplex.
- b. Explain the call establishment procedure for mobile to PSTN. 8
- c. With neat diagram explain the working of basic paging system. 6
- 10 a. List out the advantages and disadvantages of cellular system. 6
- b. Explain briefly the frequency reuse concept in cellular system. 8
- c. With neat figure explain the GSM reference architecture. 6