

--	--	--	--	--	--	--	--	--	--



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

First Semester, M. Tech – VLSI Design and Embedded System (MECE)

Semester End Examination; Jan - 2017

CMOS VLSI Design

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

- 1 a. Analyze the second order effect on IC performance with respect to,
 - i) Sub threshold conduction
 - ii) Tunneling
 - iii) Punch through effect.

6
- b. With VTC, explain the impact of variations in β values by considering CMOS inverter. 6
- c. Explain the working of differential inverter with circuit diagram and transfer characteristics. 8
- 2 a. Obtain the small signal equivalent of MOSFET and the corresponding expression for g_m . 8
- b. Derive an expression for NM_L and NM_H . 7
- c. Realize the schematic of tristate inverter and BiCMOS inverter. 5

UNIT - II



- 3 a. Explain the steps of fabrication process of NMOS technology. 9
- b. Show that the delay time and transit time are interchangeable [consider sum technology]. 6
- c. Realize the CMOS schematic and the corresponding stick diagram of NOR₃ gate. 5
- 4 a. Obtain the scaling factors for the following parameters ;
 - i) Operating frequency
 - ii) Power dissipation
 - iii) Switching energy.

6
- b. Derive an expression for delay in driving a large capacitance load in a chain of inverters with varying sizes. 8
- c. Realize the symbolic diagram of NAND₂ gate and NOR₂. 6

UNIT - III

- 5 a. Realize the function using transmission gates (TG),
 - i) $F = \bar{A} + AB + A\hat{B}C$
 - ii) $F = A\bar{B} + \bar{A}BC + ABC\bar{C}$.

6
- b. Discuss the cascading problem in Dynamic logic circuit using schematic and waveform. 6
- c. Explain the boot strapping principle and derive an expression for C_{boot} . 8
- 6 a. Obtain the Euler path for the function $F = \overline{A(D+E)+BC}$. 6
- b. With gate level, CMOS schematic and waveform, explain SR latch (NOR based). 10
- c. Find the output voltage for the following arrangements. Given $V_{DD} = 3.8$ V, $V_{Th} = 0.7$ V. 4

  

UNIT - IV

- 7 a. With necessary diagram and expression, explain the working of differential amplifier. 10
- b. Derive an expression for V_{REF} using Band gap reference concept. 10
- 8 a. Explain the concept of current mirrors along with an example. 10
- b. Explain the principle of band gap reference. Write the expression for V_{REF} . 10

UNIT - V

- 9 a. List the causes and remedies for latch-up in CMOS inverter. 10
- b. Explain the charge sharing phenomenon with an example. 6
- c. Briefly discuss the H-tree and Buffered clock distribution network. 4
- 10 a. Explain latch up in CMOS inverter with necessary diagrams. 8
- b. With a neat diagram, explain Domino logic concept. 6
- c. Discuss any three clock generating technique. 6

* * *