

--	--	--	--	--	--	--	--	--	--



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

First Semester, M. Tech - VLSI Design and Embedded System (MECE)

Make-up Examination; Feb - 2017

CMOS VLSI Design

Time: 3 hrs

Max. Marks: 100

Note: Answer **FIVE** full questions, selecting **ONE** full question from each unit.

UNIT - I

- 1 a. Discuss the working of nMOS enhancement mode transistor in different regions of operation with neat sketches and output characteristics. 10
- b. Explain the DC characteristics of the CMOS inverter with different regions of operation. 10
- 2 a. List the second order effects in a MOSFET. Briefly explain. 12
- b. Explain the pseudo nMOS inverter and differential inverter. 8

UNIT - II

- 3 a. Discuss the Lambda based design rules as applicable to MOS layers and transistors. 10
- b. Show that the expressions for rise time delay and fall time delay of a CMOS inverter is

$$t_f = 4 \frac{C_L}{\beta_h V_{DD}} \text{ and } t_r = 4 \frac{C_L}{\beta_p V_{DD}}.$$
 10
- 4 a. Sketch the fabrication process of a CMOS inverter and briefly discuss the each step. 12
- b. Draw the CMOS circuit diagram, stick diagram and layout of a two input NAND and NOR gate. 8

UNIT - III

- 5 a. Discuss the working of CMOS transmission gate. Describe the different regions of operations and associated equations. 10
- b. Draw the gate level symbol and CMOS NOR based SR Latch and explain the operation and transient analysis of SR latch. 10
- 6 a. What is pass transistor? Describe how logic '0' transfer and logic '1' transfer takes place in pass transistor. 10
- b. Explain the operation of voltage bootstrapping with suitable circuits and equation. 10

UNIT - IV

- 7 a. Explain the differential amplifier with a neat circuit diagram. 10
- b. Discuss the different types of current mirror circuits. How can these be used in the design of a differential amplifier. 10
- 8 a. Explain the cross operations amplifier with necessary expression and characteristics. 10
- b. Analyze the performance of band gap reference due to variation in temperature. 10

UNIT - V

- 9 a. List the advantages and disadvantages of CMOS over nMOS technology. 10
- b. What is the latch V_p in bulk CMOS? Mention the causes and prevention of latch up problem in CMOS inverter. 10
- 10a. Explain the clock generation and clock distribution type and storages types in dynamic CMOS inverter circuits. 10
- b. Differentiate between CMOS and Silicon-On-Insulator (SOI) Technology. 5
- c. Differentiate between nMOS and CMOS fabrication process. 5

* * *