



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Second Semester, M. Tech - VLSI Design and Embedded System (MECE)

Make-up Examination; July - 2016

Design of Analog and Mixed Mode VLSI Circuits

Time: 3 hrs

Max. Marks: 100

Note: i) Answer **FIVE** full questions, selecting **ONE** full question from each unit.
 ii) Assume missing data suitably.

UNIT - I

- 1 a. Discuss the channel length modulation concept and substrate effect and hence, develop the complete circuit model of MOSFET for small signal operation, considering device capacitances. 8

- b. For the CS stage with diode-connected load, shown in Fig. 1. Derive the expression

$$\frac{\partial V_{out}}{\partial V_{in}} = -\sqrt{\frac{(\mu/L)_1}{(\mu/L)_2}} \cdot \frac{1}{1+\eta}$$

with usual notations.

 


Fig. 1: CS stage with diode-connected load. 4

- c. Prove that $\frac{\partial V_{out}}{\partial V_{in}} = g_m (1+\eta) R_D$ for the circuit shown in Fig.2 and sketch the input-output characteristics.

 


Fig. 2: CG Stage 8

- 2 a. Considering the resistance and body effect, derive the expression for the small signal voltage gain and output resistance for source follower circuit with current source. Draw the equivalent circuit. 12

- b. Calculate the input resistance of CG stage shown in Fig. 3 and draw the small-signal equivalent circuit.

 


Fig. 3: CG Stage

8

UNIT - II

- 3 a. For the differential pair shown in Fig. 4, derive an expression for $(I_{D1} - I_{D2})$

 


Fig. 4: Differential pair

8

- b. Develop the circuit of Gilbert cell starting from the basics of differential pair. 12
- 4 a. Explain with a circuit diagram, the realization of cascode current mirror using cascode current source. 8
- b. Develop the expression for CMRR in a differential pair with active current mirror sensing common mode change. 12

UNIT - III

- 5 a. Draw the circuit of a source follower with output capacitance and its high frequency equivalent circuit. Derive the expression for the transfer function. 10
- b. Draw the source follower circuit showing noise sources and develop the expression for the input referred noise voltage. 10
- 6 a. For the simplified cascode stage shown in Fig. 5, neglecting the body effect ($\gamma = 0$), calculate the transfer function (V_{out}/ V_{in}) . 10

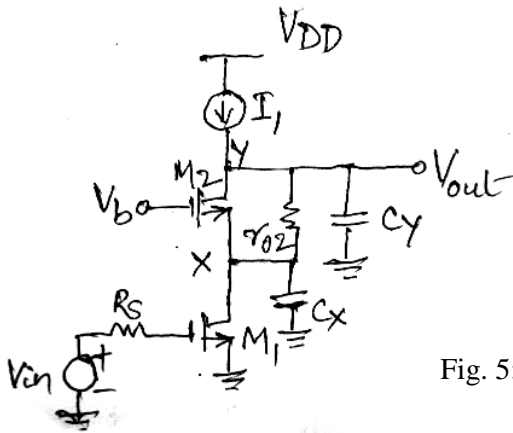


Fig. 5: Simplified cascode stage at high frequencies

- b. Draw the differential pair circuit including input-referred noise sources and prove that the input noise squared of differential pair is twice the input noise voltage squared of a common-source state. 10

UNIT - IV

- 7 a. Draw the circuit implementation of two-stage Op-AMP and explain the functions of each state. 6
- b. Discuss the various methods of boosting the gain in differential cascade. 6
- c. Discuss the response of a linear Op-AMP to a step input and hence obtain the expression for the output voltage, sketch the circuit diagram and relevant waveforms. 8
- 8 a. Calculate the expression for the input-referred thermal noise voltage of a two-stage Op-AMP. 10
- b. Derive the expression for the low-frequency PSRR of the feedback circuit shown in Fig. 6.

 


Fig 6: Differential pair with active current mirror and feedback

UNIT - V

- 9 a. Sketch the circuit of three stage ring oscillator and explain the important aspects of closed loop transfer function. 8
- b. Draw the cross-coupled oscillator circuit with tail current source and describe how the problems of conventional oscillators are overcome. 12
- 10 a. Discuss the response of a phase locked loop (PLL) of a phase step and frequency step. 12
- b. Explain the problem of lock acquisition and its solution in type-I PLL. 8

* * * *