



| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Second Semester, M. Tech - Electronics and Communication Engineering (VLSI)

Semester End Examination; June - 2016

Design of Analog and Mixed Mode VLSI Circuits

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

- 1 a. Derive the expression for I_D of a MOS transistor starting from the basics and hence obtain the expressions for I_D when the device operates in,
 - (i) Triode region 10
 - (ii) Saturation region.
- b. Discuss the second order effects in a MOS device. 10
- 2 a. Obtain the expression for voltage gain of CS amplifier using small signal analysis for the following loads :
 - (i) Resistive load, R_D 10
 - (ii) Diode connected load
 - (iii) Current source load.
- b. Obtain the expression for input impedance of CG stage taking channel length modulation and body effect into consideration. 10

UNIT - II

- 3 a. For a basic differential pair, show that under equilibrium,

$$|A_v| = \sqrt{\mu_c C_{ox} [W / L] I_{SS} R_D}$$
 10
- b. For an active current mirror processing a signal obtains the expressions for R_{out} and A_v . Explain how the drain currents of M_1 and M_2 are combined? 10
- 4 a. Explain the operation of cascode current mirror and also discuss how gate voltage bias is generated? 10
- b. Discuss the common mode response of differential pair :
 - (i) In the presence of resistor mismatch 10
 - (ii) With finite tail capacitance.

UNIT - III

- 5 a. For a source follower, using its high frequency equivalent circuit, obtain the expression for $V_{out}(s)/V_{in}(s)$ and hence obtain the expression for significant pole. 10

- b. For a common source stage obtain the expressions for $V_{out}(s)/V_{in}(s)$ and the pole frequencies. 10
- 6 a. Discuss the high frequency response of cascode stage. 10
- b. For a differential pair, using its high frequency model obtain the expression for $\frac{V_o(s)}{V_i(s)}$. 10

UNIT - IV

- 7 a. Explain the operation of single stage folded cascode Op-Amp. 10
- b. What is gain boosting? Explain how gain boosting is done in a differential cascode stage? 10
- 8 a. Discuss the Response of linear Op-Amp to step input. 10
- b. Discuss the compensation in a two-state Op-Amp. 10

UNIT - V

- 9 a. For a Colpitts oscillator obtain the expressions for,
(i) Frequency of oscillations 10
(ii) Min gains for sustained oscillations.
- b. Develop the linear model of Type-I PLL and discuss its step response. 10
- 10 a. For a unity gain switched capacitor amplifier, obtain the expression for,
 $\frac{V_{out}(s)}{V_{in}(s)}$ and hence obtain the expression for its time constant. 10
- b. Discuss the methods of generating temperature independent reference voltage. 10

* * * *