

U.S.N

--	--	--	--	--	--	--	--	--	--

P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

First Semester, M. Tech. - VLSI Design and Embedded Systems (MECE)

Make-up Examination; Feb -2017

Digital System Designing Using Verilog

Time: 3 hrs

Max. Marks: 100

Note: i) Answer FIVE full questions selecting ONE full question from each unit.

ii) Assume suitable missing data if any.

UNIT - I

- 1 a. Develop a sequential circuit with a single data input 's' and single data output '1'. The output is 1 when the input value in the current clock cycle is different from input value in the previous clock cycle. Describe also the timing diagram. 6
- b. Explain the capacitive load and propagation delay. 4
- c. Discuss the design methodology for an embedded system with block diagram. 10
- 2 a. Develop a verilog model for the burglar alarm to be priority encoder with zone 1 having highest priority zone 8 having lowest priority. 10
- b. Explain axioms of Boolean Algebra and also prove the absorption laws using only the axioms. 10

UNIT - II

- 3 a. Develop a verilog model of a code converter to convert 4 bit gray code to 4 bit unsigned binary integer. 10
- b. Describe IEEE standard 754 floating point formats. 10
- 4 a. Design a circuit for a modulo 10 counter and also develop a verilog model. 10
- b. Explain clock synchronous timing methodology with relevant diagram. 10

UNIT - III

- 5 a. Explain multiport memories. Develop a verilog model of a dual port 4K x 16 bit flow through synchronous SRAM. One port allows data to be written and read while other port allows only data to be read. 8
- b. Compute 12 bit ECC word corresponding to 8 bit data word 01100001. 4
- c. Explain the difference between synchronous and asynchronous static RAM using timing diagram. 8
- 6 a. Describe I/O block of an FPGA with neat schematic. 6
- b. Explain programmable array logic with example. 10
- c. Describe differential signalling. How does it improve noise immunity? 4

Contd.....2

UNIT - IV

- | | | |
|------|--|----|
| 7 a. | Develop a verilog model to determine greater of Value-1 and Value-2. | 10 |
| b. | Describe instruction encoding of Gumnut processor. | 10 |
| 8 a. | Explain the working of 3 bit R string DAC. | 8 |
| b. | Explain different serial interface standards. | 12 |

UNIT - V

- | | | |
|-------|--|----|
| 9 a. | Explain Kernel of an algorithm. If Kernel of an algorithm is accelerated by a factor of 100 and Kernel accounts for 90% of execution time before acceleration, what is overall speed up? | 4 |
| b. | Describe briefly video edge detection using Sobel convolution mask. Write a Sobel edge detection algorithm. | 8 |
| c. | Develop a verilog model for Sobel accelerates bus slave interface. | 8 |
| 10 a. | Explain different optimization techniques in design methodology. | 10 |
| b. | Discuss built in self test technique. | 10 |

* * *