



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Third Semester, B.E. - Computer Science and Engineering

Semester End Examination; Dec - 2017/Jan - 2018

Digital Logic Design

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

- 1 a. Realize the function $y = AB + \bar{C}$ using only (i) NAND gates and (ii) NOR gates. 8
- b. Simplify the following function using Quine-McClusky method : 12
 $f(A B C D) = \Sigma m(4, 8, 10, 11, 12, 15) + d(9, 14)$.
- 2 a. Design a minimal hardware combinational circuit with 4 inputs A, B, C and D and 1 output Z, such that $Z = 1$ if numbers of 1's in the input is more than numbers of 0's, $Z = 0$ if numbers of 1's in input is less than numbers of 0's, $Z = \text{don't care}$ when numbers of 1's is equal to numbers of 0's. 8
- b. State and prove the following theorems with example : 10
 i) Duality Theorem ii) Demorgan's Theorem.
- c. Mention any two differences between positive logic and negative logic. 2

UNIT - II

- 3 a. Design and implement 2-bit magnitude comparator. 8
- b. Implement full adder using 4 x 1 MUX. 6
- c. Implement the following functions using 3 x 8 decoder : 6
 $F_1(A, B, C) = \Sigma m(0, 2, 3, 5)$, $F_2(A, B, C) = \Sigma m(1, 2, 4, 7)$ and $F_3(A, B, C) = \Sigma m(1, 3, 6, 7)$.
- 4 a. Design and implement 4-bit carry look ahead adder. 10
- b. Write a note on parity checker and parity generator circuit with example. 10

UNIT - III

- 5 a. Implement the following functions using PLA : 6
 $F_1(A, B, C) = \Sigma m(0, 2, 4, 6)$, $F_2(A, B, C) = \Sigma m(1, 3, 5, 7)$ and $F_3(A, B, C) = \Sigma m(0, 1, 2, 3)$.
- b. Give characteristic equations, state diagram and excitation table for : 12
 (i) SR-flip flop (ii) JK-flip flop (iii) D-flip flop (iv) T-flip flop.
- c. How do you convert JK-flip flop to T-flip flop? 2
- 6 a. Explain Edge triggered SR-Flip flop. 5
- b. Explain Master-slave JK-flip flop. 8
- c. Convert SR Flip- flop to JK-Flip flop. 7

UNIT - IV

- 7 a. Design a synchronous counter using JK-flip flops to count the sequence: 0-2-4-6-0. 10
- b. Explain parallel in serial out shift register with circuit diagram, truth table and waveform. 10
- 8 a. Briefly explain the design of Ring counter and Johnson counters using shift register. 10
- b. Design mod-6 synchronous counter using T-flip flop. 10

UNIT - V

- 9 a. Explain Dual-slope A/D conversion. 10
- b. Write Verilog/ VHDL code to implement : 10
- (i) 8 x 1 MUX (ii) 3:8 decoder.
- 10 a. Explain Binary ladder. 5
- b. Write VHDL code to implement : 15
- (i) 3 bit up counter and down counter
- (ii) Johnson Counter
- (iii) Ring Counter

* * *