

--	--	--	--	--	--	--	--	--	--



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Third Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; Dec - 2017 / Jan - 2018

Electrical Network Analysis

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

- 1 a. Distinguish the following with suitable examples: 10
 - i) Linear and non-linear elements
 - ii) Independent and dependent sources.
- b. Write the equation for the circuit shown in Fig-1b. Determine mesh currents using mesh analysis. 10
- 2 a. Develop a general model equation for a general network in the form $[Y][V] = [I]$, where $[Y]$ = Admittance matrix, $[V]$ = Node voltage matrix and $[I]$ = Source current matrix. 10
- b. Find the power delivered by the 5 A current source in the circuit shown in Fig-2b, using the node analysis method. 10

UNIT - II

- 3 a. Define the following with suitable examples : 10
 - i) Planar and non-planar graphs
 - ii) Twigs and links
 - iii) Incidence matrix.
- b. For the circuit shown in Fig.-3b, write the graph of the network and obtain the tie-set schedule considering J_1, J_2, J_3 as tree branches. Calculate all the branch currents. 10
- 4 a. Explain with example the principle of duality. 10
- b. Find the maximum possible number of tree for the network shown in Fig-4b. 10

UNIT - III

- 5 a. Find the condition for the maximum power transfer in the following Fig-5a, network type AC source, complex source impedance and complex load impedance but only load resistance varying. 10
- b. Obtain the Thevenin's equivalent of the network shown in Fig-5b, between the terminals X and Y. 10
- 6 a. Show that the resonant frequency of series resonant circuit is equal to the geometric mean of two half power frequencies. 10
- b. A series RLC circuit consists of a 50Ω resistance, 0.2 H inductance and $10 \mu\text{F}$ capacitor with an applied voltage of 20 V. Determine the resonant frequency. Find the Q factor of the circuit. Compute the lower and upper frequency limits and also find the bandwidth of the circuit. 10

UNIT - IV

- 7 a. Establish the procedure for evaluating the initial conditions with suitable examples. 10

- b. In the circuit shown in Fig-7b, $V = 10\text{ V}$, $R = 10\ \Omega$, $L = 1\text{ H}$, $C = 10\ \mu\text{F}$ and $V_c = 0$, find $i(0+)$, $di(0+)/dt$ and $d^2i(0+)/dt^2$. Assume switch is closed at $t = 0$. 10
- 8 a. Obtain the Laplace transformation of the waveform shown in Fig.-8 a. 10
- b. State and prove convolution theorem. Using the same find $f(t)$ when $F(s) = (1)/(s^2(s+1))$. 10

UNIT - V

- 9 a. Test whether the following polynomial is Hurwitz: $P(S) = S^4 + S^3 + 5S^2 + 3S + 4$. 10
- b. Realize Cauer-II form of LC network for the following function: 10

$$Z_{LC}(S) = \frac{S(S^4 + 3S^2 + 1)}{3S^4 + 4S^2 + 1}$$

- 10 a. Define h-parameters. Show that the transmission parameter matrix of a cascade of two port networks is the product of the transmission parameter matrices of the individual two port networks. 10
- b. Determine the y-parameter of the two-port network shown in Fig.-10b. 10

