


 U.S.N

--	--	--	--	--	--	--	--	--	--

P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Seventh Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec - 2017/Jan - 2018

AC-DC Drives

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

- 1 a. With a neat block diagram, state the essential parts of an electric drive system. Explain them briefly. 10
- b. Explain the four quadrant operation of DC motor drive. State the conditions to be satisfied for each quadrant operation. 10
- 2 a. With a neat circuit diagram and waveforms, explain the working of DC series motor fed from single phase half controlled rectifier. Assume continuous conduction mode. 10
- b. A 200 V, 875 rpm, 150 A separately excited DC motor has an armature resistance of 0.06Ω . It is fed from a single phase fully controlled rectifier with an AC source voltage of 220 V, 50 Hz. Assuming continuous conduction, calculate; 10
- i) Firing angle for rated motor torque and 750 rpm
- ii) Firing angle for rated motor torque and -500 rpm
- iii) Motor speed for $\alpha = 160^\circ$ and rated torque.

UNIT - II

- 3 a. Explain the operation of three phases fully controlled rectifier control of DC separately excited motor. 10
- b. A 220 V, 1500 rpm, 50 A separately excited DC motor with armature resistance of 0.5Ω is fed from a three phase fully controlled rectifier. Available AC source has a line voltage of 440 V, 50 Hz. A star-delta connected transformer is used to feed the armature. So that motor terminal voltage equals rated voltage when converter firing angle is zero. 10
- I) Calculate transformer turns ratio
- II) Determine the value of firing angle :
- i) Motor is running at 1200 rpm and rated torque
- ii) When motor is running at -800 rpm and twice the rated torque.
- 4 a. Explain with a circuit diagram and waveforms, the regenerative braking of a separately excited DC motor by using Chopper. 10

- b. A DC-DC converter is used on regenerative braking of a DC series motor. The DC supply voltage is 600 V. The armature resistance is $R_a = 0.02 \Omega$ and the field resistance is $R_f = 0.03 \Omega$. The back emf constant is $K_v = 15.27 \text{ mV/A rad/s}$. The armature current is $I_a = 250 \text{ A}$. If the duty cycle is 0.6. Determine; 10
- i) Average voltage across chopper ii) Power regenerated to the dc supply
 iii) Minimum possible braking speed iv) Maximum possible braking speed
 v) Motor speed.

UNIT - III

- 5 a. Derive an expression for closed loop control of a separately excited DC motor for change in voltage. 10
- b. With the help of block diagram, explain the open loop control operation of a DC drives. 10
- 6 a. What meant by phase locked loop? With the help of block diagram, explain the concept of PLL. 10
- b. With the help of block diagram, explain the closed loop control operation of DC drives using microcontroller. 10

UNIT - IV

- 7 a. Discuss on brief the speed control by frequency control and v/f control methods. 10
- b. Explain in brief the plugging and regenerative braking of an induction motor. 10
- 8 a. A three phase, 460 V, 60 Hz, 4 pole Y connected induction motor has the following parameters : 10
- $R_s = 1.01 \Omega$, $R'_r = 0.69 \Omega$, $X_s = 1.3 \Omega$, $X'_r = 1.94 \Omega$ and $X_m = 43.5 \Omega$. The no-load loss is negligible. The load torque is proportional to the speed squared, is 41 N-m at 1740 rpm. If the motor speed is 1550 rpm. Determine; 10
- i) Load torque ii) Rotor current iii) Stator supply voltage
 iv) Motor input current v) Motor input power.
- b. With necessary circuit and speed torque curves, explain the operation of static scherbius drive. 10

UNIT - V

- 9 a. With a neat circuit, explain the working of self controlled synchronous motor drive employing load commutated thyristor inverter. 10
- b. Explain the operation of a synchronous motor when fed from a fixed frequency supply. 10
- 10 a. With a neat sketch, explain paper mill drive system. 10
- b. With the help of block diagram, explain the various stages of operation involved in cement mills. 10