



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Third Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; Dec - 2017/Jan - 2018

Analog Electronics Circuits


Time: 3 hrs

Max. Marks: 100


Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

 - 1 a. With a neat diagram, explain the structure of *n*-channel enhancement type MOSFET. 6
- b. Design the circuit shown in Fig. 1(b) to obtain a drain current of 80 μ A. Find the value required for R, and find the DC voltage V_D , let the NMOS transistor have $V_t = 0.6$ V, $\mu_n C_{ox} = 200 \mu$ A/V², $L = 0.8 \mu$ m and $w = 4 \mu$ m. (Assume $\lambda = 0$). 6



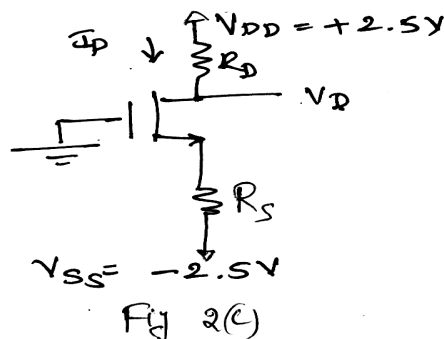- c. Explain the working of MOSFET as an amplifier with the help of a neat diagram and the transfer characteristics. 8
- 2 a. With relevant diagram, explain biasing by fixing V_{GS} . 6
- b. With the help of equivalent circuit and the simplified circuit, explain common source amplifier. 8
- c. Design the circuit shown in Fig. 2(c) so that the transistor operates at $I_D = 0.4$ mA and $V_D = +0.5$ V. The NMOS transistor has $V_t = 0.7$ V, $\mu_n C_{ox} = 100 \mu$ A/V², $L = 1 \mu$ m and $w = 32 \mu$ m. Neglect channel-length modulation effect ($\lambda = 0$). 6



UNIT - II

- 3 a. Define : 6
 - i) Input offset current ii) Slew rate iii) Input offset voltage.
- b. Design a non-inverting amplifier to have a voltage gain of 66 for input amplitude of 15 mV by using Op-Amp741. (Assume $I_{Bmax} = 500$ nA). 6

- c. Explain the operation of a difference amplifier with neat diagram and derive the equation for output voltage. 8
- 4 a. With a neat diagram, explain the use of single polarity supply for capacitor-coupled voltage follower. 6
- b. Design a capacitor-coupled voltage follower using a 741 operational amplifier. The lower cut-off frequency for the circuit is to be 50 Hz and the load resistance $R_L = 3.9 \text{ k}\Omega$. [Assume $I_{B_{\max}} = 500 \text{ nA}$]. 6
- c. With neat diagram, illustrate how high input impedance capacitor coupled voltage follower can be designed? 8

UNIT - III

- 5 a. With neat diagram, explain the phase lag compensation. 6
- b. List precautions that should be observe for Op-Amp circuit stability. Explain in each case. 8
- c. With the help of waveforms, explain the effect of slew rate on bandwidth and output amplitude. 6
- 6 a. With neat diagram, explain the working of non-inverting zero crossing detector. 6
- b. With neat diagram, explain the working of integrating circuit. 6
- c. Design a differentiating circuit to give an output of 5 V, when the input changes by 1 V in a time of 100 μs . Use the Op-Amp with a bipolar input voltage. Draw the circuit diagram. 8

UNIT - IV

- 7 a. Explain the working of saturating precision half wave rectifier. 6
- b. Show how a half wave precision rectifier can be combined with a summing circuit to produce a full wave precision rectifier. Explain. 8
- c. Show how Zenor diodes can be used to limit the output. 6
- 8 a. Sketch an Op-Amp precision rectifier peak detector circuit. Explain the circuit operation. 6
- b. Using a BIFET Op-Amp design an astable multi-vibrator to have a $\pm 9 \text{ V}$ output with a frequency of 1 kHz. Draw the circuit diagram. 7
- c. Explain the working of 555 timer as an astable multi vibrator. 7

UNIT - V

- 9 a. Explain the working of phase shift oscillator. 6
- b. Design a second order low pass filter for a cut-off frequency of 1 kHz. Draw the circuit diagram [use Op-Amp 741]. 6
- c. With neat diagram, explain the working of triangular / rectangular wave generator. 8
- 10 a. With neat diagram, explain the working of adjustable output regulator. 8
- b. Explain the working of 723 as low voltage regulator. 6
- c. Design LM317 for an output voltage of 9 V. 6