



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Third Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; Dec - 2017 / Jan - 2018

Network Analysis and Synthesis

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

1 a. Using Mesh analysis, find the steady state sinusoidal current i_1 for the circuit shown in

Fig. 1a. When $V_s = 10\sqrt{2} \cos[100t + 45^\circ]$ Volt.

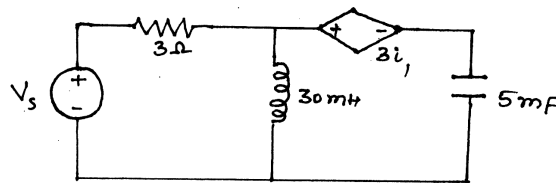


Figure - 1a

10

b. Using Nodal analysis, find the power delivered by the source in the circuit shown in Fig. 1b.

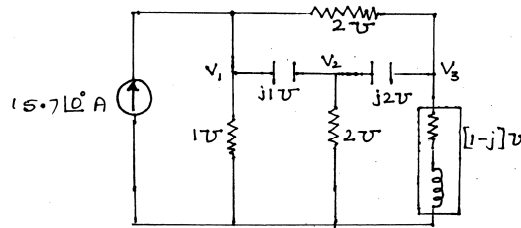


figure - 1b

10

2 a. State and prove maximum power transfer theorem for AC circuits.

7

b. For the Network shown in Fig. 2b, obtain the Thevinin's equivalent as seen from terminals p and q.

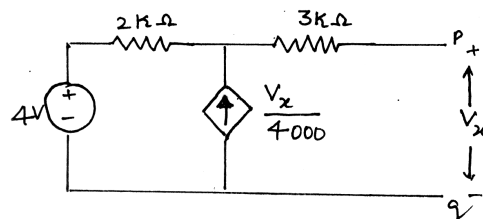


figure - 2b

7

c. The network shown in Fig. 2c consists of two star connected circuits in parallel. Obtain the single delta connected equivalent.


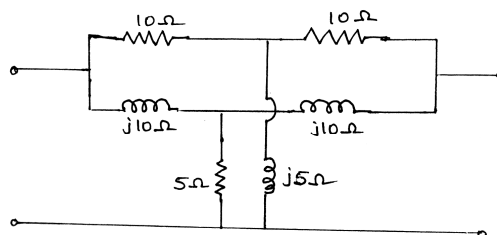


figure - 2c


6

UNIT - II

- 3 a. Derive the expression for the resonant frequency of the circuit where R_L = resistance in the inductor branch and R_C = resistance in the capacitor branch. Also show that the circuit will resonate at all frequencies if $R_L = R_C = \sqrt{\frac{L}{C}}$. 10
- b. A 220 V, 100 Hz AC source supplies a series RLC circuit with a capacitor and a coil. If the coil has 50 mΩ resistance and 5 mH inductance, find at a resonance frequency of 100 Hz, what is the value of capacitor? Also calculate 'Q' factor and Half power frequencies. 10
- 4 a. In a circuit as shown in Fig. 4a, the switch K is changed from position 1 to 2 at $t = 0$. The steady state having been reached before switching. Find values of $i(t)$, $\frac{di(t)}{dt}$ and $\frac{d^2i(t)}{dt^2}$ at $t = 0^+$. 10

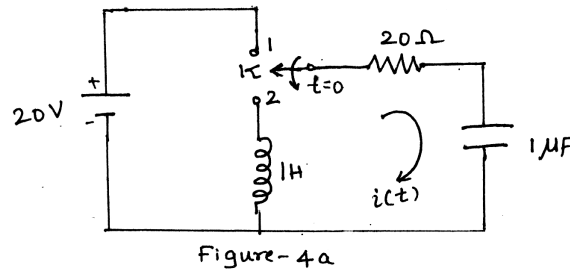

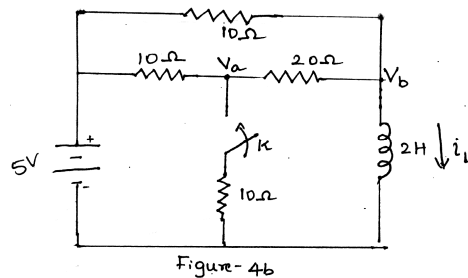- b. In the network shown in Fig. 4b, a steady state is reached with the switch K open. At $t = 0$ the switch is closed for the element values given, determine the values of $V_a(0^-)$ and $V_a(0^+)$. 10



UNIT - III

- 5 a. State and prove;
- i) Initial value theorem 10
 - ii) Final value theorem as applied to Laplace-Transform.
- b. Find the Laplace transform of the following :
- i) $\sin^2(t)$ ii) $\cos^2(t)$ iii) $5 + 4e^{-2t}$. 10
- 6 a. Using the convolution theorem, find the inverse Laplace transform of the following functions: 10
- i) $F(s) = \frac{1}{s(s+1)}$ ii) $F(s) = \frac{1}{(s-a)^2}$.

- b. The switch in the network of Fig. 6b opens at $t = 0$. Use Laplace transformation analysis to determine the voltage across the capacitor for $t \geq 0$.

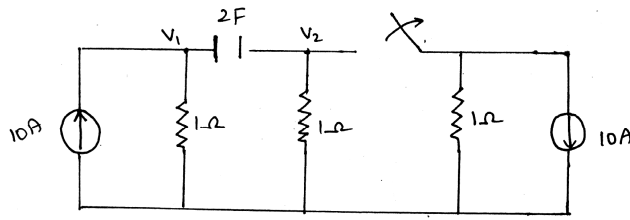


Figure - 6b

10

UNIT - IV

- 7 a. Obtain Z- Parameters of the circuit shown in Fig.7a.

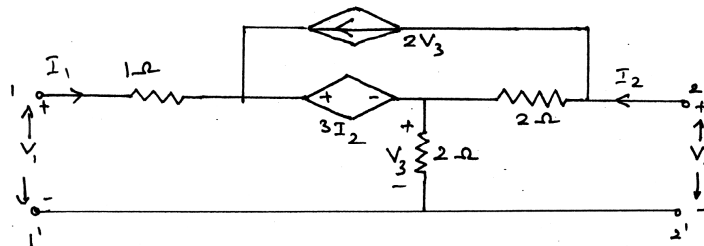


Figure-7a

10

- b. Determine Y parameters of the two-port network shown below in Fig. 7b.


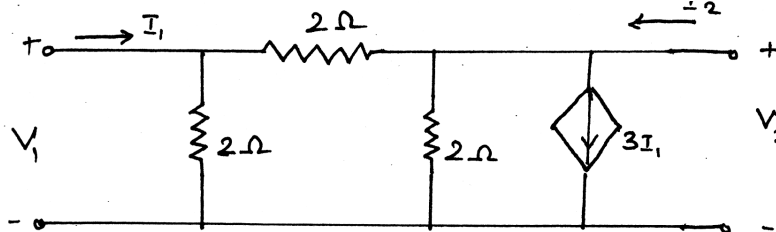


Figure-7b


10

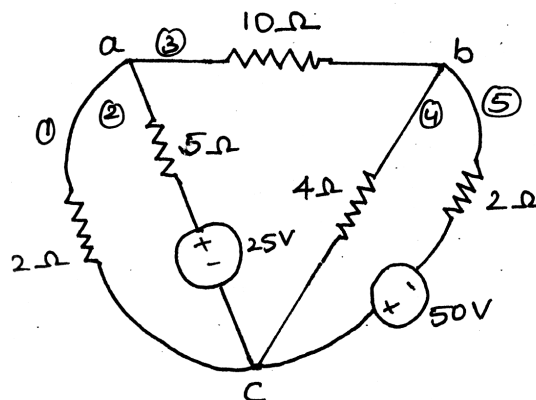- 8 a. For the network shown in Fig. 9a, draw the graph. Select a tree with branches 2 and 4. Draw the cut-set matrix. Write down the equilibrium equations with node-pair voltages as variables. Solve these equations and find the various branch voltages and currents. The integers indicate branch numbers.



12

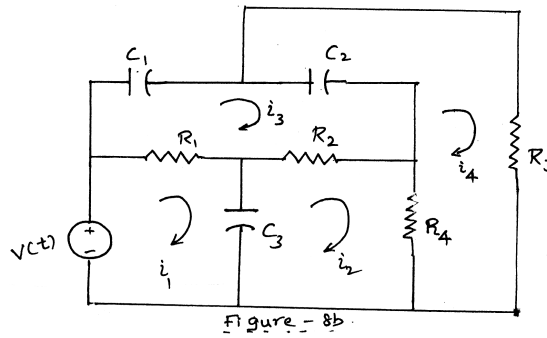- b. Draw the dual of the network shown in Fig. 8b. Show that the loop equations of the network are the duals of the nodal equations of the dual network.



8

UNIT - V

- 9 a. Test whether the following polynomial is Hurwitz:

$$G(s) = s^3 + 2s^2 + 3s + 6.$$

7

- b. Test whether the function given is a positive real function :

$$F(s) = \frac{s^2 + 2s + 25}{s^2 + 5s + 16}.$$

7

- c. List the properties of LC immitance function.

6

- 10 a. Synthesize the following functions in Foster Form :

$$Z(s) = \frac{(s+1)(s+4)}{(s+2)(s+3)}.$$

8

- b. Synthesize the following functions in Caver form :

$$Z_{LC}(s) = \frac{(s^2 + 1)(s^2 + 4)}{s(s^2 + 2)}.$$

8

- c. List the properties of R-L impedances and R-C admittances.

4

* * *