



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Third Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec - 2017/Jan - 2018

Analog Electronics Circuits


Time: 3 hrs

Max. Marks: 100

Note: Answer **FIVE** full questions, selecting **ONE** full question from each unit.


UNIT - I

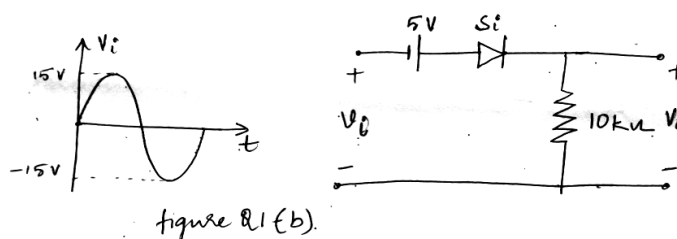- 1 a. What is biasing of transistor? Explain the factors that affect selection of Q-point anywhere in the active region for the transistor to operate as an amplifier. 8
- b. For the clipping circuit shown in Fig. Q 1(b). Determine the transfer characteristics and sketch the output wave form.



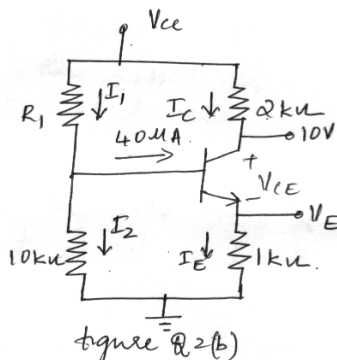- c. Explain the effect of various capacitors on frequency response of the amplifier. 6
- 2 a. Explain the operation of negative clamper. 6
- b. For the voltage divider bias shown in the Fig. Q 2(b). Determine;
 - (i) I_C and V_E (ii) V_{CC} and V_{CE} (iii) V_B and R_1 .

Assume silicon transistor with $\beta = 80$.



- c. Explain the operation of voltage doubler circuit. 6

UNIT - II

- 3 a. Derive the expression for A_V , A_I , R_i and R_o for CE amplifier using h-parameter model. 10
- b. With the neat circuit diagram explain the operation of RC phase shift oscillator. Write the expression for the frequency of oscillation. 10
- 4 a. Derive the expression for frequency of wein bridge oscillator and explain its operation with a neat circuit diagram. 10

- b. Starting from fundamentals, define h-parameter and obtain h-parameter equivalent circuit of common emitter configuration. 10

UNIT - III

- 5 a. With a block diagram, explain the concept of feedback. List the advantages of Negative feedback. 10
- b. Draw the block diagram of voltage series feedback amplifier and find the effect of feedback on input and output impedances. 10
- 6 a. Derive the expression for input resistance of current series and current shunt feedback amplifier. 10
- b. Determine the voltage gain, input and output impedance with feedback for voltage series having $A = -100$, $R_i = 10 \text{ k}\Omega$ and $R_o = 20 \text{ k}\Omega$ for feedback with $\beta = -0.1$. 5
- c. Show how bandwidth of an amplifier increases with negative feedback? 5

UNIT - IV

- 7 a. Draw the circuit of class A transformer coupled power amplifier. Explain the operation of the circuit with the help of neat waveform. Also derive an expression for maximum efficiency of conversion. 12
- b. A class B power amplifier is delivering an input voltage of 10 V peak to a 8Ω load, if DC power supply is 30 V. Calculate; 8
- (i) DC power input (ii) AC power delivered to load
- (iii) Conversion efficiency (iv) Power developed in the collector of each transistor.
- 8 a. With a neat diagram and waveform, explain the operation of class-B push-pull power amplifier. Also show how even harmonic can be eliminated with push-pull operation? 10
- b. Explain the operation of series fed direct coupled class-A power amplifier. Also show that the maximum efficiency of series fed direct coupled class-A power amplifier is 25%. 10

UNIT - V

- 9 a. Sketch the circuit of 4-input R-2R DAC and explain its operation. 10
- b. Draw the diagram of an Op-Amp inverting schmitt trigger circuit. Explain the circuit operation. Define UTP and LTP. Sketch the typical input and output waveform. 10
- 10 a. Briefly explain : 8
- (i) Successive approximation A/D converter
- (ii) Sample and hold circuit.
- b. With the help of neat circuit diagram. Explain how output offset voltage can be nullified using Op-Amp? 6
- c. Briefly explain how Op-Amp can be used as comparator. 6