



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Fifth Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec - 2017/Jan - 2018

Operational Amplifiers and Linear Integrated Circuits

Time: 3 hrs

Max. Marks: 100


Note: i) Answer **FIVE** full questions, selecting **ONE** full question from each unit
 ii) Use of standard registers, capacitors and data sheets of Op-Amps are allowed.

UNIT - I

- 1 a. Sketch the circuit for capacitor coupled voltage follower. Design and explain its operation. 10
- b. A capacitor coupled non-inverting amplifier using 741 Op-Amp is to have $A_v = 100$ and $V_s = 5$ V. The load resistance is $10\text{ k}\Omega$ and lower cut-off frequency is to be 100 Hz. Design a suitable circuit. 10
- 2 a. Sketch the circuit of high input impedance capacitor coupled non-inverting amplifier. Briefly explain the circuit diagram. 10
- b. Draw a sketch to show how a capacitor coupled voltage follower should be with a single polarity supply. Briefly explain. 10

UNIT - II

- 3 a. Show how feedback on an Op-Amp inverting amplifier can produce instability. State the Bark Hausen criteria and explain condition for oscillations. 10
- b. Explain Miller effect, and show how it can be used to stabilize an Op-Amp circuit. 10
- 4 a. Define bandwidth, gain bandwidth product and unity gain frequency for an Op-Amp. Briefly explain. 8
- b. Determine the typical upper cutoff frequency for the inverting amplifier in Fig. 1. 8

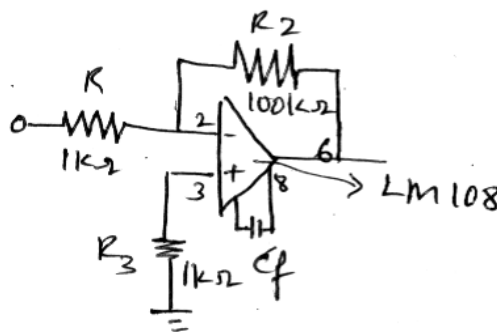

When the compensating capacitor (C_f) value is, i) 30 pF ii) 3 pF

- c. Explain how load capacitance can cause instability? 4

UNIT - III

- 5 a. Sketch the circuit of a saturating type half-wave precision rectifier. Explain with neat waveforms. 10

- b. Design a precision full wave rectifier to produce a 2 V peak output from a sine wave input with a 0.5 peak value and 1 MHz frequency use bi-polar Op-Amps with a supply voltage of ± 15 V. 10
- 6 a. Design a triangular waveform generator to produce a ± 2 V, 1 kHz output. Use ± 15 V supply and specify the minimum Op-Amp SR (Slew Rate). 10
- b. Explain the operation of Wein-bridge oscillator with neat diagram. 10

UNIT - IV

- 7 a. Sketch the circuit of an Op-Amp employed as a non-inverting zero-crossing detector. Explain with neat waveforms. 10
- b. Sketch and explain a typical input /output characteristics for an inverting Schmitt trigger circuit. 10
- 8 a. Sketch the circuit of a second order low pass active filter and explain its operation. 10
- b. Define cutoff frequency, bandwidth, pass band, stop band and insertion loss. 10

UNIT - V

- 9 a. Draw the circuit of a state-variable filter. Briefly explain the circuit operation and write equations for Q and f_0 . 10
- b. Draw the basic block diagram and waveforms for a PLL system. Explain briefly. 10
- 10 a. With reference to voltage regulator, define source effect, load effect, line regulation and load regulation with equations. 10
- b. Design the voltage regulator circuit to produce a 12 V output with a 50 mA maximum load current. 10

* * *