



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

First Semester, B.E. - Semester End Examination; Dec - 2017/Jan - 2018

Basic Electronics

(Common to All Branches)

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

- 1 a. Define Q-Point. Explain the importance of Q-point selection on the DC load line. 5
- b. With the help of neat circuit diagram and waveform, derive an expression for the Ripple factor of HWR with capacitor filter. 8
- c. In a full wave bridge rectifier, the transformer secondary voltage is $100 \sin \omega t$. The forward resistance of each diode is 25Ω with Load resistance 950Ω . Calculate; 7
- i) DC output voltage ii) Ripple factor
- iii) Efficiency iv) PIV across diodes.
- 2 a. With necessary circuit diagram and waveforms, explain the working principle of center tapped transformer FWR: 8
- b. Design a Zenor voltage regulator for the following specification : 6
- Output voltage = 5 V, Load current = 20 mA, Zenor voltage = 500 mV, Input voltage = 12 ± 3 V.
- c. Write a note on Solar cell. 6


UNIT - II

- 3 a. Sketch and explain drain and transfer characteristics for an n-channel depletion type MOSFET. 8
- b. Compare enhancement type n-channel MOSFET with p-channel using symbol and characteristics curve as a parameter. 6
- c. Design a FET based phase shift oscillator with $g_m = 5000 \mu\text{sec}$, $r_d = 40 \text{ k}\Omega$, $R = 10 \text{ k}\Omega$ for oscillator operation at 1 kHz and R_d for $A > 29$. 6
- 4 a. Sketch the transfer characteristics for an n-channel depletion type MOSFET with $I_{DSS} = 10 \text{ mA}$ and $V_p = -4 \text{ V}$. 7
- b. State and explain Barkhausen criteria. 5
- c. With the suitable diagram, explain FET based phase-shift oscillator. 8

UNIT - III

- 5 a. Develop a gain equation from an AC equivalent circuit of Op-Amp in inverting mode. 6
- b. Explain i) Gain-Bandwidth ii) Slewrates iii) Maximum Signal frequency. 7

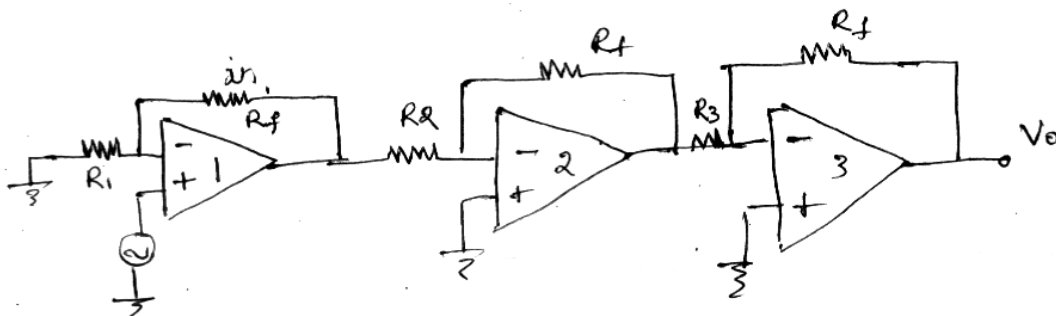- c. Determine the output voltage of an Op-Amp for input voltages of $V_{i1} = 150 \mu\text{V}$ and $V_{i2} = 140 \mu\text{V}$. The amplifier has a differential gain of $A_d = 4000$ and the value of CMRR is : $a = 100$ and $b = 10^5$ 7
- 6 a. In the circuit shown below $R_f = 470 \text{ k}\Omega$, $R_1 = 4.3 \text{ k}\Omega$, $R_2 = 33 \text{ k}\Omega$ and $R_3 = 33 \text{ k}\Omega$. Find the output voltage for an input of $80 \mu\text{V}$.



- b. With a neat circuit diagram, explain : 6
- i) Current controlled current source ii) Voltage controlled voltage source. 8
- c. Write the Op-Amp based LPF and HPF. Also mention its frequency response. 6

UNIT - IV

- 7 a. Using Boolean identities prove the following : 4
- i) $(A + B) \cdot (\bar{A} + C) = A + BC$ ii) $ABC + \bar{A}\bar{B}C + A\bar{B}\bar{C} = AB + AC$ 4
- b. Perform the following : 8
- i) $658.825_{(10)} = \dots_{(8)}$ ii) $725.25_{(8)} = \dots_{(10)} = \dots_{(2)}$
- iii) $0.0111_{(2)} = \dots_{(10)}$.
- c. Simplify and implement the following boolean expression using NOR gates only : 8
- i) $Y = \overline{(A + \bar{B} + C)(\bar{A} + B + C)(A + B)}$ ii) $Y = \bar{A}BC + A\bar{B}C + ABC$.
- 8 a. Design and implement full adder using two half adder. 8
- b. Subtract : 6
- i) $(11001 - 101101)_2$ using 2^s complement ii) $48 - 23$ using 2^s complement. 6
- c. List and explain the characteristics of digital ICs. 6

UNIT - V

- 9 a. Define Amplitude Modulation. Derive an expression for total transmitted power of AM wave. 10
- b. With neat block diagram, explain superheterodyne receiver. 10
- 10 a. With a neat diagram, explain LVDT. Also mention advantage and disadvantage of LVDT. 10
- b. Illustrate the working of monochrome cathode ray tube with neat diagram. 10