



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

First Semester, B.E. - Semester End Examination; Dec - 2017/Jan - 2018

Basic Electrical Engineering
(Common to All Branches)


Time: 3 hrs

Max. Marks: 100


Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

- 1 a. State and explain KCL and KVL as applied to DC circuits. Give the sign conventions used, and illustrate the same through a sample circuit example. 8
- b. Two identical coils of 1200 turns each are placed side by side such that 60% of flux of one coil links the other. A 10 A current in first coil sets flux of 0.12 mWbr. If the current in that coil changes from (+10A) to (-10A) in 20 ms. Find; 6
 i) Self inductance (ii) Self emf induced for both coils.
- c. A portion of a network has a configuration as shown in Fig Q. 1(c). The voltage drop across 15 Ω is 30 V. Find the values of R and I. 6

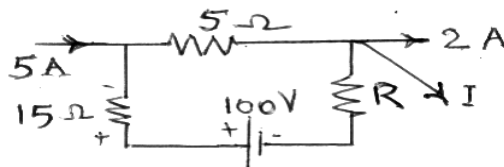


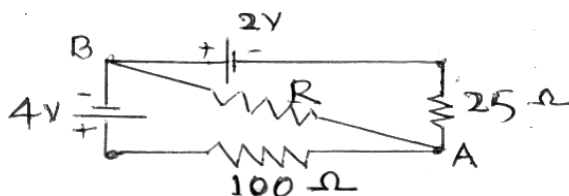- 2 a. Define clearly the following : 12
 i) Faraday's Laws ii) Lenz's law
 iii) Fleming's rule iv) Statistically and Dynamically induced emf.
- b. For the network shown in Fig. Q 2(b) determine the direction and magnitude of current flow in the resistor 'R' of 10 Ω.



UNIT - II

- 3 a. Show that the voltage across a pure inductor and the current through it are displaced by 90°. Hence prove that the average power in a pure inductive circuit is zero. Draw the necessary wave shapes of current, voltage and power signals involved. 8
- b. The series circuit of R = 8 Ω, L = 20 mH, has an applied voltage, v(t)=283sin (300t+90°) V. Find the current drawn by the circuit. 6
- c. Define RMS value of an AC quantity. Derive an expression for the same in terms of the maximum value. 6
- 4 a. For the waveform shown in Fig. Q 4 (a). Find; 8
 i) Peak voltage ii) Frequency
 iii) periodic Time iv) Instantaneous values at t = 2 ms, 6 ms and 10 ms.

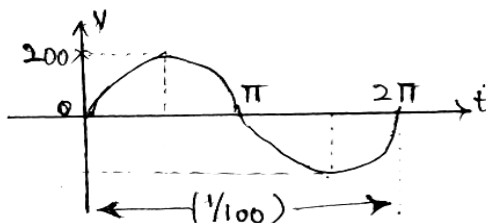

- b. Define: i) Form Factor and peak factor and find their values for a sinusoidally varying current. 6
 ii) Power factor and give its value for a Pure-R, Pure-L and Pure-C circuit.
- c. A resistor 'R' is connected in series with the capacitor 'C' to a 50 Hz, 240 V supply. Find the values of R and C, so that 'R' absorbs 300 W at 100 V. 6

UNIT - III

- 5 a. Obtain the relations for line voltages and line currents for delta connected load. Draw the phasor diagram. Also state the corresponding relations for the star connected load. 8
- b. Three coils each of $R = 8 \Omega$ and $X_L = 6 \Omega$ are connected in star across a 400 V, 3 phase supply. Calculate the line current and the power absorbed. 6
- c. Discuss on the need for and advantages of three phase AC systems. 6
- 6 a. With the help of a neat sketch, explain the construction and working of a single phase energy meter. 8
- b. Write a note on : i) Need for earthing 6
 ii) Electric shock and precautions needed to protect against the same.
- c. The power input to a 3-phase circuit was measured by two watt meters and readings are: (3400 W) and (-1200 W) respectively. Calculate the total power and PF of load. 6

UNIT - IV

- 7 a. Draw the cross sectional view of DC machine and explain the function of each part. 8
- b. Derive an equation for the torque developed in a DC motor and state the torque is proportional to the product of armature current and flux. 6
- c. A 500 V shunt motor has 4 poles and wave wound armature, with 492 conductors. Flux per pole is 50 mWbr, FL current is 20 A and $R_a = 0.1 \Omega$, $R_f = 250 \Omega$; Calculate the speed and torque developed. 6
- 8 a. With a neat sketch, explain the constructional details of a synchronous generator. 8
- b. Write briefly on : i) Necessity of a starter in DC motors 6
 ii) Applications of DC motor.
- c. A 3-phase, 16 pole alternator has Y-connected winding with 144 slots and 10 conductors per slot. Flux per pole is 30 mWbr and speed is = 375 RPM. Find the frequency, the phase and line emf. Assume pitch factor $k_p = 0.1$ and distribution factor $k_d = 0.96$. 6

UNIT - V

- 9 a. What are the main parts of transformer? What is the function and the main material of construction in each case? 6
- b. With respect of a transformer, give reasons for the following :
 i) This is a small primary current even when on no load 6
 ii) The core losses are constant for any load.
 iii) There is an inrush of current in primary circuit when the secondary is loaded.
- c. Define power efficiency and regulation of a transformer. The maximum efficiency at FL and upf of a single phase, 25 kVA, 500/1000 V, 50 Hz, transformer is 98%. Determine the efficiency at : 8
 i) 75% load, 0.9 pf ii) 50% load, 0.8 pf.
- 10 a. Define Synchronous speed, slip speed and motor speed of a 3-phase induction motor. Explain why the induction motor cannot run at a synchronous speed? 6
- b. Why is a starter needed for starting a 3-phase induction motor? 4
- c. Discuss on the application of squirrel cage and slipring induction motors. 4
- d. A 3-phase, 5 HP, 400 V, 50 Hz, induction motor is working at full load with 90% efficiency at a pf of 0.866 lag. Determine the power input and line current (Take 1 HP equal to 746 W). 6