

--	--	--	--	--	--	--	--	--	--



## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Fourth Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; June - 2017

Operational Amplifier and Applications

Time: 3 hrs

Max. Marks: 100

*Note: Answer FIVE full questions, selecting ONE full question from each unit.*

### UNIT - I

- 1 a. Draw the basic operational amplifier circuit. Explain. 7
- b. A 741 op-amp is used in a non-inverting amplifier with a voltage gain of 50. Calculate the typical output voltage that would result from a common mode input with a peak level of 100 mV. 6
- c. Sketch an illustration to show the effect of operational amplifier slew rate. Explain state a typical op-amp slew rate. 7
- 2 a. Design an inverting amplifier using 741 op-amp, the voltage gain is to be 50 and the output voltage amplitude is to be 2.5 V. 7
- b. Design an inverting summing amplifier to give the direct sum of two inputs which each range from 0.1 V to 1 V. Use 741 op-amp. 6
- c. Sketch the circuit of a capacitor-coupled non-inverting amplifier. Explain the circuit operation. 7

### UNIT - II

- 3 a. Discuss the upper cutoff frequency of an op-amp circuit and show how the cut-off frequency can be set for inverting and non-inverting amplifier? 10
- b. Explain operational amplifier circuit stability and show how feedback in an inverting amplifier can produce instability? Explain the conditions necessary for oscillations to occur in an op-amp circuit. 10
- 4 a. Explain the following frequency compensation methods : 10
- i) Phase-log            ii) Phase-leaf            iii) Miller-effect.
- b. Calculate the slew rate-limited cutoff frequency for a voltage follower circuit using a 741 op-amp, if the peak of sine wave output is to be 5 V. Determine the maximum peak value of the sinusoidal output voltage that will allow the 741 voltage follower circuit to operate at the 800 kHz unity-gain cut-off frequency. 4
- c. List the precautions that should be observed for operational amplifier circuit stability. 6

**UNIT - III**

- 5 a. Sketch the circuit of a low-resistance voltage source using an op-amp as a bipolar transistor. Show how a Zener diode is used to determine the output voltage? Explain. 7
- b. Show how current to voltage converter should be modified to function as a current amplifier/attenuator with a ground load? Explain the operation of the amplifier/attenuator and derive an equation for current gain. 7
- c. Design a non saturating precision half-wave rectifier to produce a 2 V peak output from a sine wave input with a peak value of 0.5 V and frequency of 1 MHz. Use a bipolar op-amp with a supply voltage of  $\pm 15$  V. 6
- 6 a. A  $\pm 5$  V, 10 kHz square wave from a signal source with a resistance of  $100 \Omega$  is to have its positive peak clamped precisely at ground level. Tilt on the output is not to exceed 1% of the peak amplitude of the wave. Design a suitable op-amp circuit. Use a supply of  $\pm 12$  V. 8
- b. Explain voltage follower type peak detector circuit operation. 8
- c. What is sample and hold circuit? Write the waveform for the same. 4

**UNIT - IV**

- 7 a. With circuit diagram and wave form, describe the working principle of triangular/rectangular wave generator. 10
- b. Draw the circuit of a Wein bridge oscillator. Sketch the output and feedback voltage waveform and explain the circuit operation. 10
- 8 a. Using a 741 op-amp with a supply of  $\pm 12$  V, design a inverting Schmitt trigger circuit to have trigger points of  $\pm 2$  V. 6
- b. Discuss the design process for an op-amp monostable multivibrator and write the equations for calculating each component value. 8
- c. Explain how the filters are classified? 6

**UNIT - V**

- 9 a. Describe the operation of op-amp series voltage regulator. 10
- b. Explain the working operation of 723 general purpose regulators. 10
- 10 a. What is PLL? Explain. 7
- b. Describe the working principal of VCO. 7
- c. Explain the operation of A/D converter. 6

\* \* \* \*