



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Sixth Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; June - 2017

Analog CMOS VLSI Design

Time: 3 hrs

Max. Marks: 100

Note: i) Answer **FIVE** full questions, selecting **ONE** full question from each unit.

ii) Assume missing data suitably.

UNIT - I

1. a. Starting from fundamentals derive the equation for drain current of MOS device. Modify the equation for the device operating in triode region and saturation region. 8
- b. Write a note on body effect. 4
- c. For a common source stage with source degeneration, obtain the expression for A_V taking body effect and channel length modulation into account. 8
2. a. For a source follower, obtain the expression for A_V using large signal model. Verify the result using small signal model. 10
- b. For a common gate amplifier derive the expression for A_V taking body effect, channel length modulation and input source resistance into account. 10

UNIT - II

3. a. Using the quantitative approach obtain the expression for voltage gain of a differential pair. 10
- b. Discuss the common mode response of a differential amplifier : 10
 - i) In the presence of resistor mismatch
 - ii) With finite tail capacitance.
4. a. For a differential amplifier with current mirror as the load, obtain the expression for A_V . 10
- b. Discuss the operation of cascade current mirror. 10

UNIT - III

5. a. Discuss the operation of circuit that provides supply-independent current. Show that

$$I_{out} = \frac{2}{M_n C_{ox} \left(\frac{W}{L}\right)_N} \cdot \frac{1}{R_s^2} \left[1 - \frac{1}{\sqrt{k}} \right]^2 \quad 10$$

Also discuss how startup problem is eliminated?

- b. Discuss the generation of temperature independent voltage. How the effect of Op-Amp off-set is reduced? 10
6. a. For a unity gain sampler operating in amplification mode, obtain the expression for $\frac{V_o(s)}{V_i(s)}$ and τ_{amp} . 10

b. Write note on the following :

- i) Switched-Capacitor integrator 10
- ii) Switched-Capacitor common mode feedback.

UNIT - IV

- 7 a. For a three stage ring oscillator, obtain the expression for frequency of oscillations and minimum gain for sustained oscillations. Plot the poles for $0 < A_0 < 2$, $A_0 = 2$ and $A_0 > 2$. 10
- b. For a Colpitts oscillator, obtain the expression for frequency of oscillations and minimum gain for sustained oscillator. 10
- 8a. Discuss two methods to generate negative resistance that can be used in oscillator circuit. 10
- b. What is VCO? Briefly explain the important performance parameters of VCO. 10

UNIT - V

- 9 a. Discuss the response of PLL to frequency step and phase step. 10
- b. For a type-I PLL obtain the expression for closed loop transfer function obtain the response for step input when the PLL is under damped. 10
- 10a. Obtain the linear mixer of charge pump PLL and discuss. 10
- b. Discuss any two applications of PLL. 10

* * * *