



**P.E.S. College of Engineering, Mandya - 571 401**

(An Autonomous Institution affiliated to VTU, Belagavi)

**Fourth Semester, B.E. - Electrical and Electronics Engineering**

**Semester End Examination; June - 2017**

**Network Analysis - II**

Time: 3 hrs

Max. Marks: 100


Note: Answer FIVE full questions, selecting ONE full question from each unit.

**UNIT - I**

1 a. What do you mean by initial conditions in electrical networks and what is the purpose of determining them? 6

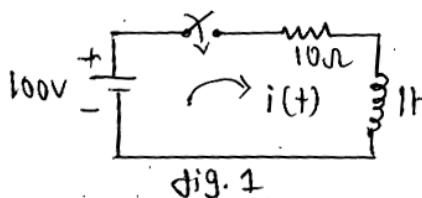
b. In the given network of Fig.1, the switch is closed at  $t = 0$ , with zero current in inductor. Find;

$i, \frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0+$ .




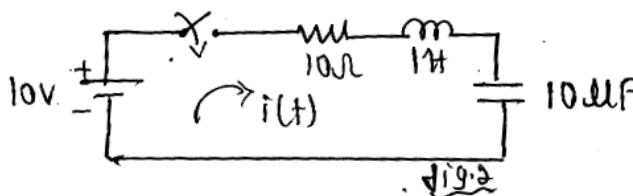c. In the network shown in Fig.2 the switch is closed. Assuming all initial conditions are zero.


Find  $i, \frac{di}{dt}, \frac{d^2i}{dt^2}$  at  $t = 0+$ .



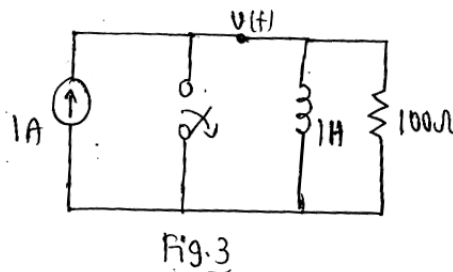2 a. In the network shown in Fig. 3, at  $t = 0$ , the switch is opened. Calculate  $v, \frac{dv}{dt}, \frac{d^2v}{dt^2}$  at  $t = 0+$ .



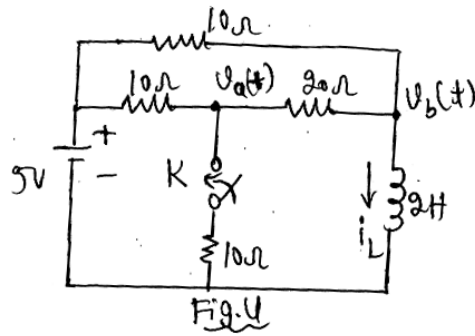b. In the network shown in Fig 4. a steady state is reached with the switch 'k' open. At  $t = 0$ , the switch is closed. For the elemental values given, determine the value of  $V_a(0-)$  and  $V_a(0+)$  and  $V_b(0+)$ . 10



**UNIT - II**

3 a. Clearly discuss the following functions :

- (i) Step function            (ii) Ramp function            (iii) Gate function.


6

b. Sketch the waveforms for the given functions :

- (i)  $t u(t-T)$             (ii)  $(t-T) u(t)$             (iii)  $\sin(\omega t - T/4) u(t - T/4)$ .

6

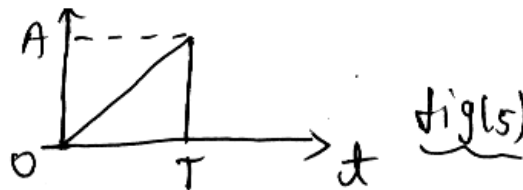c. Obtain the Laplace transform of saw tooth waveform shown in Fig. (5)




8

4 a. Show that the Laplace transform of a train of periodic waveforms with a period 'T' is given by

$$\frac{F_1(S)}{1 - e^{-TS}} = F(S) \text{ where } F_1(S) = L\{f_1(t)\}.$$

10

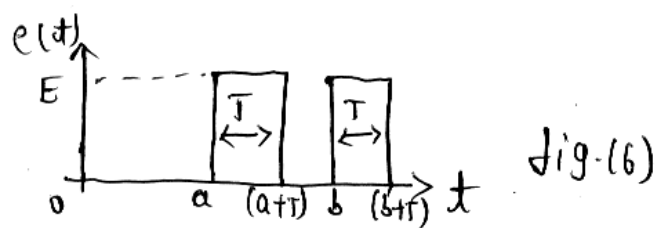
b. Find the Laplace transform of a pair of rectangular pulses each of duration 'T' Sec shown in Fig. (6).



10

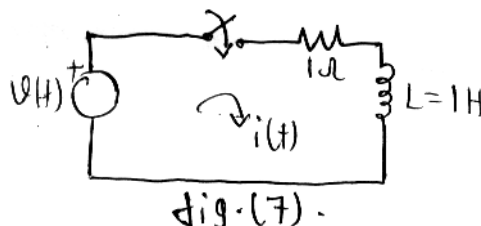
**UNIT - III**

5 a. At  $t = 0$ , unit pulse voltage of unit width is applied to series RL circuit as shown in Fig. (7), obtain an expression for  $i(t)$ ,  $v(t) = u(t) - u(t-1)$ .



10

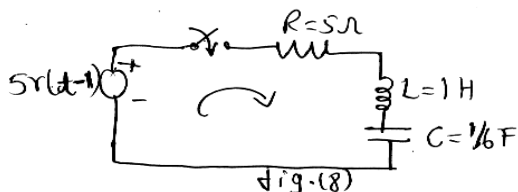- b. For the network shown in Fig. (8). Find  $i(t)$  when the switch is closed at  $t = 0$  with zero initial conditions.




10

6. a. State and prove Convolution theorem. 10  
 b. Calculate the initial value of the current using the initial value theorem given that the Laplace transformation of current is  $I(S) = \frac{2S+5}{(S+1)(S+2)}$ , find  $i(0+)$ . Also verify  $i(0+)$  from time response. Also calculate  $i(t)$  at  $t = 2$  sec. 10

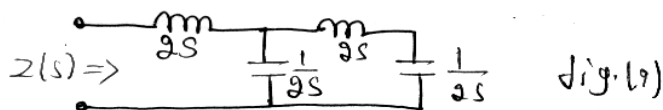
**UNIT - IV**

- 7 a. Determine the driving point impedance function of the network shown in Fig. (9) 6  
 b. Obtain the pole-zero plot of the following functions : 6  
 (i)  $F(S) = \frac{S(S+2)}{S^2+2S+2}$  (ii)  $F(S) = \frac{S(S+2)}{(S+1)(S+3)}$   
 c. Plot the following on the pole-zero plot and determine the time response of each of the individual poles, assuming the response is current (i)  $S_1 = 0$  (ii)  $S_2 = -1$  (iii)  $S_3 = -2$ . 8



8

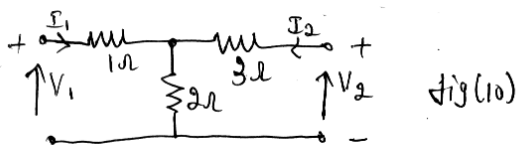- 8 a. Obtain the expression of Z parameters in terms of ABCD parameters. 10  
 b. Find the Y-parameters for the network shown in Fig. (10)



10

**UNIT - V**

- 9 a. Test whether the polynomial  $P(S) = 2S^4 + 5S^3 + 6S^2 + 3S + 1$  is Hurwitz or not. 10  
 b. Just whether the function  $F(S) = \frac{S(S+3)(S+5)}{(S+1)(S+4)}$  is PR function or not. 10  
 10 a. Realize the Foster I & II form of the following impedance function :  $F(S) = \frac{4(S^2+1)(S^2+9)}{S(S^2+4)}$  10  
 b. Realize the cover II and I form of the following Impedance function :  $Z(S) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s}$  10