



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Eighth Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; June - 2017

HVDC Power Transmission

Time: 3 hrs

Max. Marks: 100

Note: Answer *FIVE* full questions, selecting *ONE* full question from each unit.

UNIT - I

- | | | |
|------|-----------------------------------------------------------------------------------------------------------------------------|---|
| 1 a. | Compare HVAC and HVDC transmission based on the economics of power transmission. | 6 |
| | b. Draw and explain the different types of HVDC links. | 6 |
| | c. Illustrate the choice of voltage level for a fixed power transfer for both point to point and back to back HVDC systems. | 8 |
| 2 a. | Compare HVAC and HVDC transmission based on voltage control and problems of AC interconnection. | 6 |
| | b. Draw and explain the different configuration for asynchronous interconnection of HVDC systems. | 6 |
| | c. Sketch schematic diagram of a typical HVDC converter station and briefly explain. | 8 |

UNIT - II

- | | | |
|------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----|
| 3 a. | What is Graetz circuit? Comment on the choice of best configuration. | 6 |
| | b. Perform the analysis of Graetz circuit neglecting the overlap condition, derive the Average dc output voltage with necessary voltage waveforms at $\alpha = 0^\circ$ and 45° . | 14 |
| 4 a. | Discuss the turn-on and turn-off switching characteristics of Thyristor. | 10 |
| | b. Draw the circuit and explain how two 3 ϕ one way circuit combined to form a six pulse circuit? | 10 |

UNIT - III

- | | | |
|------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------|----|
| 5 a. | Derive and explain the following with reference to the converter performance : | |
| | (i) Valve Utilization Factor-VUF (ii) Transformer Utilization Factor-(TUF). | 8 |
| | b. Compute VUF for the following converter configuration : | |
| | (i) $q = 2, r = 1, s = 3$ (ii) $q = 3, r = 2, s = 1$ | 6 |
| | Select the best configuration and justify. | |
| | c. What is overlap angle? Draw the equivalent circuit of a bridge converter. | 6 |
| 6 a. | Analyse the Graetz circuit with overlap condition. Obtain the expression of direct current I_d . | 10 |
| | b. A 3 ϕ , 6 pulse rectifier is fed from a transformer with nominal rating of 220 kV/110 kV | |
| | (i) Determine the DC output voltage when $\alpha = 20^\circ$ and $u = 18^\circ$ | 10 |
| | (ii) If the direct current delivered by the rectifier is 2000 A, calculate the effective commutating reactance, power factor and fundamental component of AC current. | |

UNIT - IV

- 7 a. Outline the desired features of HVDC power control. 8
- b. With the help of schematic diagram, explain constant-current regulator for the control of HVDC converter. 12
- 8 a. With the help of equivalent circuit of dc transmission in steady state condition, explain the basic means of HVDC power control. 8
- b. Contrast the constant current and constant voltage method of HVDC power control. 6
- c. Discuss the role of Tap-changer control in HVDC power control. 6

UNIT - V

- 9 a. Discuss the procedure of control for fault clearing and reenergization of line. 7
- b. Explain the causes and consequences of uncharacteristic harmonics. 6
- c. What are the means of reducing harmonics? Briefly explain. 7
- 10 a. Discuss the following basic types-converter faults : 10
- (i) Arc through (ii) Misfire (iii) Commutation failure.
- b. Outline the important functions of smoothing reactor. 3
- c. Find the inductance of the dc reactor required to prevent consequent commutation failures in the inverter described below :
- | | | |
|------------------------------------|--------------|---|
| Number of bridges per pole | : 2 | |
| Rated voltage per bridge | : 200 kV | |
| Rated current (I_{dn}) | : 1.86 kA | 7 |
| I_{s2} | : 10.0 kA | |
| Frequency | : 60 Hz | |
| Normal extinction angle γ_n | : 16° | |
| Min extinction angle γ_m | : 8° | |

* * * *