



## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

**Second Semester, M. Tech – VLSI Design and Embedded System (MECE)**

**Semester End Examination; June - 2017**

**Design of Analog and Mixed Mode VLSI Circuits**

*Time: 3 hrs*

*Max. Marks: 100*

*Note: Answer FIVE full questions, selecting ONE full question from each unit.*

### UNIT - I

- 1 a. Discuss the important aspects of MOSFET-model and hence, construct the complete circuit model of a MOSFET for small signal operation, considering device capacitances, channel length modulation and body effect. 8
- b. Describe the operation of source follower with MOSFET as current source load, both by excluding and including body effect. 7
- c. For the common gate MOSFET amplifier with resistive load  $R_D$ , prove that  $\frac{\partial V_{out}}{\partial V_{in}} = g_m (1 + \eta) R_D$  with the usual notations. Draw the input-output characteristics. 5
- 2 a. Draw the cascode stage circuit and its equivalent circuit as well as input-output characteristics, and discuss the operation and hence, show the extension of cascode structure to two or more devices to get higher output impedance. 12
- b. Sketch the separate circuits of folded cascode with biasing and N-MOSFET input and describe their operations. 8

### UNIT - II

- 3 a. For a MOS differential pair circuit with two separate inputs, derive the expression for differential drain current  $(I_{D_1} - I_{D_2})$ . 8
- b. Sketch the circuit diagram of differential pair sensing CM-input and develop the expression for common mode to differential mode conversion  $A_{CM-DM}$ . 12
- 4 a. How is cascode current mirror realized using cascode current source? Describe with the help of circuit diagrams. 8
- b. Draw a MOS differential pair circuit with active current-mirror sensing a common mode change and develop the expression for CMRR. 12

### UNIT - III

- 5 a. Sketch the circuit of source follower with output capacitance and its corresponding high frequency equivalent circuit and derive the expression for the transfer function. 10

- b. Draw the source follower circuit showing noise sources and derive the expression for the input-referred noise voltage. 10
- 6 a. Neglecting the body effect ( $\gamma = 0$ ), calculate the transfer function ( $V_{out} / V_{in}$ ) for the simplified cascode stage shown in Fig. Q 6(a). 10

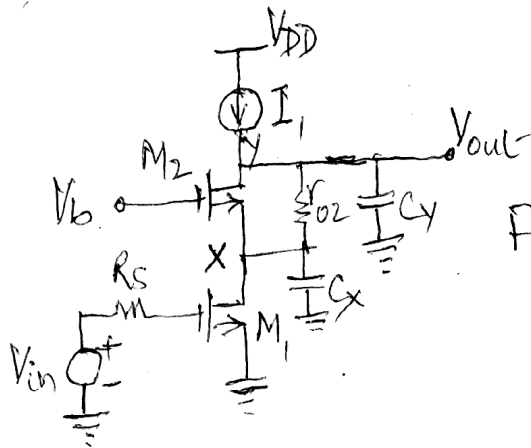


Fig Q 6(a) Simplified cascode stage at high frequencies.

- b. Show that the input noise voltage squared of differential pair is twice the input noise voltage squared of a common-source stage for a differential pair circuit including input-referred noise sources. 10

**UNIT - IV**

- 7 a. Sketch the circuit implementation of a two-stage OP-AMP and describe the functions of each stage. 6
- b. Discuss the various methods of boosting the gain in differential cascode. 6
- c. Discuss the response of a linear OP-AMP to a step input and derive the expression for the output voltage. Draw the relevant circuit diagram and the corresponding waveforms. 8
- 8 a. For a two-stage OP-AMP, derive the expression for the input-referred thermal noise voltage. 10
- b. For a differential pair with active current mirror load and capacitive feedback, develop the expression for low frequency PSRR. 10

**UNIT - V**

- 9 a. Explain the basic principles of VCO and the seven important performance parameters. 10
- b. Sketch the cross-coupled oscillator circuit with tail current source and explain how the problems of conventional oscillators are overcome? 10
- 10 a. Describe the problem of lock acquisition and its solution in type-I PLL. 7
- b. With circuit diagram, explain the methods to establish supply independent currents in order to realise current references. 8
- c. Explain the techniques to derive the temperature independent references. 5