



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belgaum)

Third Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec - 2016/Jan - 2017

Network Analysis

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.


UNIT - I

- 1 a. Draw a network which will have the following loop equations and determine V_2 such that there will be zero current through 4Ω resistor.

$$\begin{bmatrix} 5 + j2 & -j2 & 0 \\ -j2 & 4 & j2 \\ 0 & j2 & (2 - j2) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \angle 0^\circ \\ 0 \\ -V_2 \end{bmatrix}$$


10

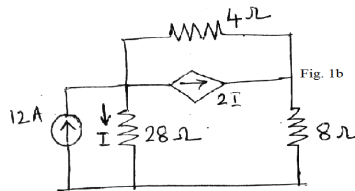- b. Use mesh analysis to evaluate the current I in the circuit shown in Fig. 1b.




5

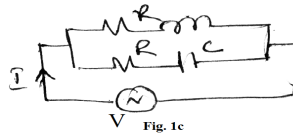- c. For a parallel circuit shown in Fig. 1C, obtain an expression for resonant frequency. Plot the graph of I versus frequency.



5

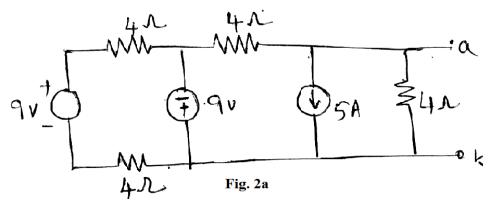- 2 a. Using source transformation method, convert the circuit shown in Fig. 2a into a single current source in parallel with a resistor.



5

- b. Find V_a , V_b and I_{ab} in the Fig. 2b by Y - Δ transformation.

10

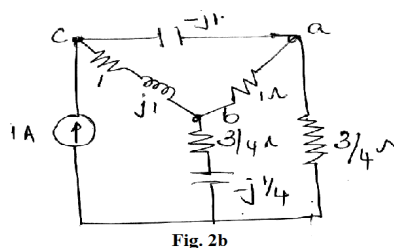



Fig. 2b

- c. Obtain an expression for frequency (f_L) in terms of circuit components in a series resonant circuit when the voltage across inductor V_L reaches its peak. Plot the variation of voltage across R, L and C as frequency varies.

5

UNIT - II

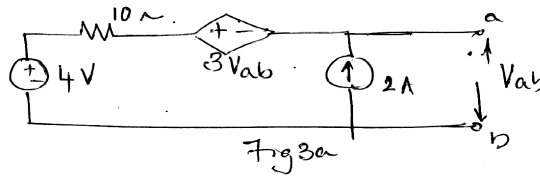3 a. Find the terminal voltage V_{ab} for the circuit shown in Fig. 3a using superposition theorem.




6

b. State and prove maximum power transfer theorem for an AC circuit when both resistance and reactance parameters of the load are variable.


7

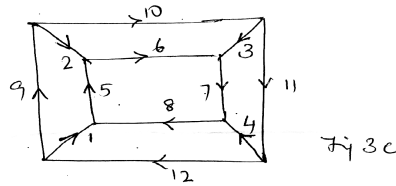c. For the graph shown in Fig. 3c, select a tree and write the cut set schedule. Obtain there from the equation giving branch voltages in terms of tree branch voltages.




7

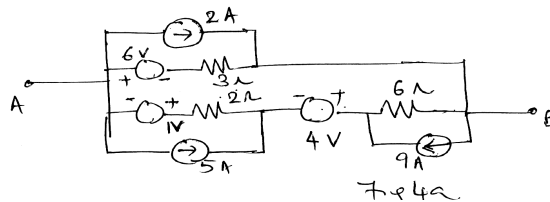4 a. Obtain the Thevenin's equivalent circuits across terminals A and B for the circuit shown in Fig. 4a.



10

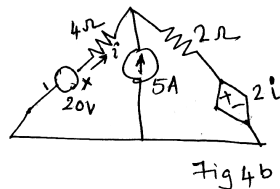b. For the circuit shown in Fig. 4b, find the current i , using super position theorem.



5

c. What is duality of electrical network? Explain with an example.

5

UNIT - III

5 a. For the circuit shown in Fig 5a. switch is closed at $t = 0$,

find, $i_1(0+)$, $i_2(0+)$, $\frac{di_1}{dt}(0+)$, $\frac{di_2}{dt}(0+)$, $\frac{d^2i_1}{dt^2}(0+)$ and $\frac{d^2i_2}{dt^2}(0+)$


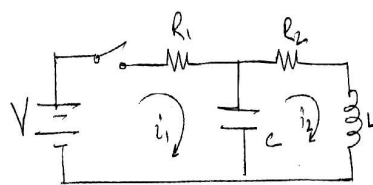


Fig. 5a


10

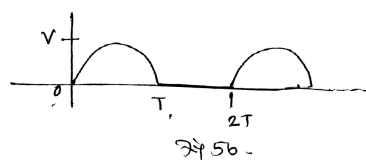b. Find the Laplace transform of a half wave rectified sine wave show in Fig. 5b.




6

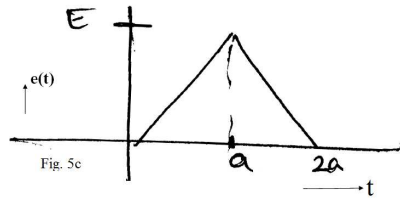c. Obtain an expression $e(t)$ for the wave fin shown in Fig. 5c.




4

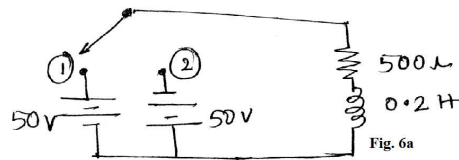6 a. For the circuit shown in Fig 6a the switch is closed to position (1) at $t = 0$, then moved to position (2) after 1 m sec. Find the time at which the current in zero and reversing the direction.




10

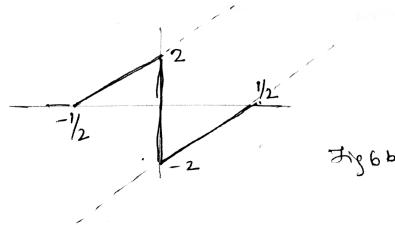b. Find the Laplace transform of the waveform shown in Fig. 6b.



6

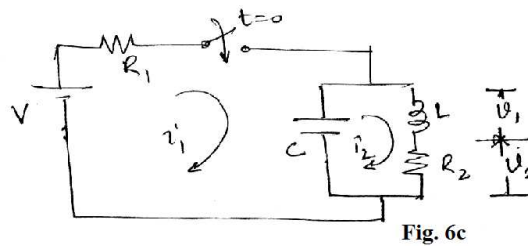
c. Find V_1 and V_2 at $t = 0+$ and $t = \infty$, for the circuit shown in Fig. 6c.



4


UNIT - IV

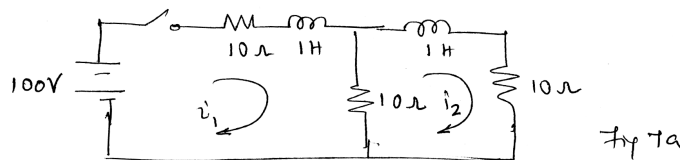7 a. In the circuit shown in Fig. 7a, switch is closed at $t = 0$. Obtain an expression $i_2(t)$ using Laplace transformation method.



10

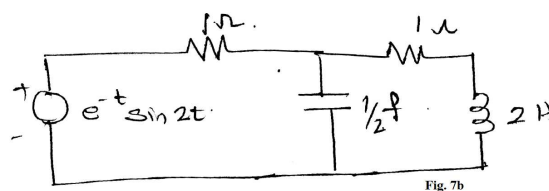b. In the circuit shown in Fig. 7b. obtain an expression for $I(S) = \frac{V(S)}{Z(S)}$




6

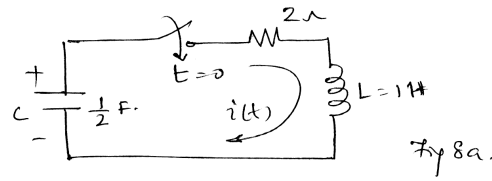c. Using convolution theorem find response to an excitation of $v(t) = e^{-2t}$ given that the impulse response of the network is $h(t) = \delta(t) - e^{-3t}$.


4

- 8 a. Obtain an expression for $i(t)$ using Laplace transformation method. Assume capacitor has charged to 1 V at $t = (0^-)$ (refer Fig. 8a)



10

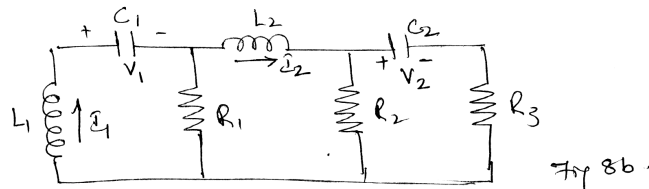- b. Write the transformed network for the circuit shown in Fig. 8b. Initial currents and voltages are present at time $t = 0$.



6

- c. State and explain Duhamel's superposition theorem.

4

UNIT - V

- 9 a. Plot the time response for the following :

- i) Complex conjugate poles on left half of S plane
- ii) A simple real pole on the left half of S plane
- iii) Complex conjugate poles on right half of S plane.


8

- b. Obtain the following:

- i) h parameters in terms of ABCD parameter
- ii) h parameter in term of Y parameter.

8

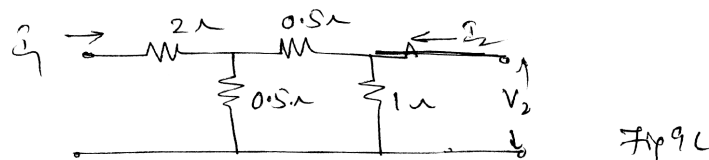- c. Find Y parameter of the following resistance network shown in Fig. 9C.



4

- 10 a. Draw the second order response of the system if,

- i) $\delta = 0$ (no damping)
- ii) $0 < \delta < 1$ (damping < 1)
- iii) $\delta > 1$ (damping > 1)
- iv) $\delta = 1$ (critically damped)


8

- b. Write the networks which are equivalent to the general two port network in terms of,

- i) Z- parameter
- ii) h - parameters

8

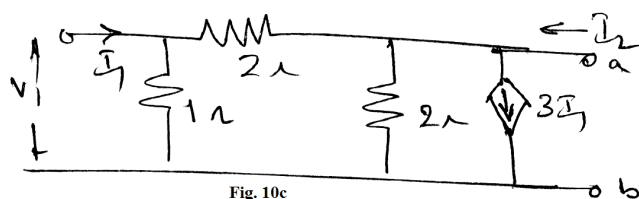- c. Find the Y parameter for the network shown in Fig. 10 C.



4