



P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belagavi)
I/II Semester, B.E. - Semester End Examination; May/June - 2018
Electronic Devices and Communication
(Common to All Branches)

Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

UNIT - I

- 1 a. With circuit diagram and waveforms, explain the working of center-tapped transformer full wave rectifier. 8
- b. What is the need of DC load line? Explain the procedure to draw DC load line and Q point for series diode configuration. 8
- c. Draw and explain the V-I characteristics of Zener diode. 4
- 2 a. Describe the operation of photodiode with biasing circuit and characteristics. 8
- b. Discuss the regulating action of Zener diode with related equations and circuit diagram. 8
- c. Explain the operation of reflective field effect LCD. 4

UNIT - II

- 3 a. With a neat diagram, explain the construction and characteristics of MESFETs. 7
- b. Discuss the process of channel formation in the *N*-channel enhancement MOSFET and draw its drain characteristics. 8
- c. Write the advantages of VMOS FET's over MOSFET's. 5
- 4 a. State and explain Barkhausen criterion for oscillation. 5
- b. Describe the working of FET phase shift oscillator with neat circuit diagram and write equation for frequency of oscillation. 7
- c. Analyze the voltage divider biasing arrangement for *N*-channel enhancement MOSFET along with circuit diagram and related equations. 8

UNIT - III

- 5 a. Discuss the concept of virtual ground in an Op-amp. Write the circuit diagram and output voltage equation of Op-amp inverting and non-inverting amplifier. 10
- b. Define the following parameters of Op-amp :
- i) Slew rate
- ii) CMRR 6
- iii) Input offset voltage
- c. Write the Op-amp circuit and output voltage equation for :
- i) Integrator 4
- ii) Voltage follower

- 6 a. With neat circuit diagram, explain the working of voltage controlled voltage source and current controlled current source. 8
- b. Design an Op-amp summing amplifier to obtain an output voltage $V_0 = - [0.5V_1 + 0.8V_2 + 2V_3]$. Where V_1, V_2, V_3 are inputs. Assume $R_f = 10 \text{ k}\Omega$. 6
- c. Explain the low pass filter and high pass filter along with circuit diagram and frequency response. 6

UNIT - IV

- 7 a. Briefly explain the features of 8-bit, 16-bit and 32-bit microcontroller. 6
- b. Draw the block diagram of microcontroller and write the fundamental differences between microprocessor and microcontroller. 8
- c. Compute the following conversion : 6
- i) $(847.951)_{10} = ()_2 = ()_{16}$ ii) $(A2C)_{16} = ()_{10} = ()_2$
- 8 a. Write the bit format of TMOD register and explain each bit. 6
- b. With a neat diagram, explain the operation of port-1 pin of 8051 μC . 7
- c. Explain the 8051 μC oscillator circuit and timing with a neat diagram. 7

UNIT - V

- 9 a. Explain basic cellular system along with block diagram. 6
- b. What is Duplexing? Explain Frequency Division Duplexing and Time Division Duplexing. 7
- c. Describe the operation of cordless telephone system. 7
- 10a. Describe the frequency management system for the Advanced Mobile Telephone System (AMPS). 8
- b. List the advantages of GSM. 5
- c. Write the advantages and disadvantages of Ad-hoc and infrastructure network. 7

* * * *