



**P.E.S. College of Engineering, Mandya - 571 401**

(An Autonomous Institution affiliated to VTU, Belagavi)

**Second Semester, B.E. - Semester End Examination; May / June - 2018**

**Basic Electronics  
(Common to All Branches)**


Time: 3 hrs

Max. Marks: 100

Note: Answer FIVE full questions, selecting ONE full question from each unit.

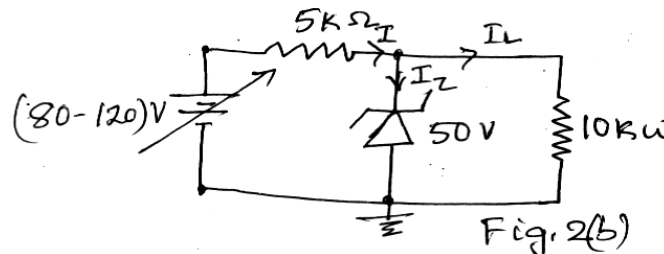**UNIT - I**


- 1 a. With the help of circuit diagram, explain different types of diode configurations. 6
- b. Explain the working of bridge rectifier. 8
- c. Describe solar cells with diagrams. 6
- 2 a. Consider a full-wave rectifier with capacitor filter. Derive an expression for ripple factor. 8
- b. For the circuit shown in Fig. 2(b), find maximum and minimum value of Zener diode current.



- c. Briefly explain transmissive and reflective field effect LCD with no applied bias conditions. 6

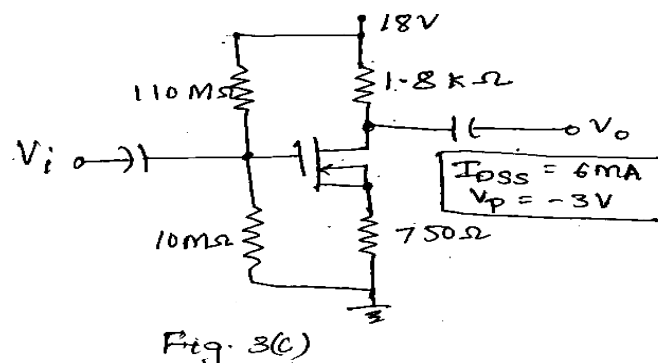**UNIT - II**

- 3 a. With the help of neat diagram, explain the construction and working principal of enhancement type MOSFET. 10
- b. Distinguish between VMOS and CMOS. 4
- c. For the N-channel depletion type MOSFET of Fig. 3(c). Determine;
  - (i)  $V_{GSQ}$  and  $I_{DQ}$
  - (ii)  $V_{DS}$



- 4 a. Derive an expression for input impedance, output impedance and voltage gain of E-MOSFET voltage-divider configuration. 8
- b. With neat diagram and necessary equation, explain FET phase-shift oscillator. 6
- c. Define oscillator. What are the conditions required to get sustained oscillation? 6

**UNIT - III**

- 5 a. Derive an expression for output voltage equation of the following :
  - (i) Summer 10
  - (ii) Integrator
- b. Discuss the offset-currents and voltages of an Op-amp. 10
- 6 a. With a neat circuit, explain voltage controlled voltage source and current controlled current source. 8
- b. What is meant by filter? Explain first order low-pass and high pass filter with frequency response. 8
- c. Determine the output voltage of an Op-amp for input voltages of  $V_{i1} = 150 \mu\text{V}$  and  $V_{i2} = 140 \mu\text{V}$  and the amplifier has a differential gain of  $A_d = 4000$ . The value of CMRR is 100. 4

**UNIT - IV**

- 7 a. Prove De Morgan's theorem. 6
- b. Compute;
  - (I)  $(1010.1100)_2 = \text{-----} (10) = \text{-----} (16)$
  - (II)  $(D7.51A)_{16} = \text{-----} (10) = \text{-----} (2)$  10
  - (III) Perform binary subtraction
    - (i)  $\begin{array}{r} 50 \\ -20 \\ \hline \end{array}$       (ii)  $\begin{array}{r} 30 \\ -70 \\ \hline \end{array}$
- c. Simplify:  $A + \overline{AB} + ABC = (A + B)$ . 4
- 8 a. With the help of a circuit diagram and truth table, explain the working of full adder. 6
- b. Implement and explain 3-to-8 decoder using basic gates. 8
- c. Realise the following :
  - (i) EXOR using NAND 6
  - (ii) OR using NOR

**UNIT - V**

- 9 a. With the help of relevant sketch, explain amplitude modulation. 8
- b. Briefly explain the operation of super heterodyne receiver. 7
- c. Illustrate the basic topology of a typical switched telephone network. 5
- 10 a. Explain the following :
  - (i) Piezo-electric transducer 8
  - (ii) Photo-electric transducer
- b. Explain the working of Linear Variable Differential Transducer (LVDT). 7
- c. Distinguish between passive and active transducers. 5