



--	--	--	--	--	--	--	--	--	--

P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Second Semester, B.E. - Semester End Examination; May / June - 2019

Basic Electronics (Common to All Branches)


Time: 3 hrs

Max. Marks: 100

Note: Answer **FIVE** full questions, selecting **ONE** full question from each unit.

UNIT - I

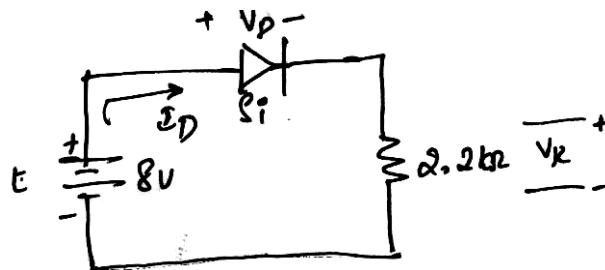- With the help of a neat circuit diagram and appropriate waveform, explain the operation of a half wave rectifier circuit. 6
- Define Q-point. For a series diode configuration, explain the construction of DC load line analysis and optimum Q-point selection using circuit diagram and characteristics. 9
- For the series diode configuration shown in below figure, determine V_D , V_R and I_D . 5



- Explain the basic block diagram of a power supply. 6
- Analyze the working of Zener diode as voltage regulator with fixed V_I and fixed R_L . 6
- Explain the operation of a capacitor filter using centre tapped full wave rectifier circuit. Calculate the ripple of a capacitor filter for a peak rectified voltage of 30 V. If capacitor $C = 50 \mu\text{F}$ and a load current of 50 mA. 8

UNIT - II

- Describe the construction of n -channel depletion type MOSFET. 6
- Illustrate the working of CMOS inverter along with circuit diagram. 6
- Explain the following in brief : 8
 - MOSFET handling
 - V-MOS
- With neat circuit diagram, explain the working of FET phase shift oscillator. Write the equation for frequency of oscillation. 6
- Explain E-MOSFET voltage divider configuration along with equivalent circuits. 6
- Describe the operation and characteristics of p -channel enhancement MOSFET with necessary diagrams. 8

UNIT - III

- a. With the help of neat circuit diagram, derive the expression for output voltage and gain of an inverting Op-amp. Write the equivalent diagram. 8
- b. Explain input offset voltage with necessary diagrams. 6
- c. Design an Op-amp summing amplifier for the following set of voltage and resistor : 6
 $V_1 = 1 \text{ V}$, $V_2 = 2 \text{ V}$, $V_3 = 3 \text{ V}$; $R_1 = 500 \text{ k}\Omega$, $R_2 = 1 \text{ M}\Omega$, $R_3 = 1 \text{ M}\Omega$. Use $R_f = 1 \text{ M}\Omega$.
- a. Describe following types of Op-amp controlled sources :
 i) Voltage controlled voltage source 8
 ii) Current controlled voltage source
- b. Explain the following Frequency parameters : 12
 i) Gain Bandwidth ii) Slew rate iii) Maximum signal frequency

UNIT - IV

- a. Realize the following circuits/ gates :
 i) AND gate using NOR gate 6
 ii) XOR gate using NAND gate
- b. Prove De-Morgan's theorem with an example. 6
- c. Compute the following :
 $(57345)_{10} = ()_{16} = ()_2$ 8
 $(47.5434)_{16} = ()_{10} = ()_8$
 $(11010101.11)_2 = ()_{10} = ()_{16}$
- a. With the help of circuit diagram and truth table, explain the working of a full adder. 8
- b. Explain the operation of 8:1 MUX. 6
- c. Compute the following :
 i) $(110.101)_2 - (100.101)_2$ using 1's complement method 6
 ii) $(101.101)_2 - (100.100)_2$ using 2's complement method

UNIT - V

- a. With neat diagram, explain the elements of a communication system. 6
- b. Explain the operation of super heterodyne receiver with necessary block diagram . 8
- c. Describe the working of monochrome cathode ray tube with neat figure. 6
- a. Distinguish between Amplitude Modulation and Frequency Modulation . 8
- b. Describe the working of Piezoelectric transducer . 6
- c. Describe the working of Hall-effect transducer with neat figure. 6

* * * *