



P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belagavi)
I Semester, B.E. – Electronics & Communication Engineering
Basic Electronics


Time: 3 hrs

Max. Marks: 100


Note: Answer FIVE full questions, selecting ONE full question from each unit

UNIT - I

- 1 a. Compare Half Wave Rectifier(HWR), Full wave Rectifier(FWR) and Bridge rectifier on the basis of i) Ripple factor ii) Efficiency iii) DC output voltage iv) Transformer utility 6
- b. With the help of neat diagram & associated waveforms, explain the working of full wave rectifier with center tapped transformer. 8
- c. Two diodes are connected as shown in fig. Q 1(c). Determine the currents I_1 , I_2 & I_{D_2} 6

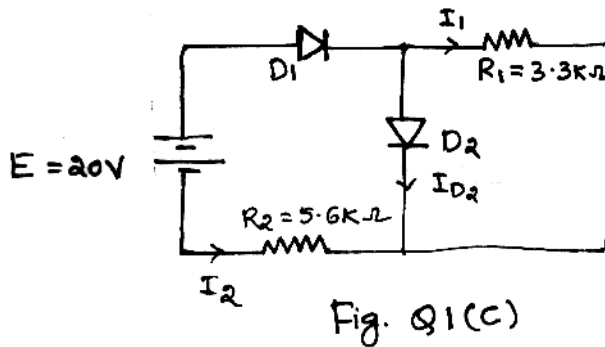

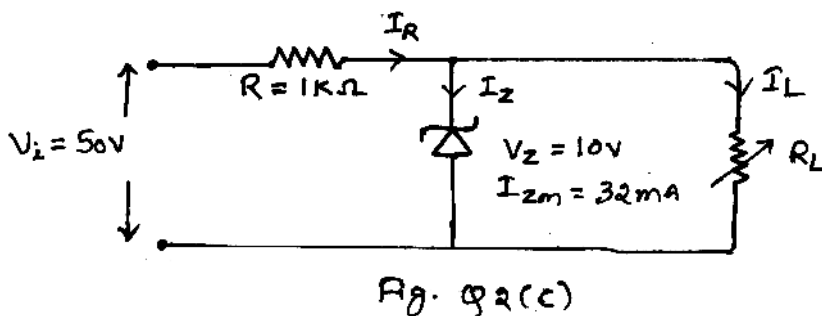- 2 a. Mention any two differences between Diode & IR emitter? With the help of a neat diagram explain IR emitter diode. 8
- b. Derive an expression for the ripple factor of a full wave rectifier with capacitor filter. 6
- c. For the network of fig. Q2(c), determine the range of R_L & T_L that will result in V_{RL} being maintained by 10V. 6



UNIT - II

- 3 a. With the help of a neat diagram explain the construction & operation N-channel enhancement type MOSFET. 6
- b. Mention the important characteristics CMOS MOSFET arrangement with a diagram explain CMOS inverter. 6
- c. If an average threshold voltage $V_{GS(th)}=3V$ & $V_{GS(on)}=10V$, $I_{D(on)} =3mA$. Sketch the transfer characteristics of N-channel enhancement MOSFET, for $V_{GS}=5, 8,10,12$ & 14 V. 8

- 4 a. State & explain Barkhausen criterion for sustained oscillation. 5
- b. Draw an AC equivalent network for an amplifier constructed using E-MOSFET drain feedback configuration. 5
- c. For the n-channel depletion-type MOSFET with $R_1=110M\Omega$, $R_2=10M\Omega$, $R_D=1.8k\Omega$, $R_S=750\Omega$, $I_{DSS}=6mA$, $V_p=-3V$ determine
- i) I_{DQ} & V_{GSQ} & draw DC load line
- ii) V_{DS} 8
- iii) For the transfer characteristics use, $I_D = \frac{I_{DSS}}{4} = \frac{6mA}{4} = 1.5mA$
- and $V_{GS} = \frac{V_P}{2} = \frac{-3V}{2} = -1.5V$

UNIT - III

- 5 a. List the properties of an ideal op – amp. 6
- b. Show that maximum frequency of a sinusoidal voltage that results in an undistorted output from an op-amp is given by $f_{max} = \frac{SR}{2\pi V_m}$; SR = Max. Slew rate of op-amp 6
- c. With the help of neat diagram explain how an op-amp can be used as,
- i) Integrator ii) Summing amplifier. 8
- 6 a. Design an adder circuit using op-amp to obtain an output voltage given by $V_0 = -[0.5V_1 + 0.8V_2 + 2V_3]$ 6
- when V_1 , V_2 and V_3 are the inputs.
- b. With the neat circuit diagram explain,
- i) Current controlled voltage source 6
- ii) Current controlled current source.
- c. What is a filter? Mention any 2 differences between active and passive filter. Write the op – amp circuit and frequency response curve of a 1st order active high pass filter. 8

UNIT – IV

- 7 a. Perform the following:
- i) $(725.25)_8 = (?)_{10} = (?)_2$ 5
- ii) $(31C.DE)_{16} = (?)_{10}$
- b. Simplify and realize using basic gates. 10
- i) i) $Y = AB + \bar{A}C + BC$ ii) $Y = C (B + C)(A + B + C)$
- c. Perform binary subtraction using 1s and 2s complement 1010 – 111. 5
- 8 a. With the help of truth table realize X – OR gate using i) Basic gates ii) Nand gates. 8
- b. Implement and explain 4 : 1 multiplexes using basic gate. 6
- c. Realize and implement the given expression using Nor gate only. 6
- $Y = \bar{A}BC + A\bar{B}C + ABC$

UNIT – V

- 9 a. Obtain an expression for the total average power of a sinusoidal AM wave. 8
- b. With a neat block diagram explain the operation of a super heterodyne receiver. 8
- c. Compare AM and FM. 4
- 10 a. Explain the functional Blocks of optical fibre communication. List its advantage and application. 10
- b. Explain LVDT & Capacitive transducers. 10

* * * *