



**P.E.S. College of Engineering, Mandya - 571 401**  
 (An Autonomous Institution affiliated to VTU, Belagavi)  
**Third Semester, B.E. - Computer Science and Engineering**  
**Semester End Examination; Dec. - 2019**  
**Digital Logic Design**

Time: 3 hrs

Max. Marks: 100

**Course Outcomes**


The Students will be able to:

- CO1 - Design simplified logic circuits using Boolean equation minimization techniques.
- CO2 - Design the data processing circuits.
- CO3 - Design memory circuits.
- CO4 - Design shift registers and counters using flip-flops.
- CO5 - Derive state machine models for sequential circuits and write VHDL code for all logic circuits.

**Note:** I) **PART - A** is compulsory. One question for 2 marks from each unit.  
 II) **PART - B:** Answer any **two** sub questions (from a, b, c) for Maximum of 18 marks from each unit.

Q. No.	Questions	Marks
<b>I : PART - A</b>		<b>10</b>

 I a. Get the output for the following circuit shown in fig (I.a.)



- b. Define parity generator and checker. 2
- c. Write the truth table for SR flip-flop. 2
- d. List types of registers. 2
- e. Write VHDL code for 1:4 Multiplexer. 2

<b>II : PART - B</b>		<b>90</b>
----------------------	--	-----------

**UNIT - I** **18**

- 1 a. i) Define Universal gate. Realize basic gates using NOR gate. 9
- ii) Simplify the following Boolean expression : 9  

$$f(A, B, C) = ABC + A\bar{B}C + AB\bar{C} + A$$
- b. Simplify the following Boolean function using k-map : 9
  - i)  $f(p, q, r) = \Pi M(0, 2, 4, 6) + d(1, 3)$
  - ii)  $f(a, b, c, d) = \sum m(1, 3, 7, 11, 15) + d(0, 2, 4)$
  - iii)  $f(a, b, c, d) = \sum m(2, 4, 6, 12, 13) + d(0, 3, 15)$
- c. Using Quine McCluskey method, solve the following Boolean function, 9  

$$F(a, b, c, d) = \sum m(0, 3, 4, 5, 7, 10, 14, 15)$$

**UNIT - II****18**

- 2 a. Implement  $U = ad + b\bar{c} + bd$  using: i) 16:1 MUX ii) 8:1 MUX. 12
- b. i) Implement the following using 3:8 decoder:  
 $f_1(w, x, y, z) = \sum m(0, 1, 3, 4)$  and  $f_2(w, x, y) = \sum m(2, 4, 6, 7)$  12
- ii) Design full adder using two half adders.
- c. Design 3-bit binary to grey code converter using basic gates. 6

**UNIT - III****18**

- 3 a. Implement the following Boolean function using PAL and PLA :  
 i)  $f_1(a, b, c) = \sum m(0, 1, 2, 3, 7)$  9  
 ii)  $f_2(a, b, c) = \sum m(3, 5, 6, 7)$   
 iii)  $f_3(a, b, c) = \sum m(1, 2, 6, 7)$
- b. Convert SR flip flop to JK flip-flop. 9
- c. Define race around conditions. Explain JK Master slave flip-flop with neat logic diagram. 9

**UNIT - IV****18**

- 4 a. Explain Ring counter and Johnson counter with example and logic diagram. 9
- b. Design mod-6 Synchronous Up counter using D flip flop. 9
- c. Design mod-8 Asynchronous counter using JK flip flop. 9

**UNIT - V****18**

- 5 a. Give the ASM chart for vending machine problem and explain the same. 12
- b. Write VHDL code for the following logic circuits:  
 i) 4:2 Encoder 12  
 ii) D flip-flop  
 iii) Full subtractor
- c. Differentiate between Moore model and Mealy model. 6

\* \* \*