



P.E.S. College of Engineering, Mandya - 571 401
 (An Autonomous Institution affiliated to VTU, Belagavi)
Third Semester, B.E. – Computer Science and Engineering
Semester End Examination; Dec. - 2019
Digital Logic Design


Time: 3 hrs

Max. Marks: 100

Note: I) **PART - A** is compulsory. One question for 2 marks from each unit.
 II) **PART - B:** Answer any **two** sub questions (from a, b, c) for Maximum of 18 marks from each unit.

Q. No.	Questions	Marks
I : PART - A		10

- | | | |
|------|--|---|
| I a. | State duality principle with example. | 2 |
| b. | Explain de-multiplexer with the help of block diagram. | 2 |
| c. | Give any two differences between sequential and combinational circuit. | 2 |
| d. | List: i) Types of register ii) Application of shift register. | 2 |
| e. | Give verilog structural code for the following Fig.Q1(e): | 2 |

 

II : PART - B	90
----------------------	-----------

UNIT - I **18**

- | | | |
|------|--|----|
| 1 a. | Give the truth table for the following function and reduce the same using k-map technique.
$F(A, B, C, D) = \Pi M(0,3,4,7,8,10,12,14) + d(2, 6)$ | 6 |
| b. | Define min term, max term, negative logic and positive logic. Simplify the following function using k-map technique and implement using Basic gates
$F(A, B, C, D) = \overline{A}BD + AB\overline{C}D + \overline{A}BD + ABC\overline{D}$ | 12 |
| c. | Simplify the following expression using tabulation method and give the circuit for essential prime implicant.
$F(A, B, C, D) = \sum m(1, 3, 6, 7, 8, 9, 10, 12, 14, 15) + d(11, 13)$ | 12 |

UNIT - II **18**

- | | | |
|------|--|---|
| 2 a. | What is magnitude comparator? Design one bit comparator using basic gates. | 9 |
|------|--|---|

- b. Explain 4-line to 16-line decoder with relevant circuit shows a 3 to 8 decoder and multi-input OR gates, following Boolean expressions can be realized simultaneously,

$$F_1(A, B, C) = \sum m(0, 2, 6) \quad 9$$

$$F_2(A, B, C) = \sum m(1, 2, 3, 7)$$

$$F_3(A, B, C) = \sum m(4, 7)$$

- c. Explain multiplexer in detail. Implement the following function using 8:1 multiplexer:

$$F(A, B, C, D) = \sum m(0, 2, 4, 5, 8, 11, 14) + d(1, 7, 15) \quad 9$$

UNIT - III

18

- 3 a. Convert the following flip flop and draw the circuit:

- i) SR flip flop to JK flip flop ii) SR flip flop to T flip flop

- b. Give the state transition, characteristic equation, and excitation table for SR, JK and D flip flop. 9

- c. With a neat circuit diagram explain Programmable Logic Array (PLA). Design 7-segment decoder using PLA. 9

UNIT - IV

18

- 4 a. With a relevant circuit, wave form and truth table explain ripple down counter. 9

- b. Explain the following:

- i) Switched tail Counter 9
 ii) Sequence Generator and Sequence Detector
 iii) Serial Adder

- c. Design a mod-5 synchronous counter using JK flip flop and implement the same. 9

UNIT - V

18

- 5 a. Give the output function transition table and state diagram by analyzing the sequential circuit shown in Fig. (a). 12

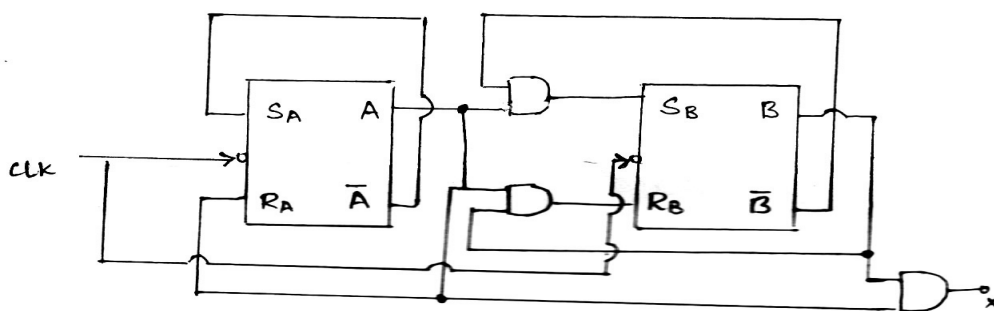


figure Q5(a)

- b. Give the state synthesis table, design equation and circuit diagram for vending machine problem (Mealy Model). 12

- c. Write the VHDL code for :

- i) D-flip flop ii) 8:1 Multiplexer 6