



--	--	--	--	--	--	--	--	--	--

## P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Third Semester, B.E. - Electronics and Communication Engineering

Semester End Examination; Dec. - 2019

Network Analysis and Synthesis

Time: 3 hrs

Max. Marks: 100

**Note:** Answer **FIVE** full questions, selecting **ONE** full question from each unit.

### UNIT - I

- 1 a. State and explain Superposition theorem with an example. 6
- b. Use source transformation to find power delivered by 50 V source in given network of Fig .1(b). 6
- c. For the network shown in Fig.1(c), determine the node voltages  $V_1$ ,  $V_2$  and  $V_3$ . 8
- 2 a. For the network shown in Fig. 2(a), find the current through  $2 \Omega$  resistance using mesh analysis. 6
- b. State and explain Thevenin's theorem with an example. 6
- c. Find the value of load resistance when maximum power is transferred across it and also find the value of maximum power transferred for the network shown in Fig. 2(c). 8

### UNIT - II

- 3 a. Define Q-factor and prove that for a parallel RLC circuit quality factor  $Q_0 = W_0RC$ . 8
- b. A series resonant circuit includes  $1 \mu\text{F}$  capacitor and a resistance of  $16 \Omega$ . If the bandwidth is  $500 \text{ rad/s}$ . Determine the following: 8
- i)  $L$       ii)  $Q$       iii)  $w_0$       iv)  $w_1$  and  $w_2$
- c. Define the following terms: 4
- i) Resonance      ii) Band width
- iii) Half power frequencies      iv) selectivity
- 4 a. Show that; 10
- i) The voltage of capacitor cannot change instantaneously
- ii) The current in an inductor cannot change instantaneously
- b. In the network shown in Fig.4 (b), the switch is changed from the position 1 to the position 2 at  $t = 0$  steady state condition having reached before switching. 10

Find the values of  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ .

### UNIT - III

- 5 a. State and prove; 10
- i) Initial Value Theorem      ii) Final Value Theorem

- b. Find the Laplace transform at, i)  $e^{-at} \cos wt$     ii)  $5 + 4e^{-2t}$  5
- c. Find the Inverse Laplace transform of  $F(s) = \frac{(s+2)}{s^2(s+3)}$ . 5
- 6 a. Prove that the Inverse Laplace transform of the product of two Laplace transform is the convolution of the individual Laplace transform. 7
- b. Referring to the RL circuit of Fig.6(b),  
 i) Write a differential equation for inductor current  
 ii) Find  $I_L(s)$  the Laplace transform of  $i_L(t)$   
 iii) Solve for  $i_L(t)$  by taking the inverse Laplace Transform of  $I_L(s)$  7
- c. Find the initial and final values of the function whose Laplace Transform is,  

$$F(s) = \frac{2s+1}{s^3+6s^2+11s+6}$$
 6

#### UNIT - IV

- 7 a. Explain impedance parameters for a two port network. 4
- b. Determine the Y-parameters for the two port network shown in Fig. 7(b). 8
- c. For the network shown in Fig.7(c), determine h-parameters. 8
- 8 a. Define the following: 4  
 i) Planar graph            ii) Tree            iii) Co-tree            iv) Path
- b. For the graph shown in Fig. 8(b), write the cutset and tieset matrices considering branches 4, 5 and 6 as twigs. 10
- c. Draw the dual of the network shown in Fig. 8(c). 6

#### UNIT - V

- 9 a. Define Hurwitz polynomial. Test whether the polynomial  $p(s) = s^5 + 3s^3 + 2s$  is Hurwitz. 8
- b. Test whether  $p(s) = \frac{s^2+1}{s^3+4s}$  is positive real function. 8
- c. List any four properties of RC driving point immittance function. 4
- 10 a. Realize cauer-II form of the function  $Z_{LC}(s) = \frac{4(s^2+1)(s^2+9)}{s(s^2+4)}$ . 8
- b. Realize Foster- I form of the function  $Z(s) = \frac{(s+1)(s+4)}{(s+5)(s+3)}$ . 8
- c. Justify which of the function is RL or RC impedance function?  
 i)  $Z(s) = \frac{3(s+2)(s+1)}{s(s+3)}$             ii)  $Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$  4

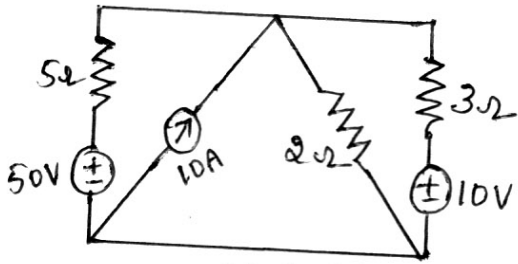


fig (1.b)

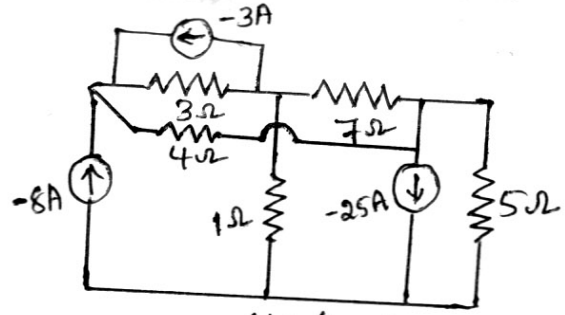


fig (1.c)

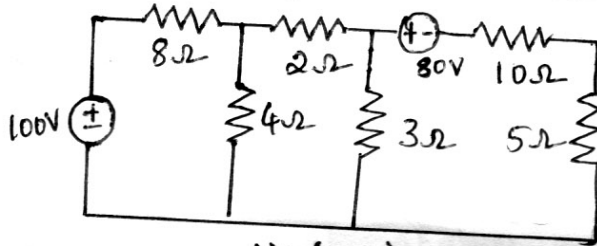


fig (2.a)

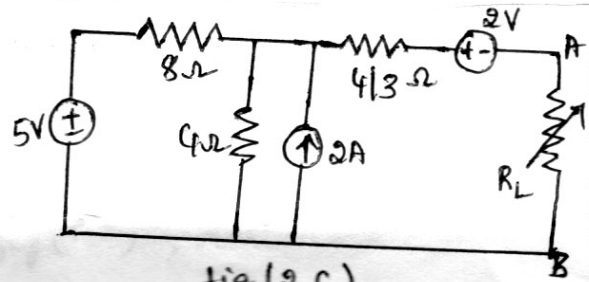


fig (2.c)

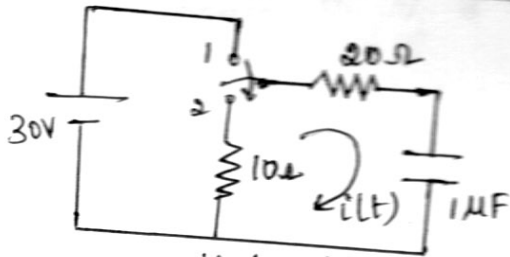


fig (4.b)

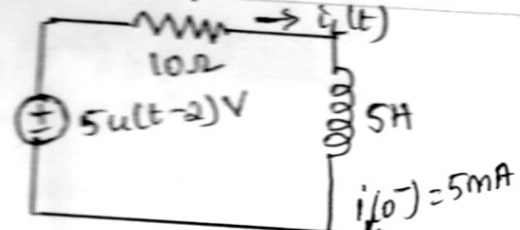


fig (6.b)

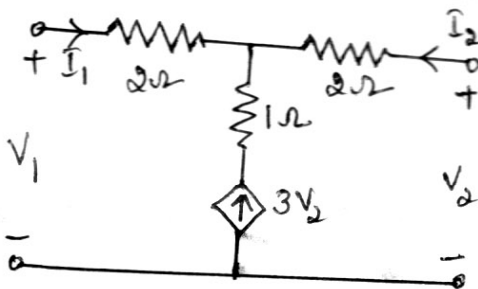


fig (7.b)

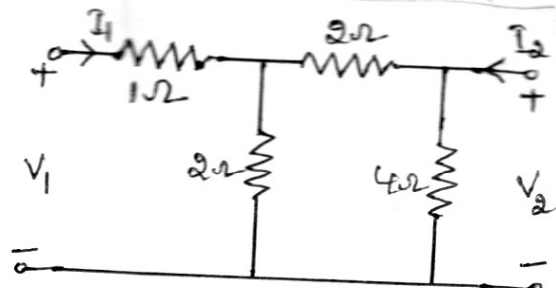


fig (7.c)

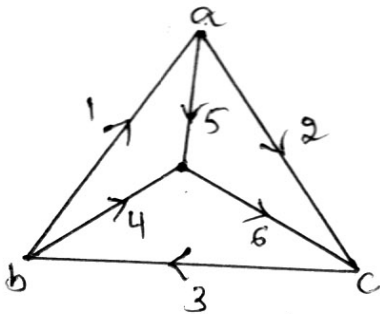


fig (8.b)

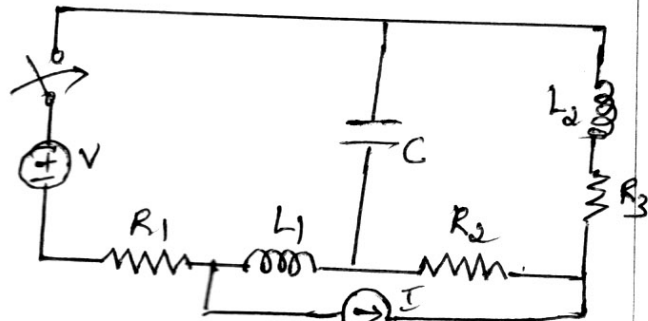


fig (8.c)

\*\*\*