

--	--	--	--	--	--	--	--	--	--



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

First Semester, B.E. - Semester End Examination; Dec. - 2019

Basic Electrical Engineering

(Common to All Branches)


Time: 3 hrs

Max. Marks: 100

Note: Answer **FIVE** full questions, selecting **ONE** full question from each unit.

UNIT - I

- 1 a. State and explain Ohm's law. 4
- b. Define coefficient of coupling and derive the expression for energy stored in an inductor. 8
- c. State the following laws: 8
 - i) Faraday's laws of electromagnetic induction
 - ii) Fleming's left hand and Right hand rule
 - iii) Lenz's Law
- 2 a. State and explain Kirchhoff's laws applied to DC circuits. 6
- b. Apply Kirchhoff's laws to find potential difference between x and y shown in the network. 8

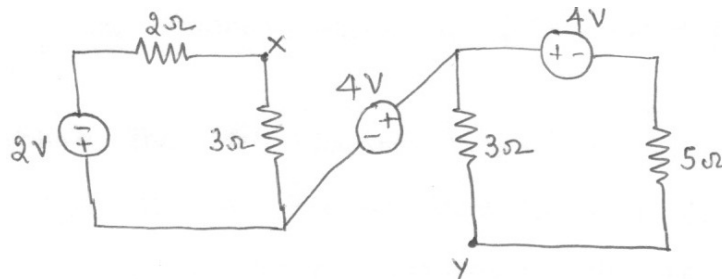

- c. The self-inductance of a coil having 500 turns is 0.25 Henry. If 60% of the flux is linked with a second coil of 10,000 turns. Calculate; 6
 - i) Mutual inductance of the two coil
 - ii) EMF induced in the second coil when current in the first coil changes at the rate of 100 A/s.

UNIT - II

- 3 a. Define the following: 6
 - i) RMS value
 - ii) Average value
 - iii) Form factor
 - iv) Peak factor
- b. Show that the average power consumed by a pure capacitance is zero. 6
- c. A series circuit with $R = 10 \Omega$, $L = 50 \text{ mH}$ and $C = 100 \mu\text{F}$ is supplied with 200 V, 50 Hz find 8
 - i) Impedance
 - ii) Current
 - iii) Power
 - iv) Power factor
- 4 a. With the usual notations, prove that the power consumed in R-L circuit is $VI \cos \phi$ 6
- b. Explain the term phase and phase difference applied to ac circuits. Distinguish between lagging power factor and leading power factor. 6
- c. A circuit consists of branches A and B connected in parallel, is connected across a 220 V, 50 Hz supply; 8

Branch A: A resistance of 7Ω in series with 0.0125 H inductor

Branch B: A resistance of 8Ω in series with $1000 \mu\text{F}$ capacitor

Find the branch current and total currents. Draw phasor diagram.

UNIT - III

- 5 a. Establish the relationship between phase and line value of voltages and currents in 3-phase star connected circuit. Draw the phasor diagram and obtain the expression for power. 8
- b. With a neat diagram, explain the construction and working principle of dynamometer type wattmeter. 6
- c. With wiring diagram, explain two-way and three-way control of lamp. 6
- 6 a. With relevant diagrams show that two wattmeter are enough to measure three phase power. 6
- b. What is the necessity of earthing? With neat figure explain plate earthing. 8
- c. A balanced delta connected load $(8 + j6) \Omega$ per phase is supplied from a 3-phase 440 V source. Find the line current, power factor, power per phase and total power. 6

UNIT - IV

- 7 a. With neat figure, explain the constructional feature of DC machines. 8
- b. Define torque. With usual notation derive the expression for the armature torque developed in DC motor. 8
- c. Calculate the flux per pole required for 4-pole generator with 360 conductors generating 250 V at 1000 rpm , When the armature is, i) Lap connected ii) Wave connected. 4
- 8 a. What is back emf in DC motor? Illustrate its significance. 6
- b. With usual notation, derive the emf equation of a synchronous generator. 6
- c. A 12 pole 500 rpm star connected alternator has 60 slots with 20 conductors per slot. The flux per pole is 0.02 Weber and is distributed sinusoidally. The winding factor is 0.93 , calculate; 8
i) Frequency ii) Phase emf iii) Line emf. Assume coil is full pitched.

UNIT - V

- 9 a. Explain the concept of rotating magnetic field in induction motor. 8
- b. Explain why induction motor needs a starter during starting? 6
- c. What is slip in an induction motor? Find the slip and speed of a 4 pole induction motor with frequency of emf in the stator is 50 Hz and in the rotor is 1.5 Hz . 6
- 10 a. Derive the EMF equation of a transformer from fundamentals and obtain expression for transformation ratio. 6
- b. The primary and secondary winding of a 500 kVA transformer have resistance of 0.5Ω and 0.002Ω respectively. The primary and secondary voltages are 10000 V and 400 V respectively and the core loss is 3 kW , the power factor on the load is 0.8 , calculate the efficiency on
i) Full load ii) Half full load 8
- c. Explain various losses that occur in a transformer? How are they minimized 6