

--	--	--	--	--	--	--	--	--	--



P.E.S. College of Engineering, Mandya - 571 401

(An Autonomous Institution affiliated to VTU, Belagavi)

Third Semester, B.E. - Electrical and Electronics Engineering

Semester End Examination; Dec. - 2019

Digital Electronic Circuits

Time: 3 hrs

Max. Marks: 100

Note: i) Answer **FIVE** full questions, selecting **ONE** full question from each unit

ii) Missing data if any, may be suitably assume.

UNIT - I

1 a. Convert the given Boolean function into min-term Canonical form,

i) $R = f(a, b, c) = (\bar{a} + b)(b + \bar{c})$

6

ii) $P = f(x, y, z) = x + \bar{x} \bar{z} (y + \bar{z})$

b. Simplify the following function into minimum number of literals,

i) $xyz + \bar{x}y + xy\bar{z}$

ii) $xz + \bar{x}zy$

8

iii) $y(w\bar{z} + wz) + xy$

iv) $xy + \bar{x} + \bar{x}y$

c. State and prove;

i) Distributive

ii) Absorption law of Boolean Algebra using identities

6

2 a. State and Prove the De-Morgan's theorem for three variables using truth table.

6

b. Simplify the following Boolean expression,

i) $a + \bar{a}b + ab\bar{c}$

ii) $a + \bar{a}b + abc + a\bar{c}$

iii) $ab + \bar{a}c + \bar{a}bc [ab + c]$

6

c. Convert the following expression into standard SOP form:

i) $AC + AB + BC = f(A, B, C)$

ii) $A + ABC = f(A, B, C)$

8

UNIT - II

3 a. Find the minimal product of the following Boolean function using Karnaugh map,

i) $f(a, b, c, d) = \sum(7, 9, 11, 12, 13, 14) + \sum d(3, 5, 6, 15)$

8

ii) $f(a, b, c, d) = \prod(2, 8, 11, 15) + \prod d(3, 12, 14)$

b. Simplify the given Boolean function using Quine Mccluskey method,

$y = f(a, b, c, d) = \sum(0, 1, 2, 6, 7, 9, 10, 12) + d(3, 5)$. Verify the result using K-map.

12

4 a. With a neat logic diagram, explain Look-ahead carry adder.

10

b. With a neat logic diagram, explain;

i) Half adder

10

ii) Full adder


UNIT - III

- 5 a. Differentiate Latch and Flip flop. 4
- b. With a neat logic diagram, explain Master Slave JK flip flop. 8
- c. With a neat logic diagram, explain 8 line to 3 line, priority encoder. 8
- 6 a. Realize the following Boolean function: 10


$$P = f(w, x, y, z) = \sum(0, 1, 5, 6, 7, 10, 15)$$
 - using, i) 16 to 1 MUX ii) 8: 1 MUX iii) 4: 1 MUX
- b. Distinguish between a decoder and an encoder. Implement full adder using IC 74138. 10

UNIT-IV

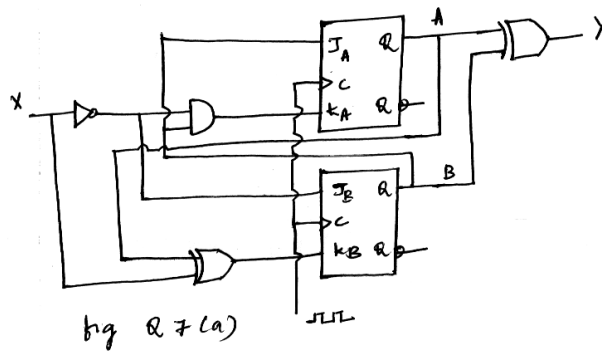- 7 a. Construct the excitation table, transition table, state table and state diagram for the Moore sequential circuit shown below, 10



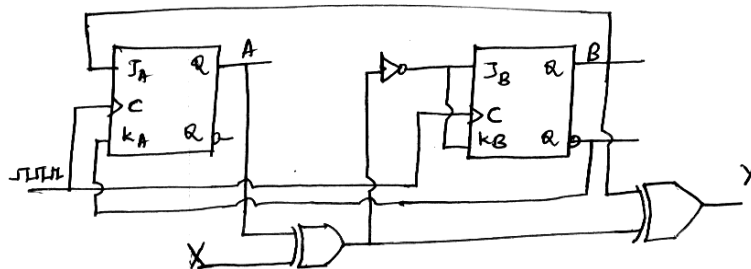- b. With a neat logic diagram, explain; 10
 - i) SISO ii) SIPO
- 8 a. Analyze the synchronous sequential circuit given below, 10



- b. Design a synchronous 5421 code sequencer using positive edge triggered D flip-flop with minimal combinational circuit. 10

UNIT - V

- 9 a. With a neat circuit diagram, explain the operation of 2-input TTL NAND gate with Totem pole output. 10
- b. With a neat diagram, explain weighted DAC and successive approximation ADC. 10
- 10a. Draw a 4 bit D/A converter using R-2R resistors and explain it working. 10
- b. With a neat circuit diagram, explain two inputs CMOS NAND gate. 10