



**P.E.S. College of Engineering, Mandya - 571 401**  
*(An Autonomous Institution affiliated to VTU, Belagavi)*  
**Seventh Semester, B.E. - Electrical and Electronics and Engineering**  
**Semester End Examination; Dec. - 2019**  
**AC - DC Drives**

Time: 3 hrs

Max. Marks: 100

*Note: Answer FIVE full questions, selecting ONE full question from each unit.*

**UNIT - I**

- 1 a. With a neat block diagram, explain the functions of the components of an electric drive. 6
- b. With neat circuit diagram and speed-torque characteristics, explain the dynamic braking and plugging operations of a separately excited DC motor. 8
- c. A 220 V, 750 rpm, 150 A separately excited DC motor has an armature resistance of  $0.1 \Omega$ . It is fed from a single phase fully controlled rectifier with as AC voltage source of 230 V, 50 Hz. Assume continuous conduction and calculate; 6
- i) Firing angle for rated motor torque and 500 rpm
- ii) Motor speed  $\alpha = 140^\circ$  and rated torque
- 2 a. For a separately excited DC motor controlled by a 1- $\phi$  fully controlled rectifier. Obtain the expression for output voltage during discontinuous conduction mode. Obtain the boundary conditions and draw the speed torque characteristics. 12
- b. Define continuous conduction and discontinuous conduction mode. For a DC separately excited motor fed from 1- $\phi$  half controlled rectifier. Explain the motor operation in continuous conduction mode and arrive at the expression for output voltage, speed and torque. 8

**UNIT - II**

- 3 a. With neat circuit and relevant waveforms, explicate the operation of a 3- $\phi$  fully controlled rectifier fed separately excited DC motor in discontinuous conduction mode. 10
- b. Exemplify the operation of a DC drive in all four quadrants, when fed by single phase dual converter? Also state how speed reversal can be obtained? 10
- 4 a. Explain and analyse the operation of a DC separately excited motor during; 10
- i) Regenerative braking
- ii) Dynamic braking when controlled by a DC converter.
- Plot the speed torque characteristics.
- b. Explain the operation of four quadrant chopper with circuit diagram and operating characteristics. 10

**UNIT - III**

- 5 a. With a neat block diagram, explain the phase locked loop control of DC motor. 10
- b. Derive an expression for closed loop operation of a separately excited DC motor for change in voltage. 10
- 6 a. Explain the operation of 3- $\phi$  induction motor with unbalanced supply voltage and single phasing. Draw the corresponding speed torque characteristics. 10
- b. Obtain the performance equations of a 3- $\phi$  IM. 10

**UNIT - IV**

- 7 a. With a neat circuit and relevant wave forms, elaborate the operation of VSI fed IM drive. 10
- b. Using V/F control, explain the speed control phenomenon of a 3- $\phi$  Induction motor. 10
- 8 a. Explain in detail with relevant circuit and characteristics, how a static Scherbius drive is used to control speed of a wound rotor Induction motor below synchronous speed. 10
- b. With neat diagrams, exemplify AC dynamic braking, self-excited braking and zero-sequence braking of Induction motor drives. 10

**UNIT - V**

- 9 a. Explain the operation of synchronous motor, when fed from a fixed frequency supply. 10
- b. With a neat circuit, discuss the operations of a self-controlled synchronous motor drive employing load commutated thyristor inverter. 10
- 10 a. With a neat sketch, explain the various processes involved for manufacturing cement in a cement mill drive system. 10
- b. Explain clearly the rating and different types of motors employed in the textile mill industry for different operations. 10

\* \* \*